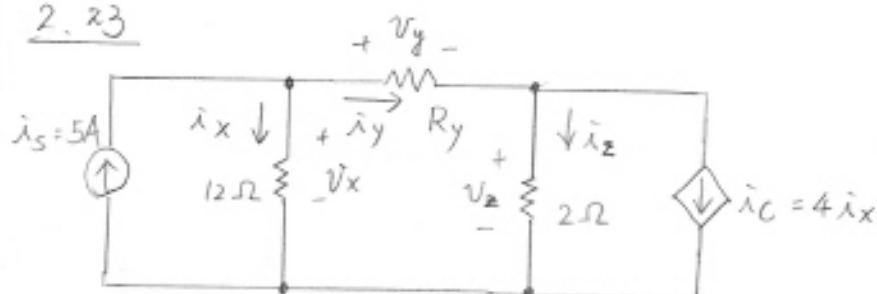


2.23




$$i_y = 5 - i_x$$

$$i_z = i_y - i_c = 5 - 5i_x$$


$$\text{KVL: } 12i_x - 3(5 - i_x) - 2(5 - 5i_x) = 0$$

$$\Rightarrow i_x = 1 \text{ A}$$

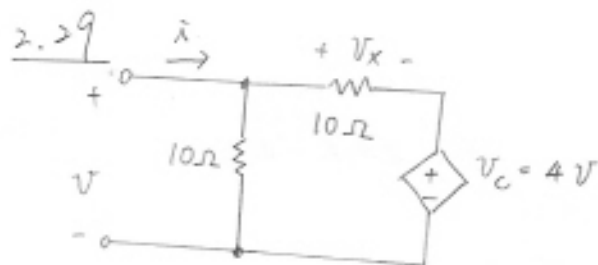

$$v_x = V - v_c = -3 \text{ V}$$
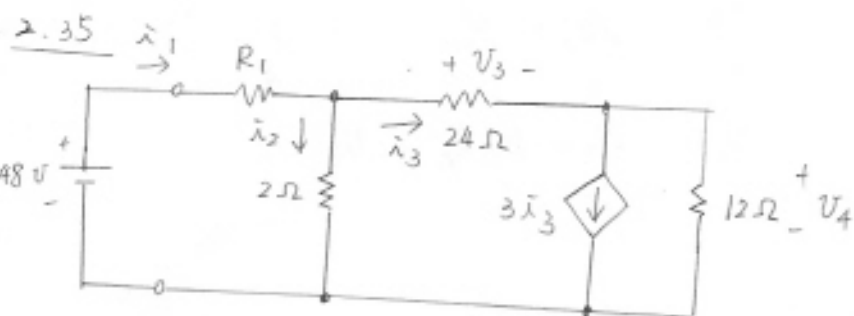
$$i = \frac{V}{10} + \frac{v_x}{10} = -\frac{V}{5} \Rightarrow R_{eq} = \frac{V}{i} = -5 \Omega$$



$$(a) i_3 = \frac{v_3}{24} = 1.5 \text{ A}$$

$$v_4 = 12(i_3 - 3i_3) = -36 \text{ V}$$

$$i_2 = \frac{(v_3 + v_4)}{2} = 0$$


$$i_1 = i_2 + i_3 = 1.5 \text{ A}$$

$$(b) R_1 = (48 - v_3 - v_4) / i_1 = 32 \Omega, R_{eq} = \frac{48}{i_1} = 32 \Omega$$

$$(c) P_s = 48 \cdot i_1 + v_4 (-3i_3) = 234 \text{ W}$$

$$P_d = R_1 \cdot i_1^2 + 2i_2^2 + 24i_3^2 + \frac{v_4^2}{12} = 234 \text{ W} = P_s$$

2.36

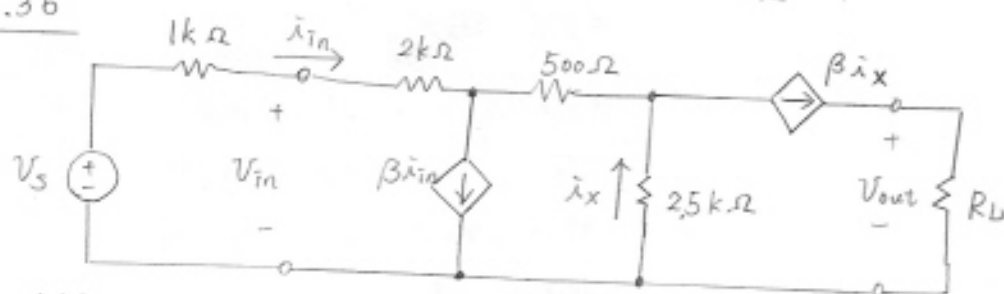

$$(a) \text{KCL at bottom node: } -i_{in} + \beta i_{in} - i_x + \beta i_x = 0 \Rightarrow i_x = -i_{in}$$

$$(b) v_{in} = 2i_{in} + 0.5(i_{in} - \beta i_{in}) + 2.5(-i_x) = (5 - 0.5\beta) i_{in}$$


$$R_{in} = \frac{v_{in}}{i_{in}} = (5 - 0.5\beta) \text{ k}\Omega$$

$$(c) i_{in} = \frac{2}{(1 + R_{in})}, v_{out} = R_L \cdot (\beta i_x) = -5\beta i_{in}$$

$\beta$	$R_{in} (\text{k}\Omega)$	$i_{in} (\text{mA})$	$v_{out} (\text{V})$
8	1	1	-40
10	0	2	-100
12	-1	$\infty$	$-\infty$
14	-2	-2	140

The model is invalid for  $\beta = 12$ , which requires infinite current from all three sources.

2.40

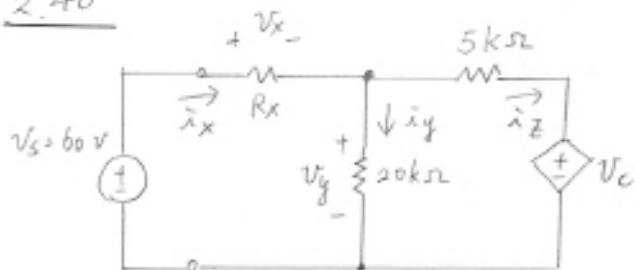


$$\hat{V}_y = \hat{i}_y \cdot 20k = 20V, \quad \hat{i}_z = (\hat{V}_y - \hat{V}_C) / 5 = 1mA$$

$$\hat{i}_x = \hat{i}_y + \hat{i}_z = 2mA, \quad \hat{V}_x = R_x \cdot \hat{i}_x = 10V$$

$$\hat{V}_S = \hat{V}_x + \hat{V}_y = 30V, \quad k = \frac{30}{V_S} = 0.5$$

$$V_x = \hat{V}_x / k = 20V, \quad V_y = \hat{V}_y / k = 40V, \quad V_C = \frac{15k \hat{i}_y}{k} = 30V$$

2.46

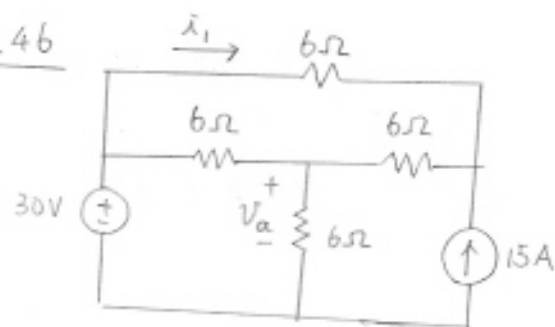

with 30-V source active:

$$R_{eq} = [6 \parallel (6+6)] + 6 = 10$$

$$V_{a-1} = 6 \cdot 30 / R_{eq} = 18V$$


with 15-A source active:

$$R_{eq} = 6 \parallel (6+6 \parallel 6) = 3.6$$

$$V_{a-2} = 6 \parallel 6 \times R_{eq} \times 15 / (6+6 \parallel 6) = 18$$

$$V_a = V_{a-1} + V_{a-2} = 36V$$

2.55

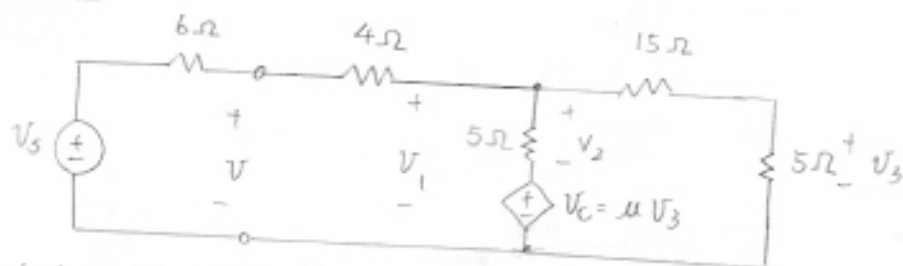

$$(a) \quad V_3 = 5V_1 / (15+5) = V_1 / 4, \quad V_2 = V_1 - \mu V_3 = (4-\mu) V_1 / 4$$

$$(b) \quad V_2 = (4-\mu) \cdot 20 / 4 = 20-5\mu, \quad \hat{i} = V_2 / 5 + V_1 / (15+5) = 5-\mu$$

$$V = 4\hat{i} + V_1 = 40-4\mu, \quad R_{eq} = \frac{V}{\hat{i}} = \frac{(40-4\mu)}{(5-\mu)}$$

$$(c) \quad \mu=0 \Rightarrow R_{eq} = 8\Omega$$

$$V_C=0 \Rightarrow R_{eq} = 4 + 5 \parallel (15+5) = 8\Omega$$

(d)


$$\hat{i} = 60 / (6 + R_{eq}), \quad V = R_{eq} \cdot \hat{i} = 60 R_{eq} / (6 + R_{eq})$$

$$P = V \cdot \hat{i} = 3600 R_{eq} / (6 + R_{eq})^2$$

$\mu$	$R_{eq} (\Omega)$	$\hat{i} (A)$	$V (V)$	$P (W)$
1	9	4	36	144
5	$\infty$	0	60	0
6	-16	-6	96	-576
7	-6	$\infty$	$-\infty$	$-\infty$
9	-1	12	-12	-144
10	0	10	0	0

This model is invalid for  $\mu=7$ , which requires infinite current from both sources.

2.57

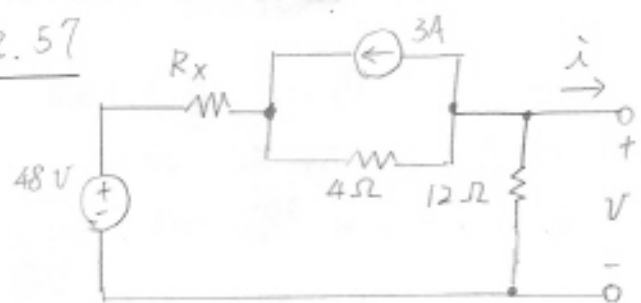

with  $\bar{i} = 0$ :

$$V_{oc-1} = 12 \times 48 / (4 + 12) = 36 \text{ V}$$

$$V_{oc-2} = (4 \parallel 12) (-3) = -9 \text{ V}$$

$$V_{oc} = 36 - 9 = 27 \text{ V}$$

with  $V = 0$ :


$$\bar{i}_{sc-1} = 48/4 = 12 \text{ A}$$

$$\bar{i}_{sc-2} = -3 \text{ A}, \quad \bar{i}_{sc} = 12 - 3 = 9 \text{ A}$$

$$R_t = 27/9 = 3 \Omega$$

for dead network:  $R_t = 4 \parallel 12 = 3 \Omega$

2.61

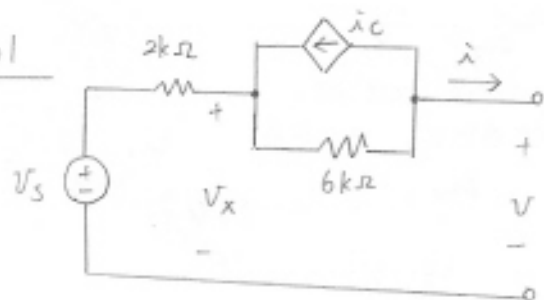

with  $V_s = 0$ :

$$\bar{i} = -\bar{i}_t, \quad \bar{i}_c = -4 \bar{i}_t$$

$$V_t = 2k \bar{i}_t + 6k(\bar{i}_t - \bar{i}_c) = 32k \cdot \bar{i}_t$$


$$R_t = V_t / \bar{i}_t = 32k \Omega$$

with  $\bar{i} = 0$ :



$$\bar{i}_c = 0 \Rightarrow V_{oc} = V_s$$

$$\bar{i}_{sc} = V_{oc} / R_t = V_s / 32k \Omega$$




2.67

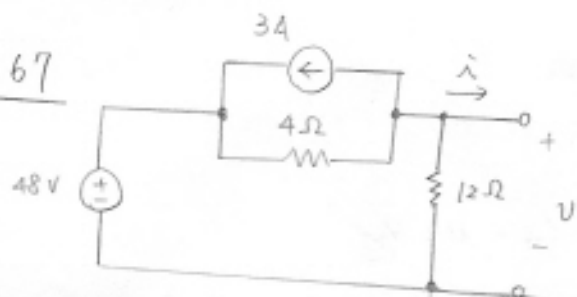
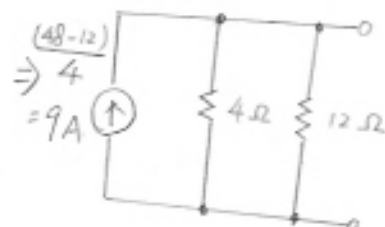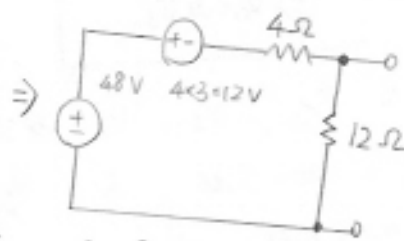
$$\bar{i}_{sc} = 9 \text{ A}, \quad R_t = 4 \parallel 12 = 3 \Omega, \quad V_{oc} = 3 \times 9 = 27 \text{ V}$$




2.71

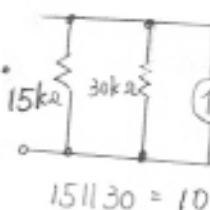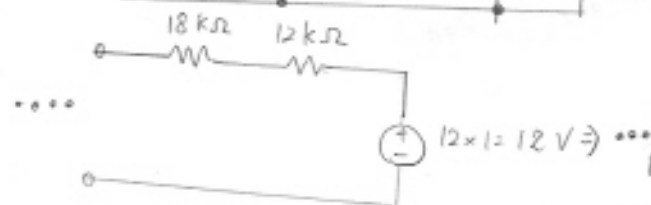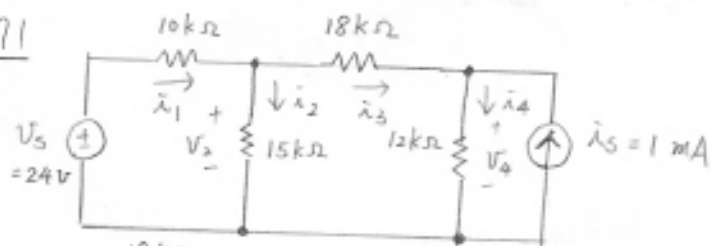

$$\bar{i}_1 = (24 - 4) / (10k + 10k) = 1 \text{ mA}$$

2.77

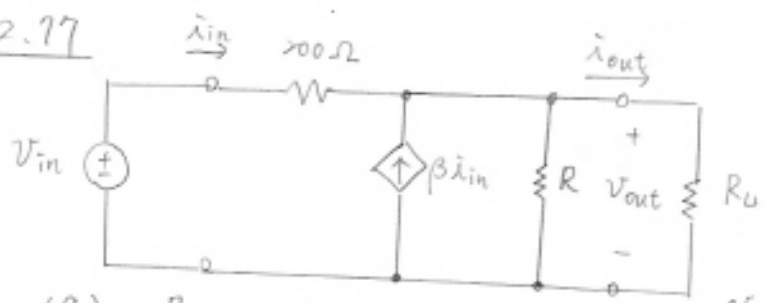

(a)  $R_L = 0$ :  $V_{out} = 0$ ,  $i_{in} = \frac{V_{in}}{200}$ ,  $i_{out} = i_{in} + 49 i_{in} = 50 \left( \frac{V_{in}}{200} \right)$   
 $\Rightarrow \frac{i_{out}}{V_{in}} = 0.25$

$R_L = \infty$ :  $i_{out} = 0$ ,  $V_{out} = 36 (i_{in} + 49 i_{in}) = 1800 i_{in}$   
 $i_{in} = (V_{in} - V_{out}) / 200$ ,  $V_{out} = 1800 (V_{in} - V_{out}) / 200 = 9 (V_{in} - V_{out})$   
 $\Rightarrow V_{out} / V_{in} = 0.9$


(b)  $i_{out-sc} = 0.25 V_{in}$ ,  $V_{out-oc} = 0.9 V_{in}$ ,  $R_t = \frac{V_{out-oc}}{i_{out-sc}} = 3.6 \Omega$

with  $V_{in} = 0$ ,  $V_{out} = V_t$ ,  $i_{out} = -i_t \Rightarrow i_{in} = -V_t / 200$

$i_t = \frac{V_t}{36} - 49 i_{in} - i_{in} = \frac{V_t}{36} - 50 \left( \frac{-V_t}{200} \right) = \frac{5 V_t}{18}$

$R_t = V_t / i_t = 3.6 \Omega$

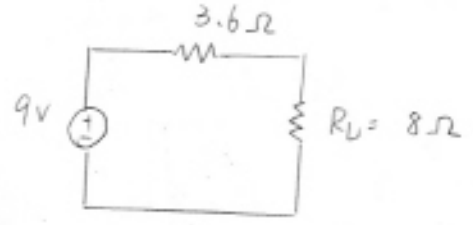(c)  $V_{out-oc} = 0.9 V_{in} = 9 V$ ,  $R_t = 3.6 \Omega$



$V_{out} = R_L \cdot \frac{V_{out-oc}}{R_t + R_L} = 6.21 V$

$P_{out} = \frac{V_{out}^2}{R_L} = 4.82 W$

$i_{in} = (V_{in} - V_{out}) / 200 = 0.019 A$ ,  $P_{in} = V_{in} i_{in} = 0.19 W$

$P_{out} / P_{in} = 25.4$