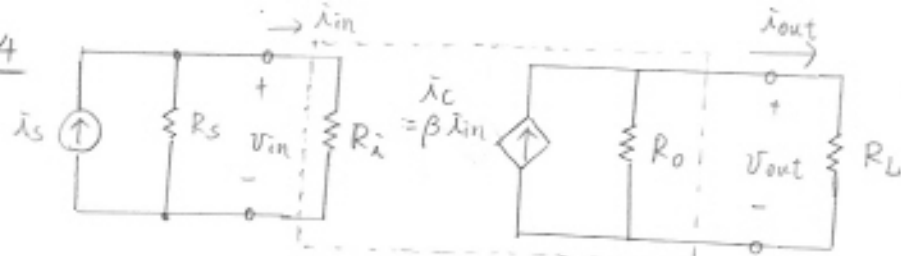



3.14



$$A_i = \frac{300}{500} \beta \frac{5k}{6k} = 60 \Rightarrow \beta = 120$$

$$A_v = \frac{1k \cdot i_{out}}{300 \cdot i_s} = \frac{10}{3} A_i = 200$$


3.16

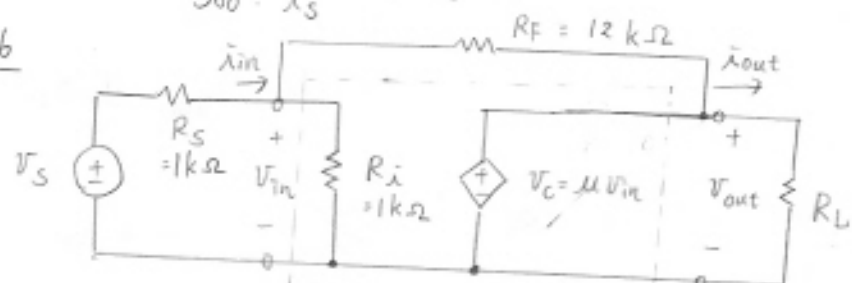

$$i_{in} = \frac{v_{in}}{R_i} + \frac{v_{in} - v_c}{R_F} = \left(\frac{1}{R_i} + \frac{1 - \mu}{R_F} \right) v_{in} = \left(\frac{1}{1k} + \frac{9}{12k} \right) v_{in} = \frac{1}{4k} v_{in}$$

$$R_i' = \frac{v_{in}}{i_{in}} = 4k\Omega, \quad A_v = \frac{v_{out}}{v_s} = \frac{v_{in}}{v_s} \times \frac{v_c}{v_{in}} = \frac{R_i'}{R_s + R_i}, \quad \mu = 8$$


3.20

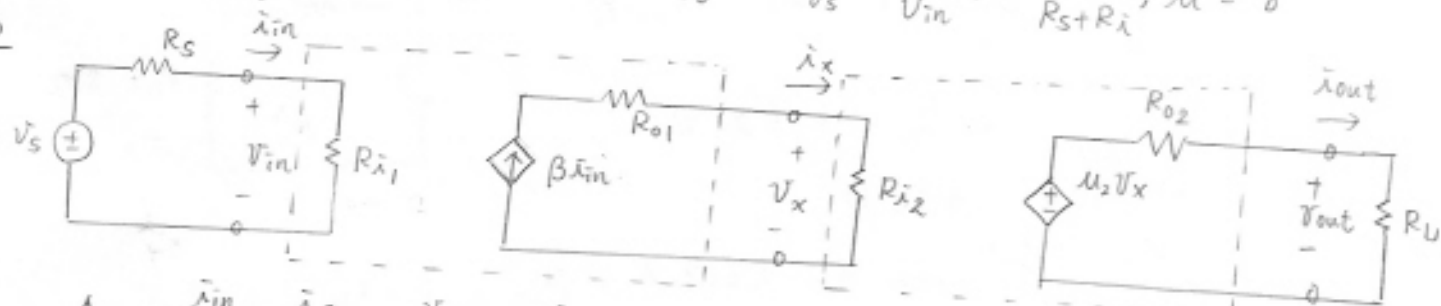


$$A_v = \frac{i_{in}}{v_s} \cdot \frac{i_{o1}}{i_{in}} \cdot \frac{v_x}{i_{o1}} \cdot \frac{v_{o2}}{v_x} \cdot \frac{v_{out}}{v_{o2}} = \frac{1}{500} \times 25 \times (1k \parallel 1k) \times \mu_2 \times \frac{8}{8+2}$$

$$= 20 \mu_2 = -300, \quad \mu_2 = -15$$

3.23

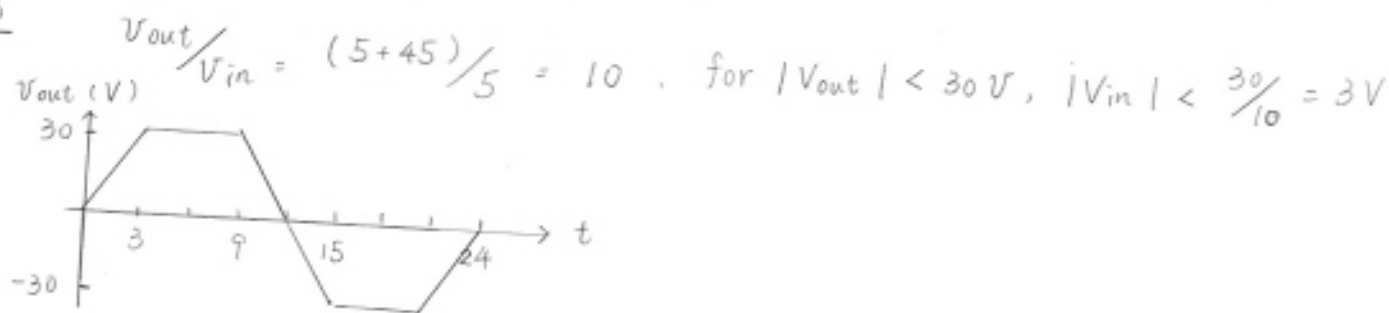


3.25

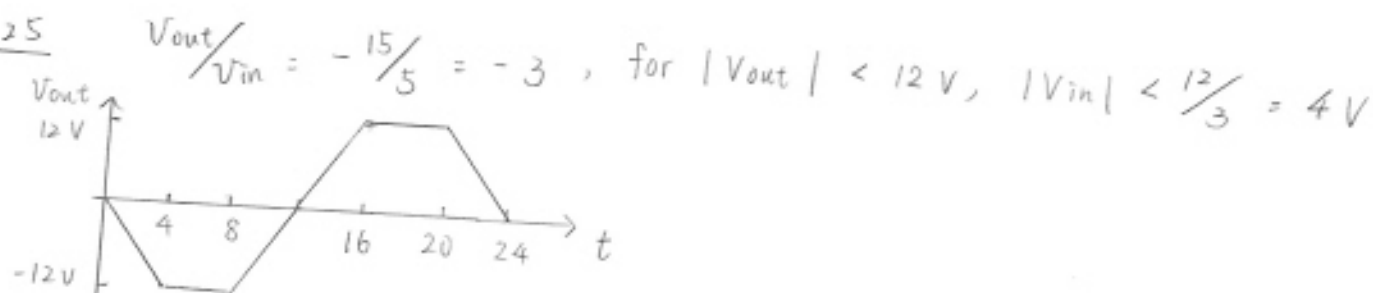

3.27

$$V_{out} = -\left(\frac{16}{4}\right)(V_i - 3) = -4V_i + 12$$

$$\text{for } |V_{out}| < 12V, \quad 0 < V_i < \frac{24}{4} = 6V$$

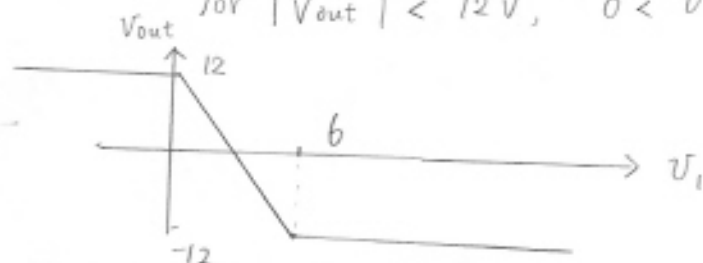

3.29

$$V_{out}/V_{in} = -1 \Rightarrow \text{inverting amplifier with } R_F/R_i = 1$$

$$\text{take } R_F = R_i = 2R$$

$$\text{pin connection: } 1-6, 2-4, 3-9, 5-7$$

$$V_{out}/V_{in} = 3 \Rightarrow \text{noninverting amplifier with } R_F/R_i = 2$$

$$\text{take } R_F = 2R, R_i = R$$

$$\text{pin connection: } 1-4, 2-8, 3-9, 5-6$$

$$V_{out}/V_{in} = -3 \Rightarrow \text{inverting amplifier with } R_F/R_i = 3$$

$$\text{take } R_F = 2R, R_i = R \parallel 2R = \frac{2R}{3}$$

$$\text{pin connection: } 1-7-8, 2-4, 3-9, 5-6$$

3.32

$$V_{out} = -[2V_a + 10(10V_b)]$$


$$= -2V_a - 100V_b$$

$$V_{ps} > 2 \times 1.5 + 100 \times 0.05 = 8V$$

$$V_1 = \frac{5+5}{5} V_a = 2V_a$$

$$V_2 = \frac{5+45}{5} V_b = 10V_b$$

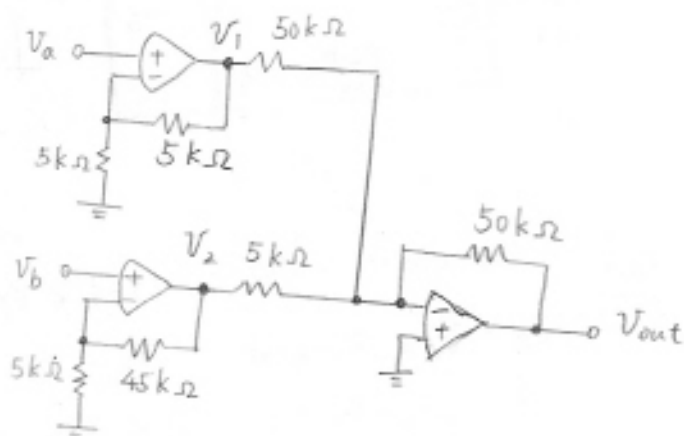
$$V_{out} = -\frac{50}{50} V_1 - \frac{50}{5} V_2 = -2V_a - 100V_b$$



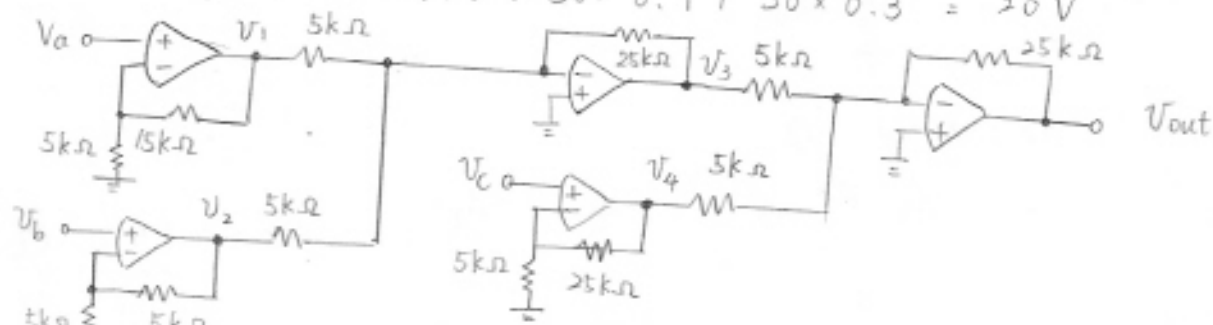3.36

$$V_{out} = -5[(-20V_a - 10V_b) + 6V_c] = 100V_a + 50V_b - 30V_c$$


$$V_{ps} > 100 \times 0.06 + 50 \times 0.1 + 30 \times 0.3 = 20V$$




$$V_1 = \frac{5+15}{5} V_a = 4V_a, \quad V_2 = \frac{5+5}{5} V_b = 2V_b, \quad V_3 = -\frac{25}{5} V_1 - \frac{25}{5} V_2 = -20V_a - 10V_b$$

$$V_4 = \frac{5+25}{5} V_c = 6V_c, \quad V_{out} = -\frac{25}{5} V_3 - \frac{25}{5} V_4 = 100V_a + 50V_b - 30V_c$$

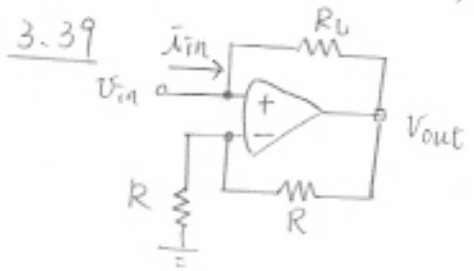
3.37 $V_1 = 1, V_2 = V_3 = 0 \Rightarrow V_{out} = -(R_F/R_1) \times 1 = -1 \Rightarrow R_1 = R_F$
 $V_2 = 1, V_1 = V_3 = 0 \Rightarrow V_{out} = -(R_F/R_2) \times 1 = -2 \Rightarrow R_2 = R_F/2$
 $V_3 = 1, V_1 = V_2 = 0 \Rightarrow V_{out} = -(R_F/R_3) \times 1 = -4 \Rightarrow R_3 = R_F/4$
 $V_{out} = -R_F (V_1/R_1 + V_2/R_2 + V_3/R_3) = -(V_1 + 2V_2 + 4V_3)$



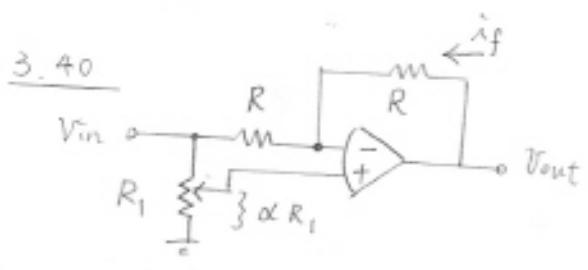3.39 $V_n = \frac{R}{R+R} V_{out} = \frac{1}{2} V_{out}, V_{in} = V_p = V_n \Rightarrow V_{out} = 2V_{in}$
 $\tilde{i}_{in} = \frac{V_{in} - V_{out}}{R_L} = -\frac{V_{in}}{R_L} \Rightarrow \frac{V_{in}}{\tilde{i}_{in}} = -R_L$




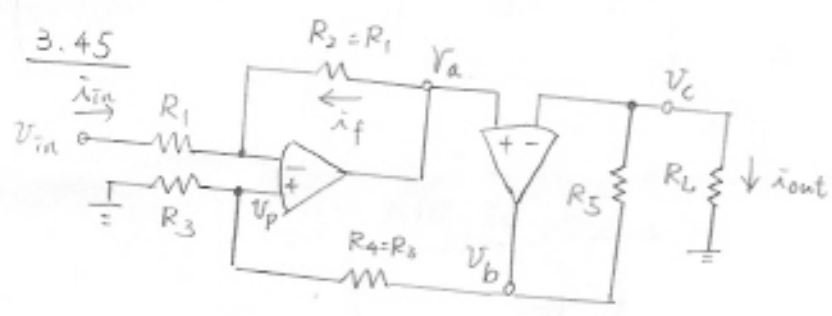3.40 $V_n = V_p = (\alpha R_1/R_1) V_{in} = \alpha V_{in}$
 $(V_{in} - V_n)/R = -\tilde{i}_f$
 $V_{out} = V_n + R\tilde{i}_f = \alpha V_{in} + \alpha V_{in} - V_{in} = (2\alpha - 1) V_{in} = \begin{cases} V_{in}, \alpha = 1 \\ -V_{in}, \alpha = 0 \end{cases}$



3.45 (a) $V_p = R_4 V_b / (R_4 + R_3) = \frac{1}{2} V_b$
 $\tilde{i}_{in} = (V_{in} - V_p)/R_1, \tilde{i}_f = -\tilde{i}_{in}$
 $V_a = V_p + R_2 \tilde{i}_f = \frac{V_b}{2} - R_2 (V_{in} - \frac{V_b}{2})/R_1$
 $= V_b - V_{in}$
 $V_c = V_a = V_b - V_{in}$

(b) For linear region: $|V_a| < V_{ps}$ and $|V_b| < V_{ps}$
 $V_a = V_c = R_L \cdot \tilde{i}_{out}, V_b = V_c + R_5 \cdot \tilde{i}_{out} = (R_L + R_5) \cdot \tilde{i}_{out}$
 $\Rightarrow |(R_L + R_5) \cdot \tilde{i}_{out}| < V_{ps} \Rightarrow (R_L + R_5) \cdot \tilde{i}_{out}|_{max} < V_{ps}$
 $\Rightarrow R_L < (V_{ps}/\tilde{i}_{out}|_{max}) - R_5$

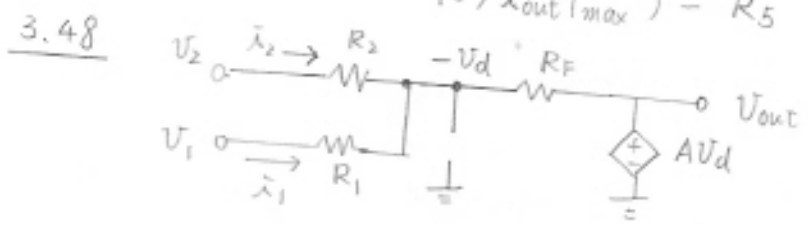

3.48 $A V_d + R_F (\tilde{i}_1 + \tilde{i}_2) + V_d = 0$
 $\tilde{i}_1 = \frac{V_1 + V_d}{R_1}, \tilde{i}_2 = \frac{V_2 + V_d}{R_2} \Rightarrow (A + \frac{R_F}{R_1} + \frac{R_F}{R_2} + 1) V_d = -\frac{R_F}{R_1} V_1 - \frac{R_F}{R_2} V_2$
 $V_{out} = A V_d = \frac{-A}{A + \frac{R_F}{R_1} + \frac{R_F}{R_2} + 1} (\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2)$