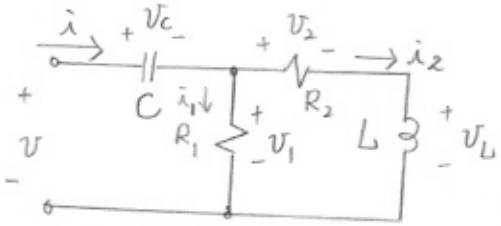
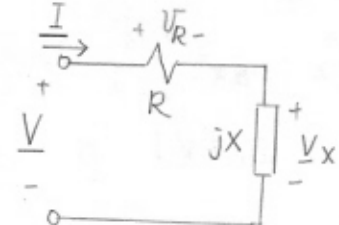
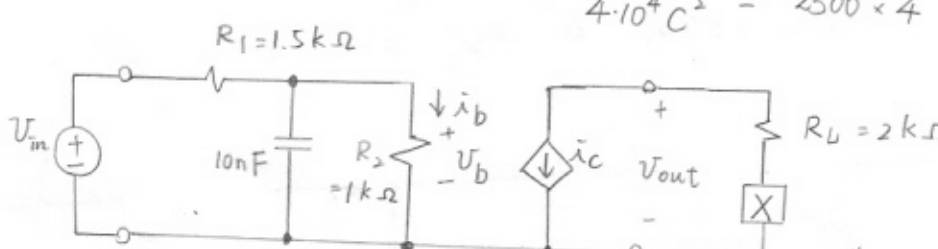


6.7  $A = (1+jx)/(1+ jy) = (1+jx)(1-jy)/(1+y^2)$   
 $= [1+xy + j(x-y)]/(1+y^2) \Rightarrow \angle A = \tan^{-1}(\frac{x-y}{1+xy})$   
 $A = [(1+x^2)^{1/2} \angle \tan^{-1} x] / [(1+y^2)^{1/2} \angle \tan^{-1} y] \Rightarrow \angle A = \tan^{-1} x - \tan^{-1} y$   
 $\therefore \tan^{-1}(\frac{x-y}{1+xy}) = \tan^{-1} x - \tan^{-1} y$

6.17  $\underline{I} = 2.6 \angle -22.6^\circ - 9 \angle -90^\circ - 12 \angle -66.4^\circ$   
 $= (2.4 - j1.0) - (0 - j9) - (4.8 - j11) = -2.4 + j19$   
 $= 19.2 \angle 97.2^\circ \Rightarrow i = 19.2 \cos(\omega t + 97.2^\circ) \text{ A}$

6.24   $Z_1 = 20 \parallel (4+j8) = 5+j5 = 7.07 \angle 45^\circ$   
 $Z = -j10 + Z_1 = 7.07 \angle -45^\circ$   
 $\underline{I} = 10/Z = 1.41 \angle 45^\circ \Rightarrow i = 1.41 \cos(2000t + 45^\circ)$   
 $\underline{V}_C = -j10 \underline{I} = 14.1 \angle -45^\circ \Rightarrow v_C = 14.1 \cos(2000t - 45^\circ) \text{ V}$   
 $\underline{V}_1 = Z_1 \underline{I} = 10 \angle 90^\circ \Rightarrow v_1 = 10 \cos(2000t + 90^\circ) \text{ V}$   
 $\underline{V}_C + \underline{V}_1 = 10 - j10 + j10 = 10 \angle 0^\circ = \underline{V}$

6.32   $X = -\frac{1}{\omega C}$  since  $|V_x|$  decreases as  $\omega$  increases  
 $\frac{V_R}{V} = \frac{50}{(50 - \frac{j}{200C})} \cdot \left| \frac{V_R}{V} \right|^2 = \frac{50^2}{50^2 + (\frac{1}{200C})^2} = \frac{1}{4}$   
 $\Rightarrow 2500 + \frac{1}{4 \cdot 10^4 C^2} = 2500 \times 4 \Rightarrow C = 57.7 \mu\text{F}$


6.36   $R_1 = 1.5 \text{ k}\Omega$ ,  $R_2 = 1 \text{ k}\Omega$ ,  $R_L = 2 \text{ k}\Omega$   
(a) Let  $Z_{in} = 1500 + \frac{10^8}{j\omega} \parallel 1000 = 1500 + \frac{10^8/j\omega}{10^3 + 10^8/j\omega} = \frac{2.5 \times 10^8 + j\omega \cdot 1500}{10^5 + j\omega}$   
 $\underline{I}_{in} = \frac{V_{in}}{Z_{in}}$ ,  $\frac{I_b}{\underline{I}_{in}} = \frac{10^8/j\omega}{10^3 + 10^8/j\omega} = \frac{10^5}{j\omega + 10^5}$   
 $\frac{I_c}{V_{in}} = 100 \frac{I_b}{V_{in}} = 100 \frac{I_b}{Z_{in} \underline{I}_{in}} = 100 \left( \frac{I_b}{\underline{I}_{in}} \right) / Z_{in} = \frac{0.04}{1 + j \cdot 6 \cdot 10^{-6} \omega}$   
 $\frac{V_{out}}{V_{in}} = [2000 + jX(\omega)] (-I_c) / V_{in} = \frac{-0.04 \cdot 2000 [1 + jX(\omega)/2000]}{1 + j \cdot 6 \cdot 10^{-6} \omega} = \frac{-80 [1 + j \cdot 5 \cdot 10^{-4} X(\omega)]}{1 + j \cdot 6 \cdot 10^{-6} \omega}$

(b) want  $\frac{V_{out}}{V_{in}} = -K \Rightarrow 1 + j5 \cdot 10^{-4} X(\omega) = 1 + j6 \cdot 10^{-6} \omega$

$X(\omega) = 0.012 \omega$  so  $X(\omega) = \omega L$ ,  $L = 12 \text{ mH}$

(p.s.,  $\frac{V_{out}}{V_{in}}$  should be  $-K$ )

6.41

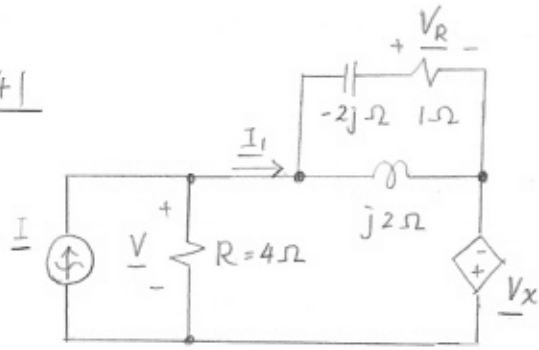

take  $V_R = 1 \Rightarrow I_R = 1$ ,  $V_X = 1$


$I_1 = I_R + \frac{-j2+1}{j2} \cdot I_R = -j0.5$

$V = (-j2+1)I_R - V_X = -j2$

$I = I_1 + \frac{V}{R} = -j$

$\frac{V_R}{V} = 0.5 \angle 90^\circ$ ,  $\frac{V}{I} = 2 \angle 0^\circ$

6.44

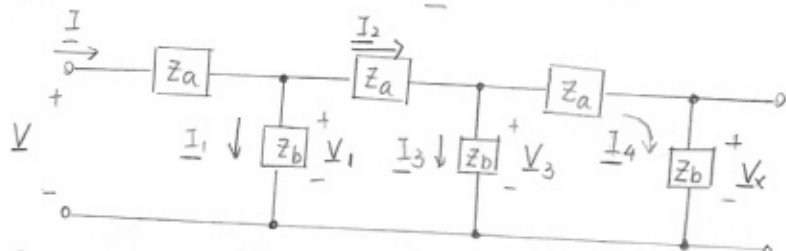

$V_x = R \cdot I = R$ ,  $V_3 = R + jX$ ,  $I_3 = \frac{V_3}{R} = 1 + j\frac{X}{R}$ ,  $I_2 = I_3 + I_4 = 2 + j\frac{X}{R}$

$V_1 = jX I_2 + V_3 = R - \frac{X^2}{R} + j3X$ ,  $I_1 = \frac{V_1}{R} = 1 - \frac{X^2}{R^2} + j\frac{3X}{R}$




$I = I_1 + I_2 = 3 - \frac{X^2}{R^2} + j\frac{4X}{R}$ ,  $V = jX I + V_1 = R - \frac{5X^2}{R} + j(6X - \frac{X^3}{R^2})$

$\angle V_x = 0$ ,  $\angle(\frac{V_x}{V}) = -\angle V = -180^\circ \Rightarrow \angle V = 180^\circ \therefore \text{Im}[V] = 0$

$\Rightarrow 6X - \frac{X^3}{R^2} = 0 \Rightarrow \sqrt[3]{(WCR)^2} = 6 \Rightarrow W_{osc} = \sqrt[3]{6RC}$

$\frac{V}{I} = R - \frac{5}{(WC)^2 R} = R - 30R = -29R \Rightarrow \frac{V_x}{V} = -\frac{1}{29}$

6.47

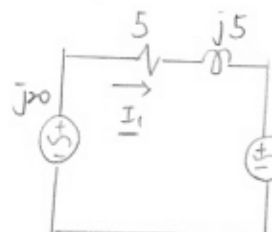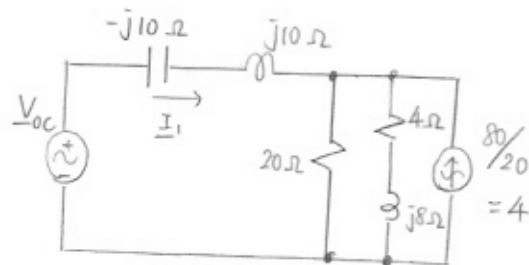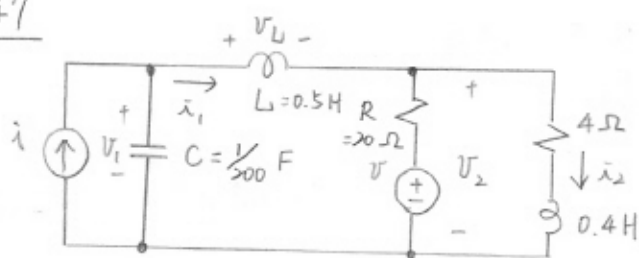

$V_{oc} = (-j10) \cdot 2 \angle 180^\circ = j20$ ,  $20 \parallel (4 + j8) = 5 + j5$

$I_1 = \frac{j20 - (20 + j20)}{5 + j5} = 2.83 \angle 135^\circ$

$i_1 = 2.83 \cos(20t + 135^\circ) \text{ A}$

$4(5 + j5) = 20 + j20$

$$6.51 \quad YV = \underline{I}_s, \quad Y = \frac{1}{4} - \frac{j}{2} + \frac{1}{(1-j2)} = \frac{(9-j2)}{20}$$

$$\underline{I}_s = 1 - \frac{V_x}{j2} - \frac{V_x}{(1-j2)} = \frac{20+8V-j4V}{20} = \frac{1}{20}(20) + \frac{1}{20}(8-j4)V$$

$$\Rightarrow \frac{1}{20}[9-j2-(8-j4)]V = \frac{1}{20}(20) \Rightarrow V = \frac{20}{1-j2} = 4-j8 = 8.94 \angle -63.4^\circ$$

$$\underline{I}_1 = 1 - \frac{V}{4} = j2 = 2 \angle 90^\circ$$

$$6.53 \quad [Y] = \begin{bmatrix} \frac{j}{10} - \frac{j}{5} & \frac{j}{5} \\ \frac{j}{5} & -\frac{j}{5} + \frac{1}{20} + \frac{1}{4+j8} \end{bmatrix} = \frac{1}{20} \begin{bmatrix} -j2 & j4 \\ j4 & 2-j6 \end{bmatrix}$$

$$[\underline{I}_s] = \begin{bmatrix} 4 \\ \frac{40}{20} \end{bmatrix} = \frac{1}{20} \begin{bmatrix} 80 \\ 40 \end{bmatrix}$$

$$\begin{bmatrix} -j2 & j4 \\ j4 & 2-j6 \end{bmatrix} \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix} = \begin{bmatrix} 80 \\ 40 \end{bmatrix} \Rightarrow V_1 = 116.6 \angle -30.9^\circ, \quad V_2 = 70.7 \angle -45^\circ$$

$$6.57 \quad Z\underline{I} = \underline{V}_s, \quad Z = 2 + j2 \parallel (-j2+1) = 6+j2$$

$$\underline{V}_s = 2 \times 6 + V_x = 12 + 4\underline{I}_1$$

$$(6+j2-4)\underline{I}_1 = 12 \Rightarrow \underline{I}_1 = 3-j3 = 4.24 \angle -45^\circ$$

$$\underline{V} = 2(6-\underline{I}_1) = 6+j6 = 8.49 \angle 45^\circ$$

$$6.59 \quad [Z] = \begin{bmatrix} -8j+8j+2 & -2 \\ -2 & 2+4+j4 \end{bmatrix} = \begin{bmatrix} 2 & -2 \\ -2 & 6+j4 \end{bmatrix}$$

$$[\underline{V}_s] = \begin{bmatrix} -8j \cdot 2 - (-10) \\ -10 \end{bmatrix} = \begin{bmatrix} 10-j16 \\ -10 \end{bmatrix}$$

$$\begin{bmatrix} 2 & -2 \\ -2 & 6+j4 \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix} = \begin{bmatrix} 10-j16 \\ -10 \end{bmatrix}$$

$$\underline{I}_1 = 10.44 \angle -73.3^\circ, \quad \underline{I}_2 = 2.83 \angle -135^\circ$$