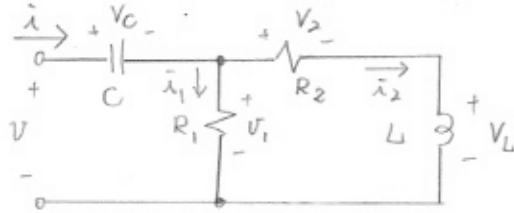


7.4



$$Z = -j5 + 20 \parallel (4 + j8) = 5 \text{ k}\Omega, |Z| = 5 \text{ k}\Omega$$

$$|I| = \frac{40}{5} = 8 \text{ mA}$$

$$I_{\text{rms}} = \frac{8}{\sqrt{2}} = 4\sqrt{2} \text{ mA}, P = \frac{1}{2} \cdot 5 \cdot 8^2 = 160 \text{ mW}$$

$$|I_1|^2 = \left| \frac{4+j8}{24+j8} \right|^2 \cdot 8^2 = 8, |I_2|^2 = \left| \frac{20}{24+j8} \right|^2 \cdot 8^2 = 40$$


$$\frac{1}{2} R_1 |I_1|^2 + \frac{1}{2} R_2 |I_2|^2 = 160 \text{ mW} = P$$

7.7


$$Z(j\omega) = 50 + j(\omega - 10^4/\omega)$$

$$P = 50 \cdot \frac{20^2}{2|Z|^2} = \frac{10^4}{[2500 + (\omega - 10^4/\omega)^2]}$$

ω	$P(\omega)$
0+	0
50	0.4
100	4
200	0.4
∞	0

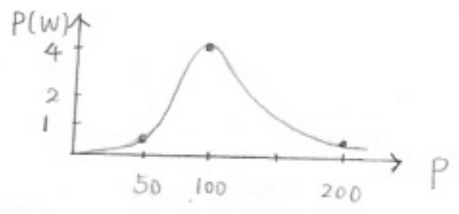


7.12

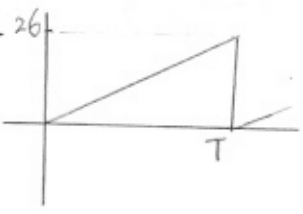

$$i = \frac{26t}{T} \text{ for } 0 \leq t \leq T, \int_0^T i^2 dt = \frac{26^2}{T^2} \int_0^T t^2 dt = \frac{26^2 T^3}{3T^2} = 225 T$$

$$I_{\text{rms}} = \left(\frac{225 T}{T} \right)^{1/2} = 15 \text{ A}$$

7.16

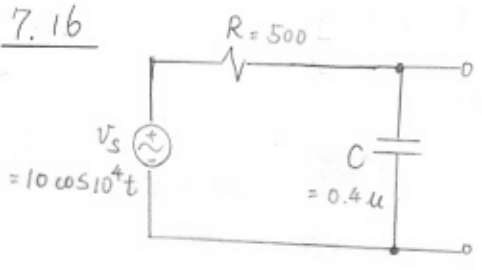

$$Z_S = 500 \parallel (-j250) = 100 - j200, Z = Z_S^* = 100 + j200$$

$$V_{\text{rms}}^2 = \left| \frac{-j250}{500 - j250} \right|^2 \cdot 10^2 = 10$$

$$P_{\text{max}} = \frac{V_{\text{rms}}^2}{(4 \cdot 100)} = 25 \text{ mW}$$

7.19

(a) $Z = Z_S^* = 24 + j7 \text{ k}\Omega, P = P_{\text{max}} = \frac{2.4^2}{4 \cdot 24} = 60 \text{ mW}, \text{Eff.} = 50\%$

(b) $Z = (4 + j3)C, |Z| = |Z_S| \Rightarrow 5C = 25, C = 5, Z = 20 + j15 \text{ k}\Omega$

$$P = \frac{20 \cdot 2.4^2}{(24+20)^2 + (7+15)^2} = 47.6 \text{ mW}, \text{Eff.} = \frac{20}{24+20} = 45\%$$

7.22

Z increases with $\omega \Rightarrow Z = \omega L$

$$Q = (\frac{|V|^2 |I|^2}{P} - P^2)^{1/2} = 960 \text{ VAR}$$

(a) $R = \frac{|V|^2}{P} = 20 \Omega, L = \frac{|V|^2}{\omega Q} = 39.8 \text{ mH}$

(b) $R = \frac{P}{|I|^2} = 7.2 \Omega, L = \frac{Q}{\omega |I|^2} = 25.5 \text{ mH}$

7.26 (a) $|Z_M| = 6 \Omega$, $|I| = \frac{240}{6} = 40 \text{ A}$, $\text{pf} = \frac{3.6}{6} = 0.6$ lagging

$P = 40^2 \cdot 3.6 = 5760 \text{ W}$, $Q = 40^2 \cdot 4.8 = 7680 \text{ W}$

(b) $C = \frac{7680}{\omega |V|^2} = 354 \mu\text{F}$, $P = 5760 \text{ W}$

$|I| = \frac{5760}{240} = 24 \text{ A}$

(c) $j4.8 - j/\omega C = 0 \Rightarrow C = 553 \mu\text{F}$, $|I| = \frac{240}{3.6} = 66.7 \text{ A}$

$P = 240 \cdot 66.7 = 16000 \text{ W}$, $|V_M| = |Z_M| |I| = 400 \text{ V}$

Series resonant circuit.

7.31 (a) $|S_1| = 2000 \cdot 40 = 80000 \text{ VA}$, $|S_2| = 2000 \cdot 15 = 30000 \text{ VA}$

$P_1 = 80000 \cdot 0.5 = 40000 \text{ W}$, $P_2 = 30000 \cdot 0.8 = 24000 \text{ W}$

$Q_1 = (80000^2 - 40000^2)^{1/2} = 69.3 \text{ kVAR}$, $Q_2 = -(30000^2 - 24000^2)^{1/2} = -18 \text{ kVAR}$

$P = P_1 + P_2 = 64000 \text{ W}$, $Q = Q_1 + Q_2 = 51.3 \text{ kVAR}$

$S = (P^2 + Q^2)^{1/2} = 82000 \text{ kVA}$, $|I| = \frac{|S|}{|V|} = 41 \text{ A}$

$\text{pf} = P/|S| = 0.78$ lagging

(b) $|S| = \frac{64000}{0.95} = 67.4 \text{ kVA} \Rightarrow |I| = \frac{|S|}{|V|} = 33.7 \text{ A}$


$Q_c + 51.3 \text{ k} = |S| (1 - 0.95^2)^{1/2} \Rightarrow Q_c = -30.3 \text{ kVAR}$

7.34 $|S_{\text{blower}}| = \frac{50}{0.707} = 70.7 \text{ kVA}$, $Q = 70.7 \cdot (1 - 0.707^2)^{1/2} = 50 \text{ kVAR}$

$|S| = 1300 \cdot 100 = 130 \text{ kVA}$

$P_{\text{heater}} = (130^2 - 50^2)^{1/2} - 50 = 70 \text{ kW}$

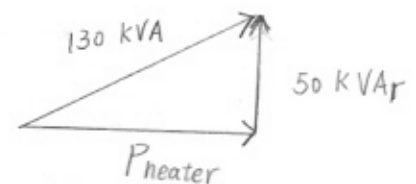$R_{\text{heater}} = \frac{1300^2}{70000} = 24.1 \Omega$



7.40 $|V I_1|^2 = |S_1|^2 = P^2 + Q^2$, $|V I_2|^2 = |S_2|^2 = P^2 + (Q + Q_c)^2$, $Q_c = -\omega C |V|^2$

$|V I_1|^2 - |V I_2|^2 = Q^2 - (Q + Q_c)^2 = -2Q Q_c - Q_c^2$

$\Rightarrow |V|^2 (|I_1|^2 - |I_2|^2) = 2Q \omega C |V|^2 - (\omega C |V|^2)^2$

$\Rightarrow Q = \frac{1}{2} [\omega C |V|^2 + (|I_1|^2 - |I_2|^2) / \omega C]$,

$P = (|V|^2 |I_1|^2 - Q^2)^{1/2}$