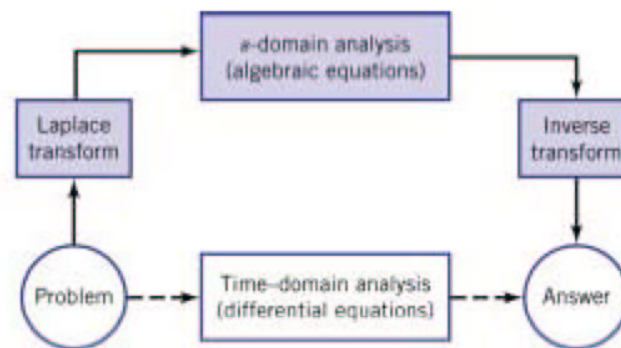


Chapter 13 Laplace Transform Analysis

Chapter 13: Outline

Circuit Complete Response Analysis Using

Laplace Transform



Laplace Transform and Transform Inversion

Transform Circuit Analysis

Zero-state response (Natural response and Forced response)

Zero-input response (initial state \rightarrow independent source)

$$\text{Complete response} = \text{Z.S.R.} + \text{Z.I.R.}$$

Laplace transforms

Laplace Transform

- s -domain phasor analysis:

$$x(t) = X_m e^{\sigma t} \cos(\omega t + \phi_x) \longrightarrow \underline{X} = X_m \angle \phi_x$$

- Laplace transform:


$$F(s) = \mathcal{L}[f(t)] \equiv \int_{0^-}^{\infty} f(t) e^{-st} dt$$
$$= \int_{0^+}^{\infty} f(t) e^{-st} dt \quad \text{if } |f(t)| < \infty, 0^- \leq t \leq 0^+$$

Laplace Transform (Three conditions)


- Unilateral (one-sided Laplace transform): Laplace transform holds for $t=0$. Previous effects are included in the initial conditions at $t=0^-$.
- Existence condition: $\lim_{t \rightarrow \infty} |f(t)|e^{-\mathbf{S}t} = 0, \mathbf{S} > \mathbf{S}_c$.
- The resulting transform is a function of s .

One-Sided Waveform

$$\text{unit step : } u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases} \Rightarrow f(t)u(t) = \begin{cases} 0, & t < 0 \\ f(t), & t > 0 \end{cases}$$
$$\Rightarrow L[f(t)u(t)] = L[f(t)], \text{ if } |f(t)| < \infty, 0^- \leq t \leq 0^+$$

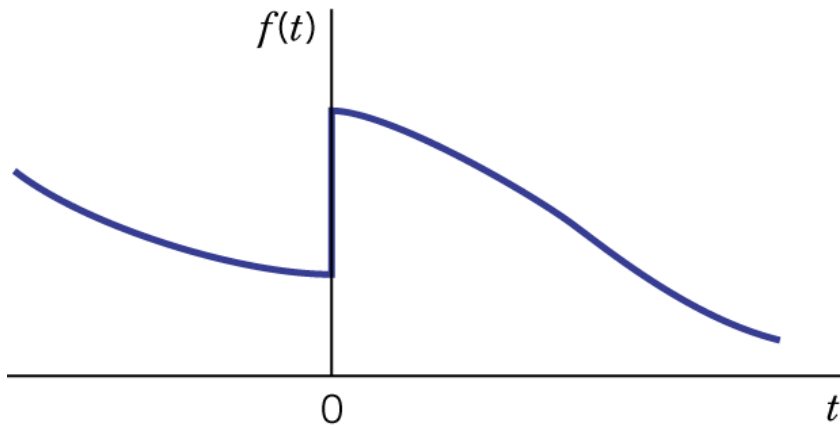

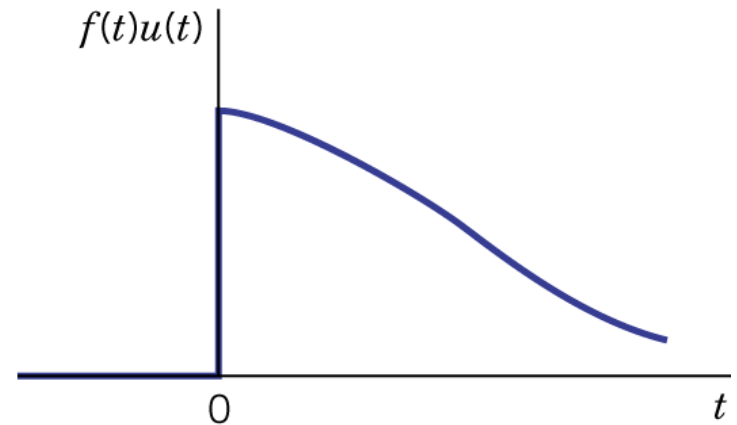(a) Waveform with discontinuity at $t = 0$



(b) One-sided waveform

Sufficient Existence Condition

$\int_{0^-}^{\infty} f(t)e^{-st} dt$ is finite

$$\int_{0^-}^{\infty} f(t)e^{-st} dt \leq \int_{0^-}^{\infty} |f(t)e^{-st}| dt = \int_{0^-}^{\infty} |f(t)| |e^{-st}| dt = \int_{0^-}^{\infty} |f(t)| e^{-st} dt$$

\Rightarrow The integral remains finite if $\lim_{t \rightarrow \infty} \int_{0^-}^{\infty} |f(t)| e^{-st} dt = 0, \mathbf{s} > \mathbf{s}_c$

$\Rightarrow f(t)$ is of exponential order

$\Rightarrow \mathbf{s}_c$: abscissa of convergence

Inverse Laplace Transform

- Inverse Laplace transform for $t=0$:

$$f(t) = \mathcal{L}^{-1}[F(s)] \equiv \frac{1}{2\pi j} \int_{c-j\infty}^{c+j\infty} F(s)e^{st} ds, c > \sigma_c$$

- Inverse Laplace transform is usually done by partial fraction expansion (will be covered in section 13.2).

Example 13.1

$$L[e^{-at}]$$


$$\lim_{t \rightarrow \infty} |f(t)| e^{-at} = \lim_{t \rightarrow \infty} e^{-(a+s)t} = 0, \text{ if } a + s > 0$$

$$L[e^{-at}] = \int_{0^-}^{\infty} e^{-at} e^{-st} dt = \int_{0^-}^{\infty} e^{-(a+s)t} dt = \frac{1}{s+a}, \text{ when } \mathbf{s}_c > -a$$

$$\text{if } a = 0, L[1] = L[u(t)] = \frac{1}{s}$$

(Note : a can be complex, $\text{Re}[a] + s > 0$)

Example 13.1

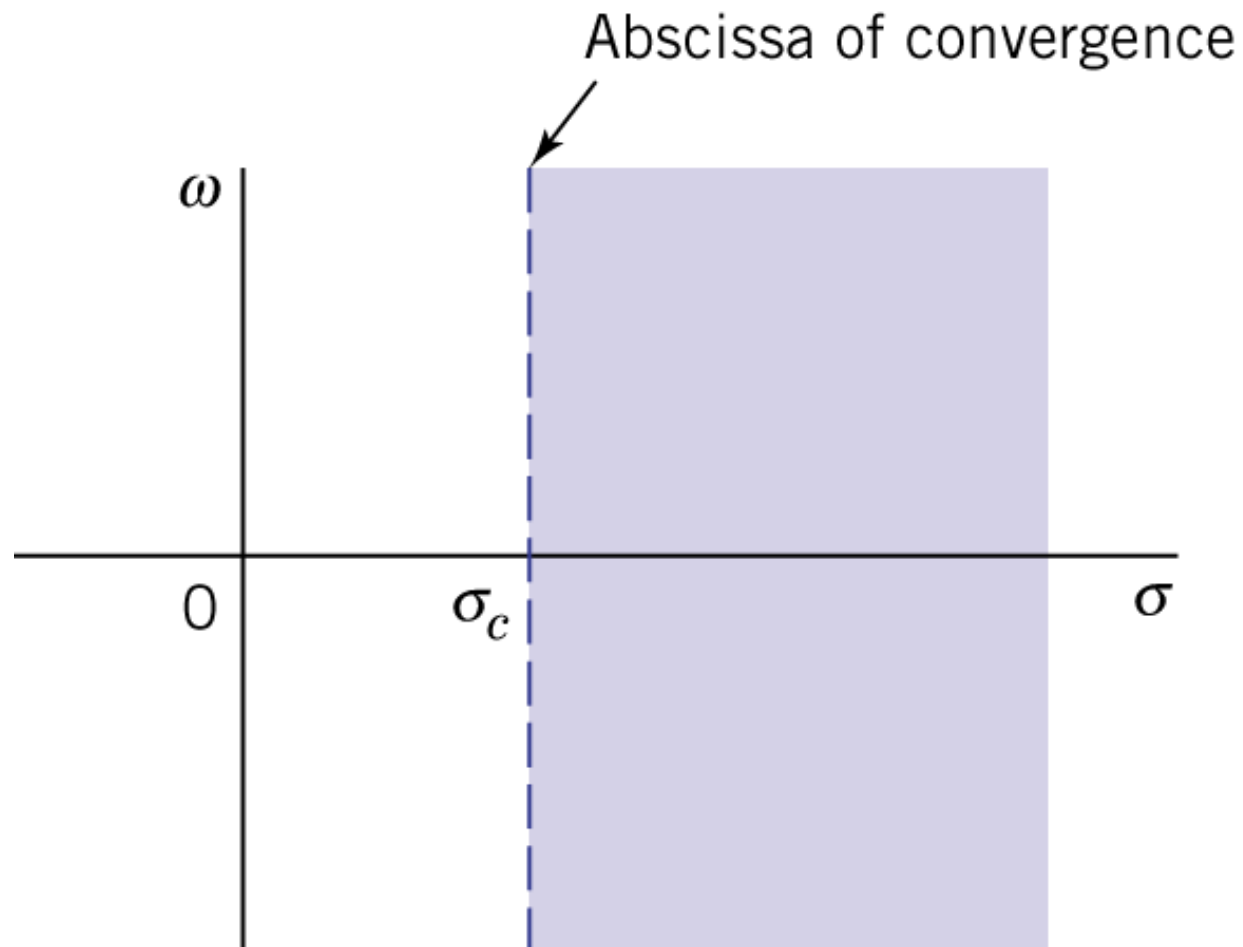

Example 13.2

$$\begin{aligned} L[\sin \mathbf{b}t] &= L\left[\frac{1}{j2} \left(e^{j\mathbf{b}t} - e^{-j\mathbf{b}t}\right)\right] \\ &= \frac{1}{j2} \left(\frac{1}{s - j\mathbf{b}} - \frac{1}{s + j\mathbf{b}} \right) = \frac{\mathbf{b}}{s^2 + \mathbf{b}^2} \\ \mathbf{s}_c &= 0 \end{aligned}$$

Transform Properties

- Linear combination:

$$L[f(t)] = F(s), \quad L[g(t)] = G(s)$$

$$L[Af(t) + Bg(t)] = AF(s) + BG(s)$$

$$L[Af(t)] = AF(s)$$

Transform Properties

- Multiplication by e^{-at} :

$$L[f(t)] = F(s)$$

$$L[e^{-at} f(t)] = F(s + a)$$

Transform Properties

– Multiplication by t :


$$\begin{aligned}\frac{d}{ds} F(s) &= \frac{d}{ds} \int_{0^-}^{\infty} f(t) e^{-st} dt \\ &= - \int_{0^-}^{\infty} t f(t) e^{-st} dt = -L[tf(t)]\end{aligned}$$

Transform Properties

- Time delay:

$$g(t) = f(t - t_0)u(t - t_0) = \begin{cases} 0, & t < t_0 \\ f(t - t_0), & t > t_0 \end{cases}$$

$$L[g(t)] = e^{-st_0} F(s)$$

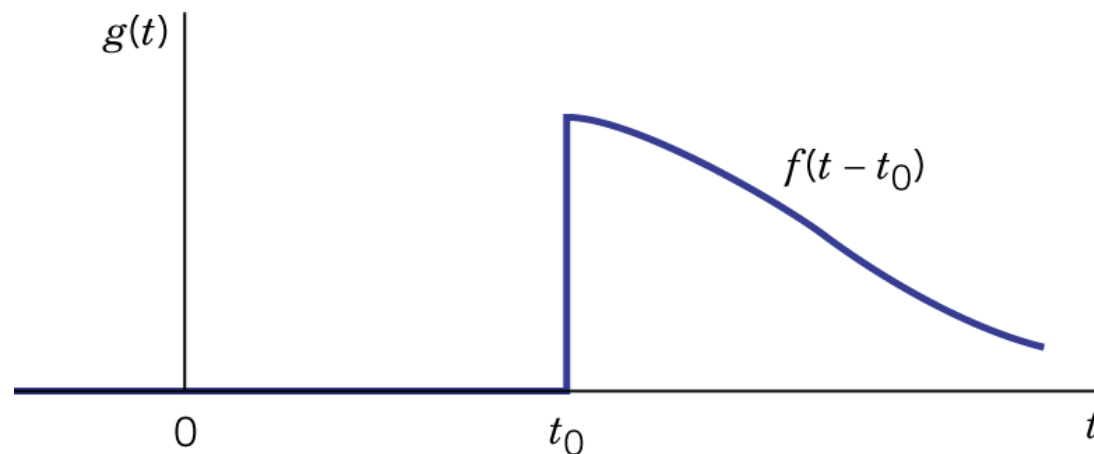

Transform Properties

– Differentiation:

$$L[f'(t)] = L\left[\frac{df(t)}{dt}\right] = sF(s) - f(0^-)$$

$$L[f''(t)] = s^2 F(s) - sf(0^-) - f'(0^-)$$

Transform Properties

- Integration:

$$g(t) = \int_{0^-}^t f(l) dl$$


$$dg(t) = f(t)dt, \quad g(0^-) = 0, \quad e^{-st} dt = d\left(\frac{e^{-st}}{-s}\right)$$

$$L[g(t)] = L\left[\int_{0^-}^t f(l) dl\right] = \frac{1}{s} F(s)$$

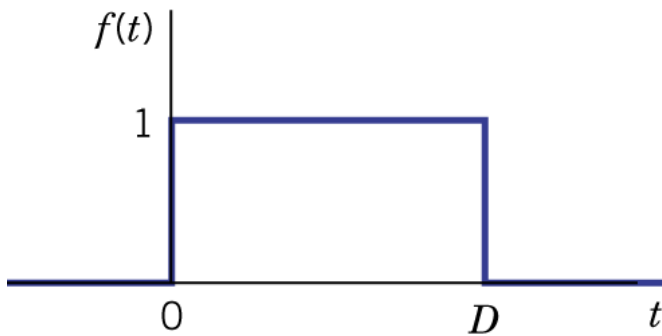
Example 13.3

$$f(t) = \begin{cases} 1, & 0 < t < D \\ 0, & \text{otherwise} \end{cases} = u(t) - u(t - D)$$

$$F(s) = \frac{1}{s} + (-1)e^{-sD} \frac{1}{s} = \frac{1 - e^{-sD}}{s}$$



(a) Rectangular pulse

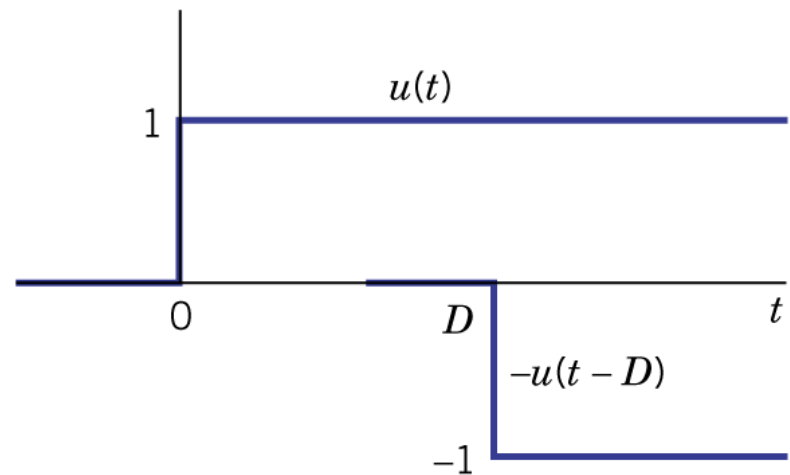

(b) Decomposition as two step functions

Example 13.4

$$f(t) = \sin bt \Rightarrow L[f(t)] = \frac{b}{s^2 + b^2}$$

$$L[f'(t)] = L[b \cos bt] = \frac{sb}{s^2 + b^2} - \sin(0^-) = \frac{sb}{s^2 + b^2}$$

$$L[\cos bt] = \frac{s}{s^2 + b^2}$$

$$L[\cos(bt + f)] = L[\cos f \cos bt - \sin f \sin bt] = \frac{s \cos f - b \sin f}{s^2 + b^2}$$

Table 13.1

TABLE 13.1 Laplace Transform Properties

| Operation | Time Function | Laplace Transform |
|-----------------------------|------------------------------------|-------------------------------|
| Linear combination | $Af(t) + Bg(t)$ | $AF(s) + BG(s)$ |
| Multiplication by e^{-at} | $e^{-at}f(t)$ | $F(s + a)$ |
| Multiplication by t | $tf(t)$ | $-dF(s)/ds$ |
| Time delay | $f(t - t_0)u(t - t_0)$ | $e^{-st_0}F(s)$ |
| Differentiation | $f'(t)$ | $sF(s) - f(0^-)$ |
| | $f''(t)$ | $s^2F(s) - sf(0^-) - f'(0^-)$ |
| Integration | $\int_{0^-}^t f(\lambda) d\lambda$ | $\frac{1}{s} F(s)$ |

Table 13.2


TABLE 13.2 Laplace Transform Pairs

| $f(t)$ | $F(s)$ |
|--------------------------------|---|
| A | $\frac{A}{s}$ |
| $u(t) - u(t - D)$ | $\frac{1 - e^{-sD}}{s}$ |
| t | $\frac{1}{s^2}$ |
| t^r | $\frac{r!}{s^{r+1}}$ |
| e^{-at} | $\frac{1}{s + a}$ |
| te^{-at} | $\frac{1}{(s + a)^2}$ |
| $t^r e^{-at}$ | $\frac{r!}{(s + a)^{r+1}}$ |
| $\sin \beta t$ | $\frac{\beta}{s^2 + \beta^2}$ |
| $\cos(\beta t + \phi)$ | $\frac{s \cos \phi - \beta \sin \phi}{s^2 + \beta^2}$ |
| $e^{-at} \cos(\beta t + \phi)$ | $\frac{(s + a) \cos \phi - \beta \sin \phi}{(s + a)^2 + \beta^2}$ |

Solving Differential Equations

- The transformation automatically incorporates the initial conditions (zero-input response).
- Transformation converts linear differential equations to s -domain algebraic equations.
- Transformation is **similar** to the s -domain phasor analysis. Denominator of the s -domain function includes the characteristic polynomial.
- Inverse transformation is required to obtain the resultant time domain function.

First-Order Example

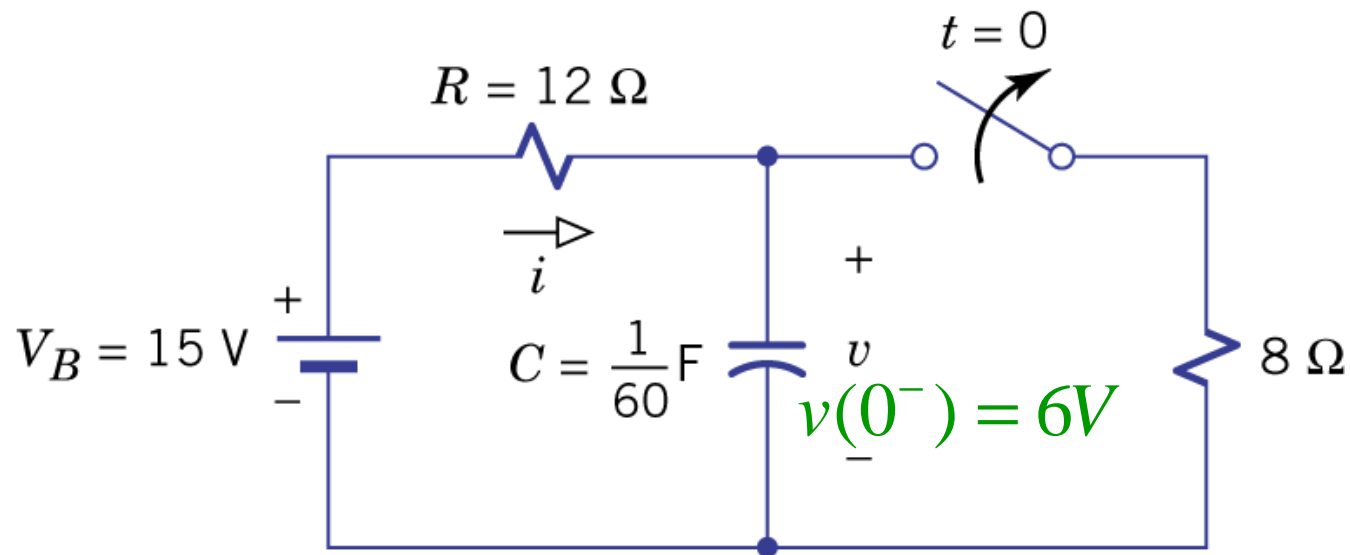


$$0.2v'(t) + v(t) = 15$$

$$0.2[sV(s) - v(0^-)] + V(s) = \frac{15}{s}$$

$$V(s) = \frac{6s + 75}{s(s + 5)} = \frac{6}{s + 5} + \frac{75}{s(s + 5)}$$

$$\begin{aligned} v(t) &= L^{-1}[V(s)] = L^{-1}\left[\frac{6}{s + 5}\right] + L^{-1}\left[\frac{75}{s(s + 5)}\right] \\ &= 6e^{-5t} + 75(-0.2)(e^{-5t} - 1) = 15 - 9e^{-5t}, t \geq 0 \end{aligned}$$

Second-Order Example

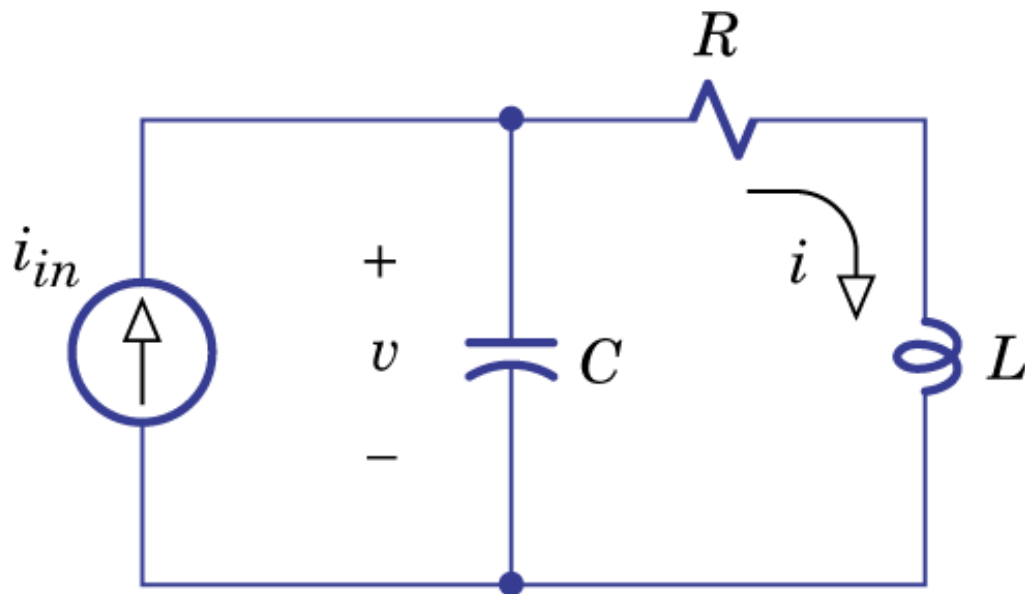

$$i_{in} = \begin{cases} I_1, & t < 0 \\ I_2, & t > 0 \end{cases}$$

$$i(0^-) = I_1, v(0^-) = RI_1$$

Second Order Example (Cont.)

$t > 0$

$$\begin{cases} Li'(t) + Ri(t) = v(t) \\ Cv'(t) + I(t) = I_2 \end{cases} \Rightarrow \begin{cases} L[sI(s) - I_1] + RI(s) = V(s) \\ C[sV(s) - RI_1] + I(s) = I_2 / s \end{cases}$$

$$I(s) = \frac{I_1 s^2 + (R/L)I_1 s + I_2 / LC}{s[s^2 + (R/L)s + 1/LC]}$$

if $I_2 = I_1$ (no switching)

$$I(s) = \frac{I_1}{s} \Rightarrow i(t) = I_1, \text{ for } t \geq 0$$

Characteristic polynomial



Transform Inversion

Partial-Fraction Expansion

- Partial-fraction expansion of a strictly proper rational function:

$$F(s) = \frac{N(s)}{D(s)} = \frac{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0}{s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}, m \leq n-1$$

- Three cases will be considered: distinct real poles, complex poles and repeated poles.

Case 1: Distinct Real Poles

- (Heaviside's theorem, cover-up rule.)

$$F(s) = \frac{N(s)}{D(s)} = \frac{A_1}{s - s_1} + \frac{A_2}{s - s_2} + \cdots + \frac{A_n}{s - s_n}$$

$$f(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + \cdots + A_n e^{s_n t}, \quad t \geq 0$$

$$A_i = (s - s_i) F(s) \Big|_{s=s_i}, \quad i = 1, 2, \dots$$

Example 13.5: Inversion of a Third-Order Function (Heaviside's theorem)

$$I(s) = \frac{I_1 s^2 + (R/L)I_1 s + I_2 / LC}{s[s^2 + (R/L)s + 1/LC]} \quad \left(\begin{array}{l} R = 12\Omega, L = 1H, C = \frac{1}{20}F \\ I_1 = -2A, I_2 = 2A \end{array} \right)$$

$$I(s) = \frac{-2s^2 - 24s + 40}{s(s+2)(s+10)} = \frac{A_1}{s} + \frac{A_2}{s+2} + \frac{A_3}{s+10}$$

$$A_1 = sI(s)|_{s=0} = 2$$

$$A_2 = (s+2)I(s)|_{s=-2} = -5$$

$$A_3 = (s+10)I(s)|_{s=-10} = 1$$

$$I(s) = \frac{2}{s} + \frac{-5}{s+2} + \frac{1}{s+10} \Rightarrow i(t) = 2 - 5e^{-2t} + e^{-10t}, t \geq 0$$

Example 13.5: (Method of Undetermined Coefficients)

$$I(s) = \frac{-2s^2 - 24s + 40}{s(s+2)(s+10)} = \frac{2}{s} - \frac{5}{s+2} + \frac{A_3}{s+10}$$

$$I(s) \Big|_{s=1} = \frac{14}{33} = 2 - \frac{5}{3} + \frac{A_3}{11} = \frac{11+3A_3}{33}$$

$$\Rightarrow A_3 = 1$$

Case 2: Complex Poles

$$D(s) = (s^2 + 2\alpha s + \omega_0^2)(s - s_3) \cdots (s - s_n)$$

$$\text{if } \mathbf{a}^2 < \mathbf{w}_0^2, \quad s_1, s_2 = -\mathbf{a} \pm j\mathbf{b} = -\mathbf{a} \pm j\sqrt{\mathbf{w}_0^2 - \mathbf{a}^2}$$

$$F(s) = G(s) + \sum_{i=3}^n \frac{A_i}{s - s_i}$$

$$G(s) = \frac{\frac{1}{2}K}{s + \mathbf{a} - j\mathbf{b}} + \frac{\frac{1}{2}K^*}{s + \mathbf{a} + j\mathbf{b}}$$

$$K = 2(s + \mathbf{a} - j\mathbf{b})F(s) \Big|_{s=-\mathbf{a}+j\mathbf{b}} = K_m e^{j\mathbf{f}}$$

$$g(t) = \frac{1}{2}K e^{-(\mathbf{a}-j\mathbf{b})t} + \frac{1}{2}K^* e^{-(\mathbf{a}+j\mathbf{b})t} = K_m e^{-\mathbf{a}t} \cos(\mathbf{b}t + \mathbf{f})$$

Case 2: Complex Poles (Cont.)

Or,...

$$g(t) = K_m e^{-at} \cos(bt + f) \quad \text{Undetermined coefficients}$$

$$L[g(t)] = \frac{(s + a)K_m \cos f - bK_m \sin f}{(s + a)^2 + b^2}$$

$$G(s) = \frac{\underbrace{Bs + C}}{s^2 + 2as + w_0^2} = \frac{(s + a)B - (aB - C)}{(s + a)^2 + w_0^2 - a^2}$$

\Rightarrow Find a , b , w_0^2 , B and C , compare coefficients, then determine K .

$$\Rightarrow B + j(aB - C)/b = K_m \cos f + jK_m \sin f = K$$

Example 13.6: Inversion with Complex Poles

$$F(s) = \frac{15s^2 - 16s - 7}{(s+2)(s^2 + 6s + 25)} \Rightarrow s_1 = -2, \quad s_2, s_3 = -3 \pm j4 = -\mathbf{a} \pm \mathbf{j}b$$

$$F(s) = \frac{A_1}{s+2} + G(s)$$

$$G(s) = \frac{\frac{1}{2}K}{s+3-j4} + \frac{\frac{1}{2}K^*}{s+3+j4} = \frac{Bs+C}{s^2+6s+25}$$

$$A_1 = (s+2)F(s)\Big|_{s=-2} = 5$$

$$K = 2 \frac{15s^2 - 16s - 7}{(s+2)(s^2 + 6s + 25)} \Big|_{s=-3+j4}$$

Example 13.6: (Cont., method of undetermined coefficients)

$$F(s) = \frac{15s^2 - 16s - 7}{(s+2)(s^2 + 6s + 25)} = \frac{5}{s+2} + \frac{Bs + C}{s^2 + 6s + 25}$$

$$\Rightarrow sF(s) = \frac{15s^3 + \dots}{s^3 + \dots} = \frac{5s}{s+2} + \frac{Bs^2 + Cs}{s^2 + 6s + 25}$$

$$s \rightarrow \infty, 15 = 5 + B \Rightarrow B = 10$$

$$F(s) = \frac{15s^2 - 16s - 7}{(s+2)(s^2 + 6s + 25)} = \frac{5}{s+2} + \frac{10s + C}{s^2 + 6s + 25}$$

$$F(0) = \frac{-7}{2 \cdot 25} = \frac{5}{2} + \frac{C}{25} \Rightarrow C = -66$$

$$g(t) = K_m e^{-at} \cos(bt + f)$$

$$K = B + j \frac{aB - C}{b} = 10 + j24 = 26 \angle 67.4^\circ$$

$$f(t) = 5e^{-2t} + g(t) = 5e^{-2t} + 26e^{-3t} \cos(4t + 67.4^\circ), \quad t \geq 0$$

Case 3: Repeated Poles

$$F(s) = G(s) + \frac{A_3}{s - s_3} + \dots + \frac{A_n}{s - s_n}$$

$$G(s) = \frac{A_{i1}}{s - s_i} + \frac{A_{i2}}{(s - s_i)^2} \quad (\text{double poles})$$

$$g(t) = A_{i1}e^{s_i t} + A_{i2}te^{s_i t}$$

$$(s - s_i)^2 F(s) = (s - s_i)A_{i1} + A_{i2} + (s - s_i)^2 \sum_{j=3}^n \frac{A_j}{s - s_j}$$

$$\Rightarrow A_{i2} = (s - s_i)^2 F(s) \Big|_{s=s_i}$$

$$A_{i1} = \frac{d}{ds} \left[(s - s_i)^2 F(s) \right] \Big|_{s=s_i}$$

Case 3: Repeated Poles (Cont.)

$$G(s) = \frac{A_{i1}}{s - s_i} + \frac{A_{i2}}{(s - s_i)^2} + \frac{A_{i3}}{(s - s_i)^3}$$

$$g(t) = A_{i1}e^{s_i t} + A_{i2}te^{s_i t} + \frac{1}{2}A_{i3}t^2e^{s_i t}$$

$$\Rightarrow A_{i3} = \left[(s - s_i)^3 F(s) \right]_{s=s_i}$$

$$A_{i2} = \frac{d}{ds} \left[(s - s_i)^3 F(s) \right]_{s=s_i}$$

$$A_{i1} = \frac{1}{2!} \frac{d^2}{ds^2} \left[(s - s_i)^3 F(s) \right]_{s=s_i}$$

Example 13.7: Inversion with a Triple Pole

$$F(s) = \frac{-s^2 - 2s + 14}{(s+4)^3(s+5)} = \frac{A_{11}}{s+4} + \frac{A_{12}}{(s+4)^2} + \frac{A_{13}}{(s+4)^3} + \frac{A_4}{s+5}$$

$$A_4 = (s+5)F(s)|_{s=-5} = 1, \quad A_{13} = (s+4)^3 F(s)|_{s=-4} = 6$$

$$F(s) = \frac{-s^2 - 2s + 14}{(s+4)^3(s+5)} = \frac{A_{11}}{s+4} + \frac{A_{12}}{(s+4)^2} + \frac{6}{(s+4)^3} + \frac{1}{s+5}$$

$$\lim_{s \rightarrow \infty} sF(s) = 0 \Rightarrow A_{11} = -1$$

$$F(0) = \frac{14}{320} = -\frac{1}{4} + \frac{A_{12}}{16} + \frac{6}{64} + \frac{1}{5} \Rightarrow A_{12} = 0$$

$$F(s) = -\frac{1}{s+4} + \frac{0}{(s+4)^2} + \frac{6}{(s+4)^3} + \frac{1}{s+5}$$

$$f(t) = -e^{-4t} + \frac{6}{2}t^2 e^{-4t} + e^{-5t}, \quad t \geq 0$$

Time Delay

Initial-Value Theorem

Final-Value Theorem

Time Delay

$$L[g(t-t_0)u(t-t_0)] = L[g(t)]e^{-st_0}$$

$$F(s) = \frac{N_1(s) + N_2(s)e^{-st_0}}{D(s)} = F_1(s) + F_2(s)e^{-st_0}$$

$$f(t) = f_1(t) + f_2(t-t_0)u(t-t_0), \quad t \geq 0$$

Example 13.8: Inversion with Time Delay

$$\text{excitation : } x(t) = 20u(t) - 40u(t - 3)$$

$$y'(t) - 5y(t) = -x(t) = -20u(t) + 40u(t - 3), \quad y(0^-) = 0$$

$$sY(s) - 5Y(s) = \frac{-20 + 40e^{-3s}}{s}$$

$$Y(s) = \frac{-20 + 40e^{-3s}}{s(s-5)} = F_1(s) - 2F_1(s)e^{-3s}$$

$$F_1(s) = \frac{-20}{s(s-5)} = \frac{4}{s} + \frac{-4}{s-5}$$

$$f_1(t) = 4 - 4e^{5t}$$


$$y(t) = f_1(t) - 2f_1(t-3)u(t-3) = 4 - 4e^{5t} - [8 - 8e^{5(t-3)}]u(t-3), \quad t \geq 0$$

Initial-Value Theorem


$$f(0^+) = \lim_{s \rightarrow \infty} sF(s)$$

($F(s)$ is strictly proper)

Initial-Value Theorem (Cont.)

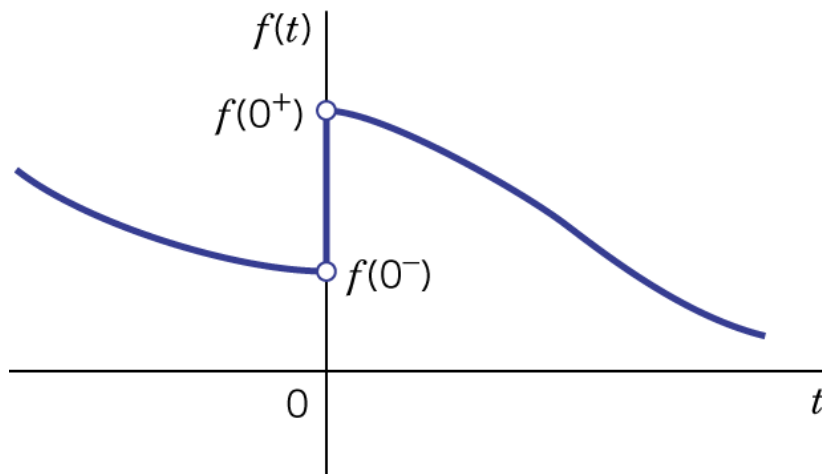

(a) Waveform with jump at $t = 0$

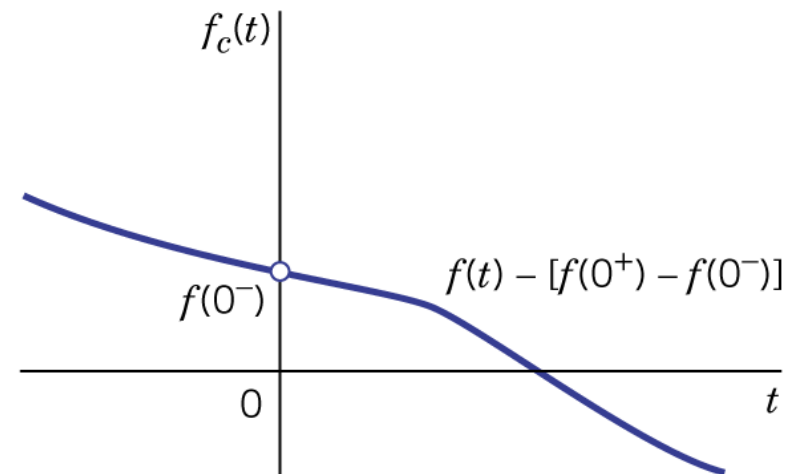

(b) Continuous waveform

$$f_c(t) = f(t) - [f(0^+) - f(0^-)]u(t)$$

$$\left(\text{i.e., } f_c(t) - f(0^-) = f(t) - f(0^+), t > 0\right)$$

Initial-Value Theorem (Cont.)

$$F_c(s) = F(s) - [f(0^+) - f(0^-)]/s$$

$$L[f'_c(t)] = sF_c(s) - f_c(0^-) = \int_{0^-}^{\infty} f'_c(t)e^{-st} dt$$

$$\lim_{s \rightarrow \infty} \int_{0^-}^{\infty} f'_c(t)e^{-st} dt = 0 = \lim_{s \rightarrow \infty} sF_c(s) - f_c(0^-)$$

($|f'_c(t)|$ is finite over $0^- \leq t \leq 0^+$)

$$\Rightarrow sF(s) - [f(0^+) - f(0^-)] - f(0^-) = 0$$

$$\lim_{s \rightarrow \infty} sF(s) - f(0^+) = 0$$

Initial Slope

Find initial slope $f'(0^+)$ assuming $f(0^-)$ is known

$$L[f'(t)] = sF(s) - f(0^-) = \frac{sN(s)}{D(s)} - f(0^-)$$

$$f'(0^+) = \lim_{s \rightarrow \infty} s \frac{sN(s) - f(0^-)D(s)}{D(s)}$$

Final-Value Theorem

$$f(\infty) = \lim_{s \rightarrow 0} sF(s)$$

(
no poles in the RHP,
no multiple poles at the origin,
no poles on the imaginary axis
)

$$L[f'(t)] = sF(s) - f(0^-) = \int_{0^-}^{\infty} f'(t)e^{-st} dt$$

$$\lim_{s \rightarrow 0} sF(s) - f(0^-) = \int_{0^-}^{\infty} f'(t) dt = f(\infty) - f(0^-)$$

Example 13.9: Calculating Initial and Final Values

$$f(0^-) = 5$$

$$F(s) = \frac{N(s)}{D(s)} = \frac{5s^3 - 1600}{s(s^3 + 18s^2 + 90s + 800)} \quad (\text{strictly proper})$$

$$f(0^+) = \lim_{s \rightarrow \infty} sF(s) = 5 = f(0^-)$$

$$f'(0^+) : \frac{sN(s) - f(0^-)D(s)}{D(s)} = \frac{-90s^3 - 450s^2 - 5600s}{s(s^3 + 18s^2 + 90s + 800)} \quad (\text{strictly proper})$$

$$f'(0^+) = \lim_{s \rightarrow \infty} s \frac{-90s^3 - \dots}{s^4 + \dots} = -90$$

Example 13.9: (Cont.)

$$f(0^-) = 5$$

$$F(s) = \frac{N(s)}{D(s)} = \frac{5s^3 - 1600}{s(s^3 + 18s^2 + 90s + 800)} \quad (\text{strictly proper})$$

For final values, check pole locations

$$f(\infty) = \lim_{s \rightarrow 0} sF(s) = -2$$

Transform circuit analysis

Transform Circuit Analysis

- Given a circuit with some initial state at $t=0^-$ and an excitation $x(t)$ starting at $t=0$, find the resulting behavior of any voltage or current $y(t)$ for $t=0$.
- Zero-state response, natural response, forced response, zero-input response and complete response.

Zero-State Response

- Zero-state response: a circuit with no stored energy at $t=0^-$.

For an n - th order network,

$$a_n \frac{d^n y}{dt^n} + \dots + a_1 \frac{dy}{dt} + a_0 y = b_m \frac{d^m x}{dt^m} + \dots + b_1 \frac{dx}{dt} + b_0 x$$

⇓

$$Y(s) = L[y(t)], X(s) = L[x(t)]$$

$$L\left[\frac{d^k y}{dt^k}\right] = s^k Y(s) \text{ ("zero initial state")}$$

⇓

$$H(s) \equiv \frac{Y}{X} = \frac{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0}{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}$$

(same as the s - domain network function)

Zero-State Response

Steps :

(1). Draw s - domain diagram, obtain $H(s) = \frac{Y(s)}{X(s)}$

(2). $x(t) \rightarrow X(s)$, $Y(s) = H(s)X(s)$

(3). $y(t) = L^{-1}[Y(s)]$

$$H(s) = \frac{N_H(s)}{P(s)}, \quad X(s) = \frac{N_X(s)}{D_X(s)}$$

$P(s)$: characteristic polynomial

Step Response

(zero initial state, by definition)

$$x(t) = u(t) = 1, t > 0$$


$$X(s) = 1/s$$

$$Y(s) = H(s) \times \frac{1}{s} = \frac{N_H(s)}{sP(s)}$$




A pole at the origin

Example 13.10: Step Response

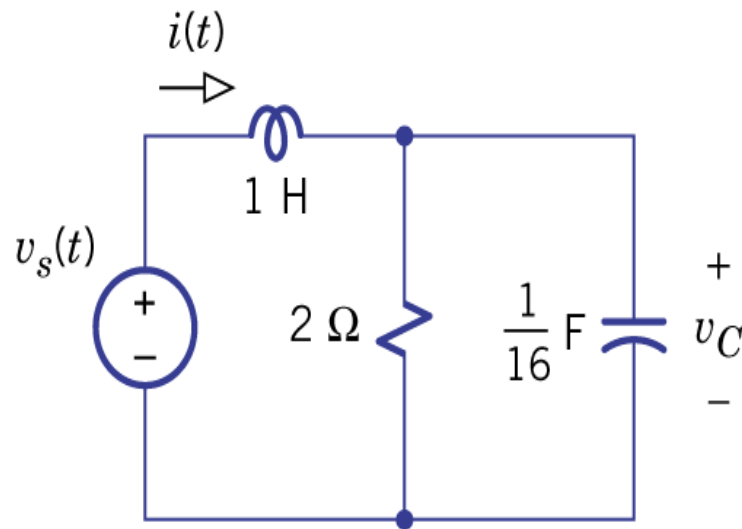

(a) Circuit for Example 13.10

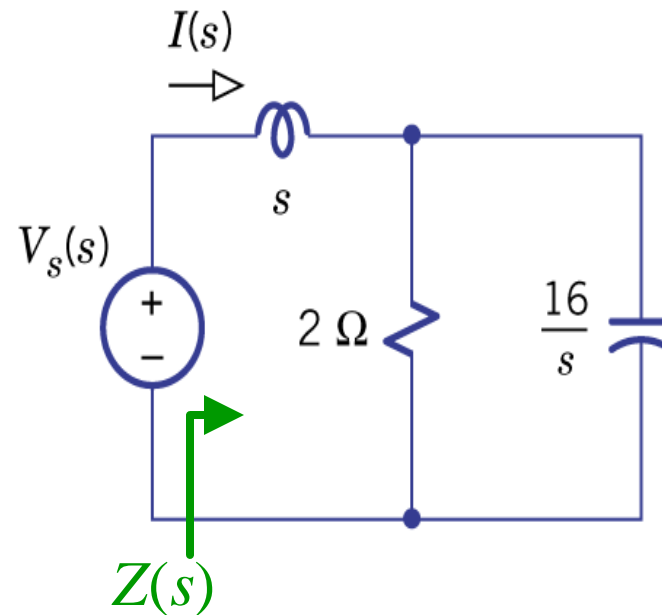

(b) s-domain diagram

$$I(s) = V_s(s)H(s)$$

$$\frac{1}{H(s)} = Z(s) = s + (2 \parallel s/16), \quad V_s(s) = \frac{1}{s}$$

Example 13.10: (Cont.)

$$I(s) = H(s) \times \frac{1}{s} = \frac{s+8}{s(s+4)^2} = \frac{0.5}{s} - \frac{0.5}{s+4} - \frac{1}{(s+4)^2}$$

$$i(t) = 0.5 - 0.5e^{-4t} - te^{-4t}, \quad t \geq 0$$

Steady state response

natural response

$$i(0^+) = \lim_{s \rightarrow \infty} sI(s) = 0$$

$$i(\infty) = \lim_{s \rightarrow 0} sI(s) = 0.5$$

Zero-state AC response

$$x(t) = X_m \cos(\mathbf{b}t + \mathbf{f}_x)$$

Forced response

From phasor analysis

$$D_X(s) = s^2 + \mathbf{b}^2$$

Natural response
from $Y(s)$

$$Y(s) = \frac{N_H(s)N_X(s)}{P(s)(s^2 + \mathbf{b}^2)} \equiv Y_N(s) + Y_F(s) = \frac{N_N(s)}{P(s)} + \frac{N_F(s)}{s^2 + \mathbf{b}^2}$$

$$y(t) = y_N(t) + y_F(t)$$

$$y_F(t) = Y_m \cos(\mathbf{b}t + \mathbf{f}_y) \quad \text{where} \quad \underline{Y} = H(j\mathbf{b})\underline{X} = Y_m \angle \mathbf{f}_y$$

Example 13.11: Zero-State AC Response (from Fig. 13.9)

$$v_s(t) = 50 \cos 8t, \quad t \geq 0 \Rightarrow V_s(s) = \frac{50s}{s^2 + 64}$$

$$I(s) = H(s)V_s(s) = \frac{50s^2 + 400s}{(s+4)^2(s^2 + 64)}$$

$$= \frac{-1}{s+4} - \frac{10}{(s+4)^2} + \frac{N_F(s)}{s^2 + 64} \equiv I_N(s) + \underbrace{I_F(s)}_{\text{Phasor analysis}}$$

$$i_N(t) = -e^{-4t} - 10te^{-4t}$$

Phasor analysis

Example 13.11: (Cont.)


$$\underline{V}_s = 50\angle 0^\circ, H(j8) = 0.141\angle -81.9^\circ$$

$$\underline{I} = H(j8) \cdot \underline{V}_s = 7.07\angle -81.9^\circ$$

$$i_F(t) = 7.07 \cos(8t - 81.9^\circ)$$

$$i(t) = i_N(t) + i_F(t) = -(1 + 10t)e^{-4t} + 7.07 \cos(8t - 81.9^\circ), t \geq 0$$
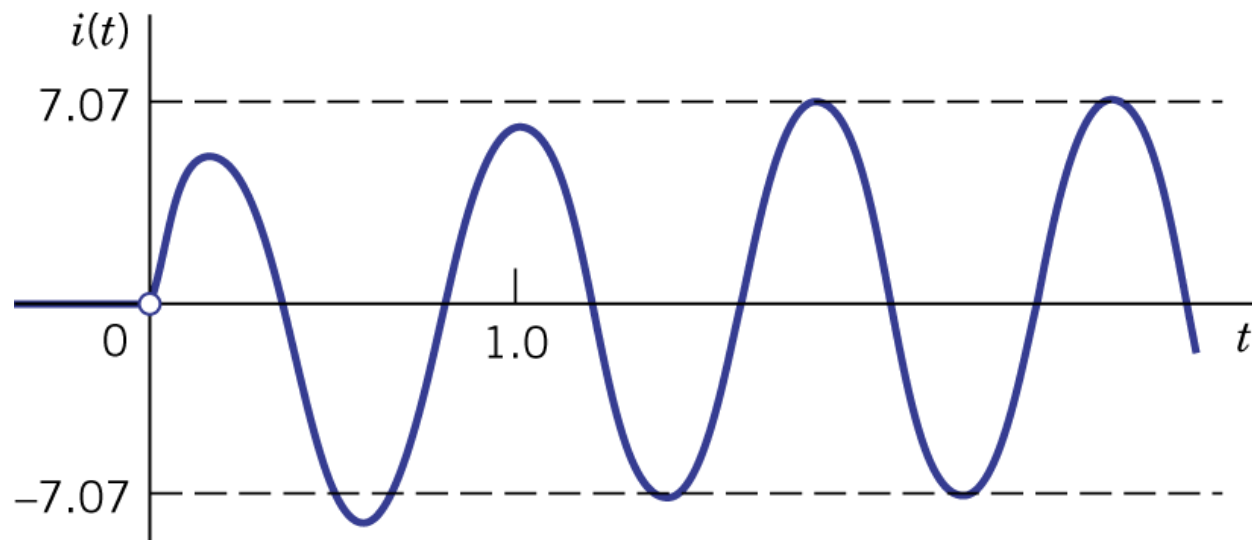
$$i(0^+) = -1 + 7.07 \cos(-81.9^\circ) = 0$$



Natural Response and Forced Response

$$\text{Let } H(s) = \frac{1}{(s+1)(s+2)}, \quad y_N(t) = A_1 e^{-t} + A_2 e^{-2t}$$

$$x(t) = 10e^{-s_0 t}$$

$$\text{case (1): } s_0 = -3 \quad (s_0 \neq -1, s_0 \neq -2)$$

$$Y(s) = H(s)X(s) = \frac{10}{(s+1)(s+2)(s+3)} = \frac{5}{s+1} + \frac{-10}{s+2} + \frac{5}{s+3}$$

$$y(t) = 5e^{-t} - 10e^{-2t} + 5e^{-3t}, \quad t \geq 0$$

(or use phasor analysis to find the forced response)

Natural Response and Forced Response (Cont.)

case (2) : $s_0 = -2$

$H(-2) \rightarrow \infty$

\Rightarrow phasor analysis is not applicable when

excitation frequency is the same as a natural frequency

\Rightarrow use transform analysis

$$Y(s) = \frac{10}{(s+1)(s+2)^2} = \frac{10}{s+1} + \frac{-10}{s+2} + \frac{-10}{(s+2)^2}$$

$$y(t) = \underset{\substack{\uparrow \\ \text{natural}}}{10e^{-t}} - \underset{\substack{\uparrow \\ \text{mixed}}}{10e^{-2t}} - \underset{\substack{\uparrow \\ \text{forced}}}{10te^{-2t}}, \quad t \geq 0$$

Zero-Input Response


- The excitation equals zero for $t=0$ but the circuit contains stored energy at $t=0^-$.
- Thévenin/Norton equivalent circuits can be established.

Zero-Input Response (Cont.)


$$i_C(t) = Cv'_C(t)$$

$$I_C(s) = C[sV_C(s) - v_C(0^-)]$$

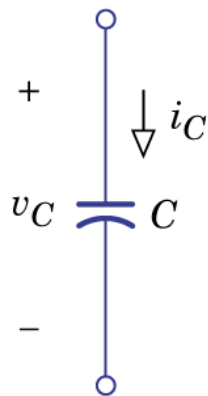
$$\Rightarrow \begin{cases} \text{Thevenin : } V_C(s) = \frac{v_C(0^-)}{s} + \frac{1}{sC} I_C(s) \\ \text{Norton : } I_C(s) = sCV_C(s) - Cv_C(0^-) \end{cases}$$



(a) Capacitor in the time domain

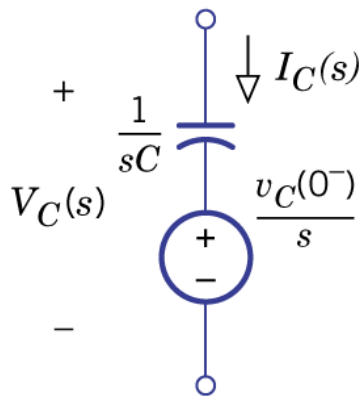

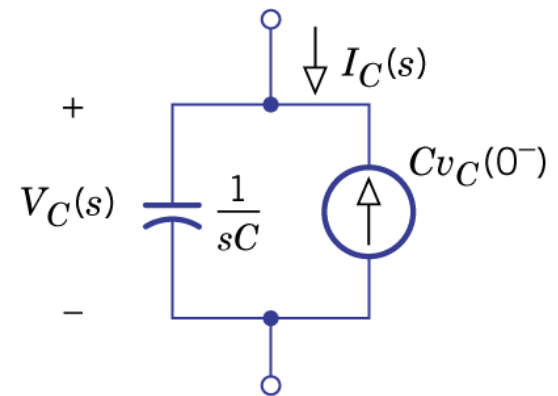(b) s -domain Thévenin model of initial voltage




(c) s -domain Norton model of initial voltage

Zero-Input Response (Cont.)


$$v_L(t) = Li'_L(t)$$

$$V_L(s) = L[sI_L(s) - i_L(0^-)]$$

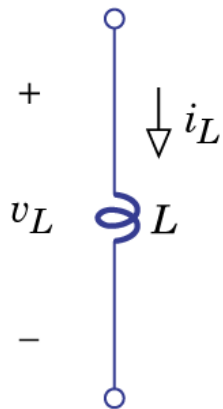
$$\Rightarrow \begin{cases} \text{Thevenin : } V_L(s) = sLI_L(s) - Li_L(0^-) \\ \text{Norton : } I_L(s) = \frac{i_L(0^-)}{s} + \frac{1}{sL}V_L(s) \end{cases}$$



(a) Inductor in the time domain

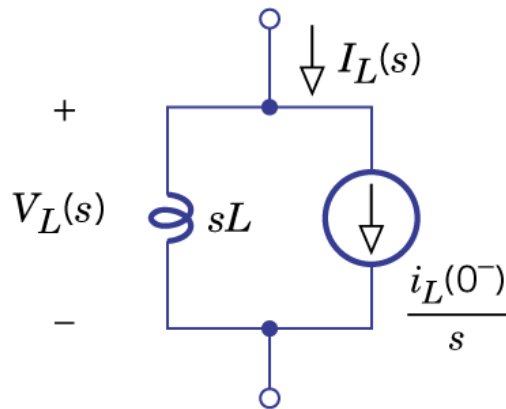


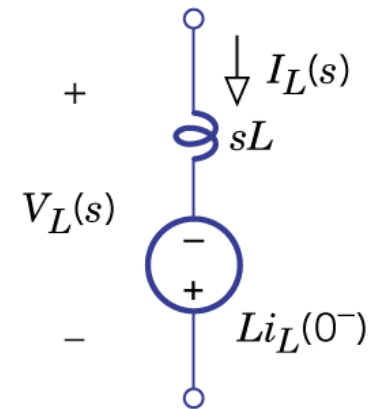(b) s -domain Norton model of initial current




(c) s -domain Thévenin model of initial current

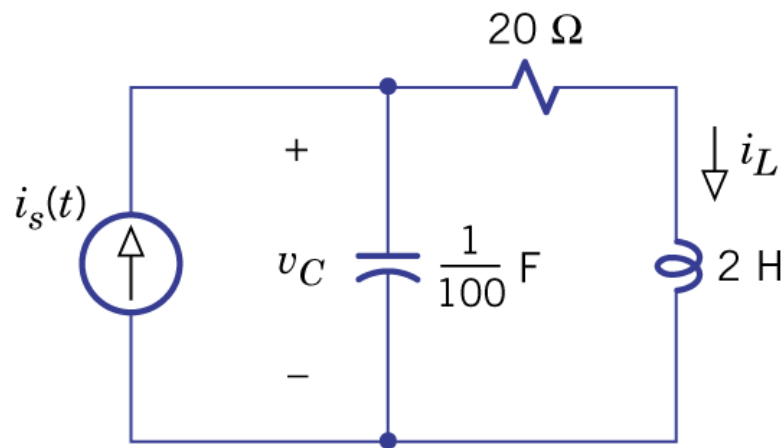Example 13.12: Calculating a Zero-Input Response



(a) Circuit for Example 13.12

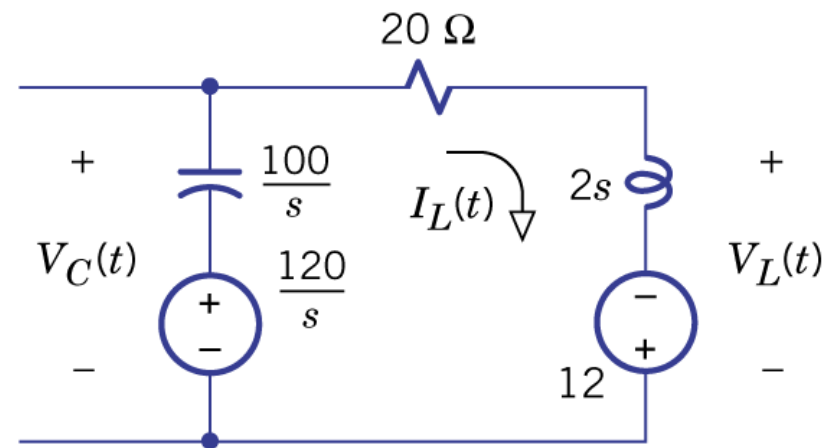

(b) s -domain diagram with initial-value sources

$$i_s(t) = 6A, t < 0$$

DC steady state analysis :

$$i_L(0^-) = 6A, v_C(0^-) = 6 \cdot 20 = 120V$$

Example 13.12: (Cont.)

zero - input response :

$$\left(2s + 20 + \frac{100}{s} \right) I_L(s) = 12 + \frac{120}{s}$$

$$I_L(s) = \frac{6s + 60}{s^2 + 10s + 50} = \frac{Bs + C}{s^2 + 2as + w_0^2}$$

$$\Rightarrow \mathbf{a} = 5, \mathbf{b} = 5, K = 6 - j6 = 6\sqrt{2} \angle -45^\circ$$


$$i_L(t) = K_m e^{-at} \cos(\mathbf{b}t + \mathbf{f})$$

$$= 6\sqrt{2}e^{-5t} \cos(5t - 45^\circ) \text{ A}, t \geq 0$$


Complete Response

- Complete response: complete response = zero-input response + zero-state response (with fictitious sources)

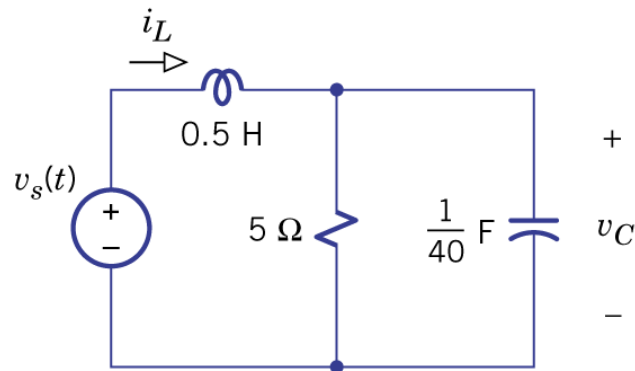Example 13.13: Calculating a Complete Response



(a) Circuit for Example 13.13

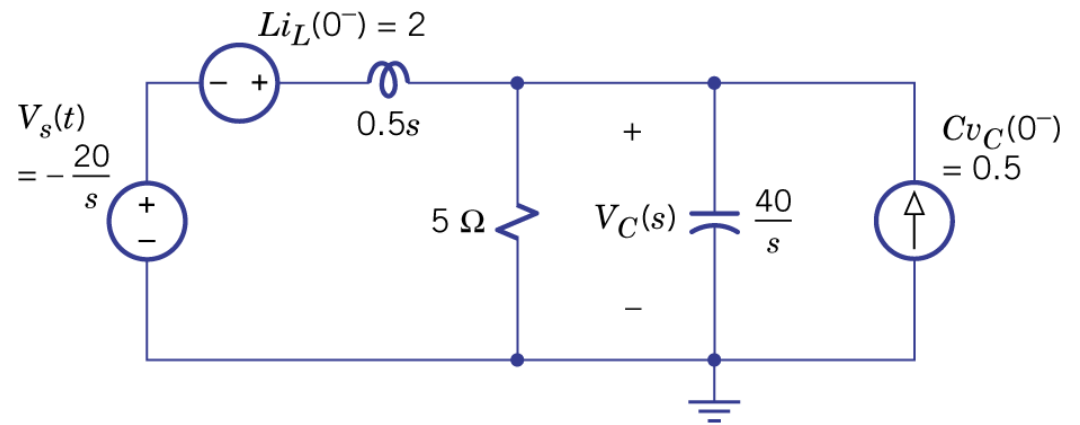

(b) s-domain diagram with input and initial-value sources

$$v_s(t) = \begin{cases} 20\text{V}, & t < 0 \\ -20\text{V}, & t \geq 0 \end{cases} \quad \text{find } v_C(t)$$

DC steady state analysis for $t < 0$


$$i_L(0^-) = 4\text{A}, \quad v_C(0^-) = 20\text{V}, \quad V_s(s) = -\frac{20}{s}$$

Example 13.13: (Cont.)

$$\left(\frac{s}{40} + \frac{1}{5} + \frac{1}{0.5s} \right) V_C(s) = \frac{2 - 20/s}{0.5s} + 0.5$$

$$V_C(s) = \frac{A_1}{s} + \frac{Bs + C}{s^2 + 8s + 80}$$

$$v_C(t) = -20 + 20\sqrt{5}e^{-4t} \cos(8t - 26.6^\circ)V, \quad t \geq 0$$

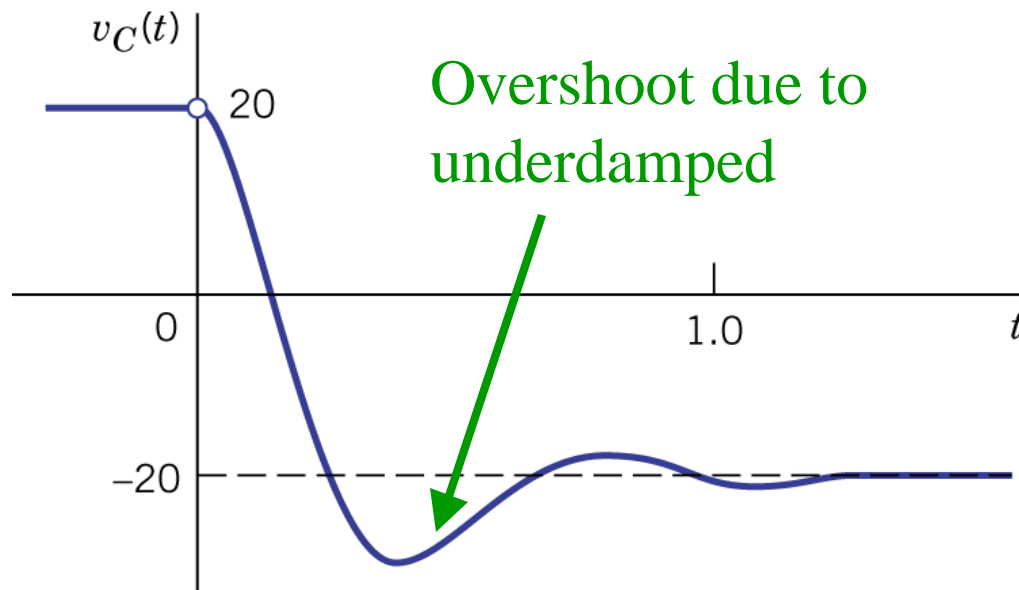

Chapter 13: Problem Set

- 6, 10, 16, 21, 25, 28, 31, 35, 38, 42, 46, 51, 57, 58, 63, 65