

電路學

*Circuits: Engineering Concepts and Analysis of
Linear Electric Circuits*

李百祺

Course Information

- 時間: 週五 9:10am-12:10pm
- 地點: 電二106
- 教科書: Circuits, by A. Bruce Carlson, Brooks/Cole, 2000.

聯絡方式: 博理館425室 (33663551)

Email: paichi@cc.ee.ntu.edu.tw

Web: <http://ultrasound.ee.ntu.edu.tw> → 課程
→ 電路學

Course Content

- Chapter 1: 1.4, 1.5
- Chapter 2: 2.3, 2.4, 2.5
- Chapter 3: 3.2, 3.3
- Chapter 4: 4.1, 4.2, 4.3
- Chapter 5.3
- Chapter 6: 6.1, 6.2, 6.3
- Chapter 7: 7.1, 7.2
- Chapter 9: 9.1, 9.2, 9.3, 9.4
- Chapter 11: 11.1, 11.2, 11.4
- Chapter 13: 13.1, 13.2, 13.3
- Chapter 14: 14.1, 14.2, 14.3

Grading and Homework


- 考試: 5次小考及期末考
- 評分方式: 小考共佔60% (最低分的一次小考不記分)、期末考佔40%
- 習題: Homework problems will be assigned but not graded. Selected problems will be solved in class.

電路學學什麼？

- 學電路
- 學電路分析
- 學電路分析與設計
- 學線性電路分析與設計
- 學集總 (lumped) 線性電路分析與設計
- 學基本代數分析方法及應用phasor, Fourier transform, Laplace transform 之分析方法

Chapter 1: Circuit Variables and Laws

Chapter 1: Outline

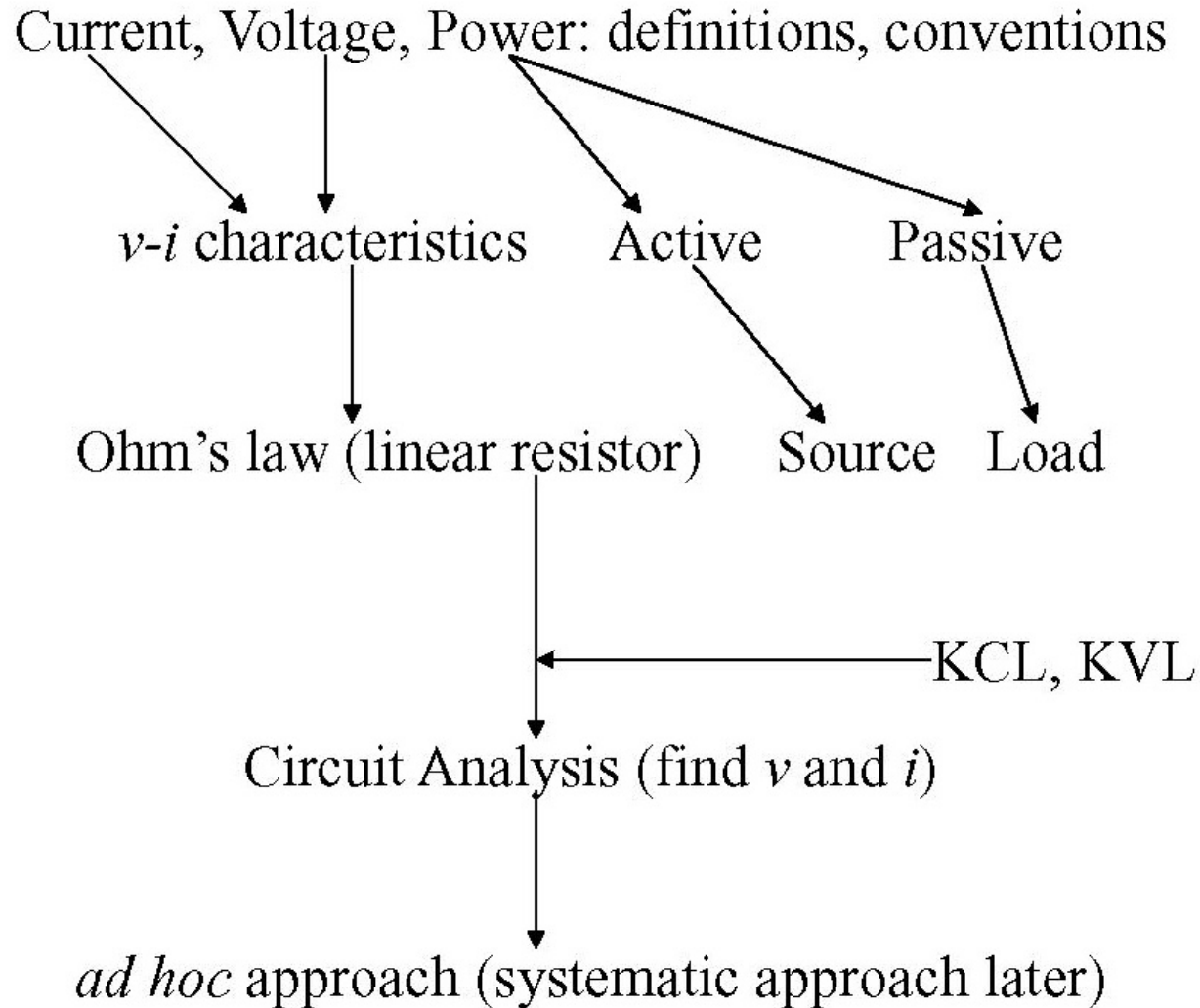

Chapter 1: Circuit Variables and Laws

- Quick review of (self reading):
 - Definition of Current, Voltage, Polarity
 - Definition of Energy, Power, Source and Load
 - Ohm's law and Resistors
- Kirchhoff's laws
 - Current (KCL)
 - Voltage (KVL)
- Elementary Circuit Analysis
 - Series and Parallel

Fundamentals

Current: Formal Definition

- Current is the net flow of charges, per time, past an arbitrary “plane” in some kind of electrical device.
- We will only be concerned with the flow of positive charges. A negative charge moving to the right is conceptually the same as a positive charge moving to the left.

Current, typically in Amperes [A] → $i = \frac{dq}{dt}$

Charge, typically in Coulombs [C] → dq

Time, typically in seconds [s] → dt

The diagram shows the equation $i = \frac{dq}{dt}$ centered on a light blue background. Three arrows point from text labels to the variables in the equation: one from 'Current, typically in Amperes [A]' to the variable i ; one from 'Charge, typically in Coulombs [C]' to the numerator dq ; and one from 'Time, typically in seconds [s]' to the denominator dt .

The Ampere

- The unit of current is the Ampere, which is a flow of 1 Coulomb of charge per second, i.e.:

$$1[A] = 1[\text{Coul/sec}]$$

- Current is defined in terms of the flow of positive charges.

One coulomb of positive charges per second flowing from left to right

- is equivalent to -

one coulomb of negative charges per second flowing from right to left.

Voltage: Formal Definition

- When we move a charge in the presence of other charges, energy is transferred. Voltage is the change in potential energy as we move between two points; it is a *potential difference*.

The diagram shows the formula $v = \frac{dw}{dq}$ centered in a light blue box. Three arrows point from descriptive text to parts of the formula: one from the left to the variable v , one from the top right to the numerator dw , and one from the bottom right to the denominator dq .

Voltage, typically in Volts [V]

Energy, typically in Joules [J]

Charge, typically in Coulombs [C]


$$v = \frac{dw}{dq}$$

Volt

- The unit of voltage is the Volt. A Volt is defined as a Joule per Coulomb.
- Voltage is defined in terms of the energy gained or lost by the movement of positive charges.

One Joule of energy is lost from an electric system when a Coulomb of positive charges moves from one potential to another potential that is one Volt lower.

Hydraulic Analogy: Voltage and Current

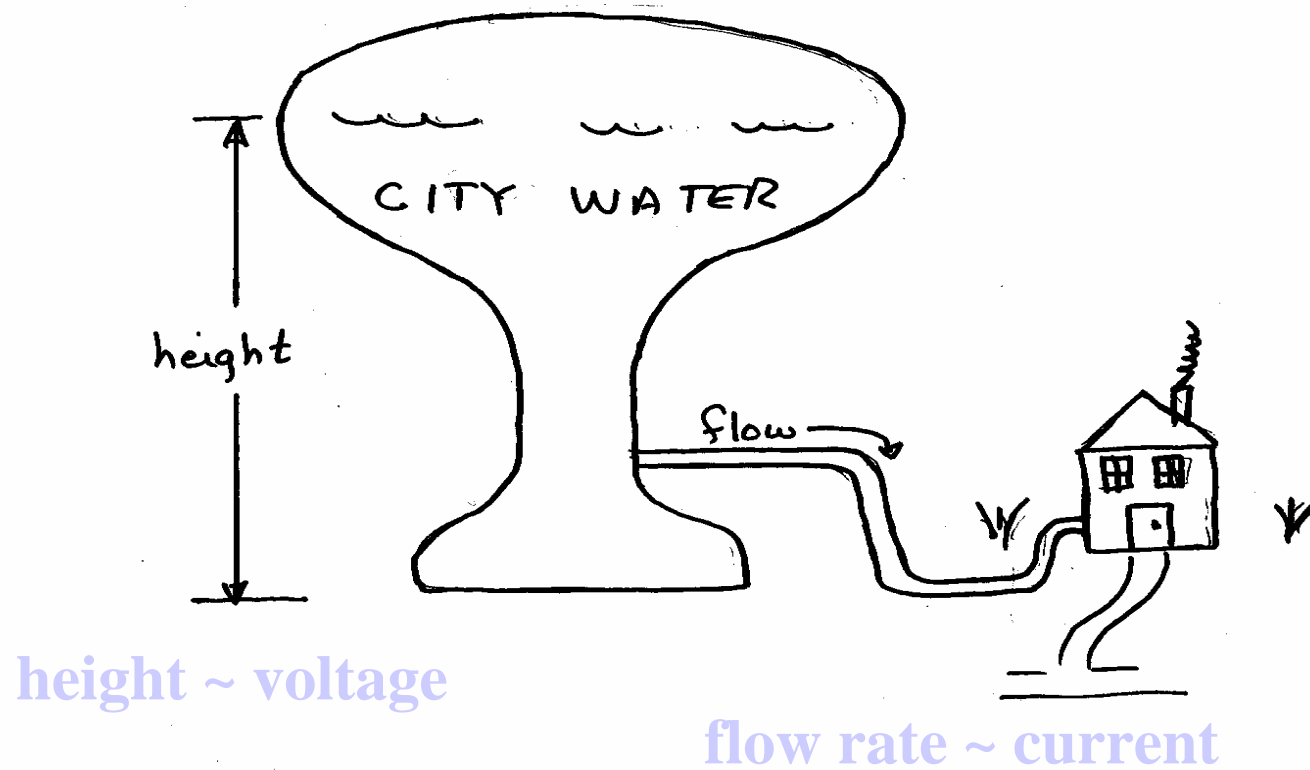


Hydraulic Analogy With Two Paths

Water is flowing *through* the pipes.


There is a height difference *across* these pipes.

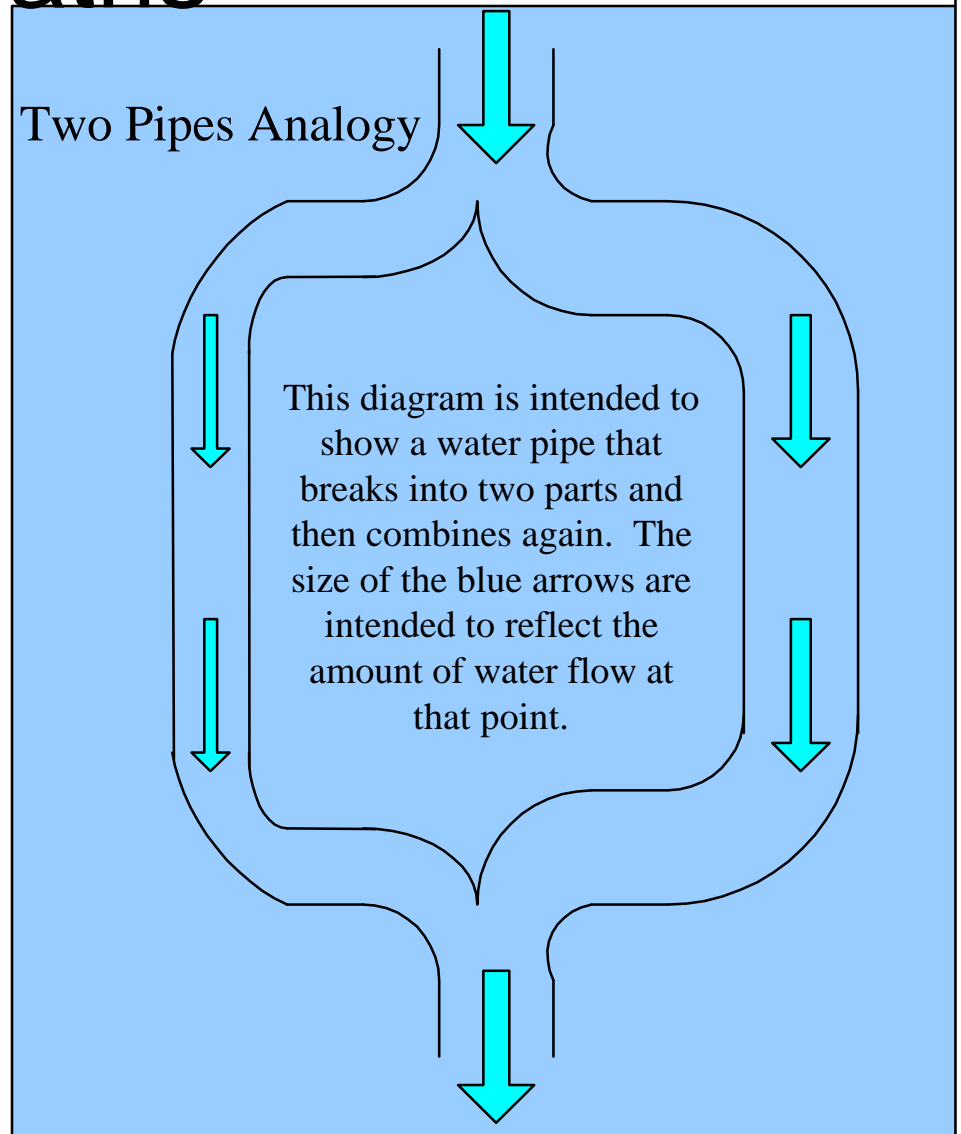We can extend this analogy to current *through* and voltage *across* an electric device...




Current *Through*...

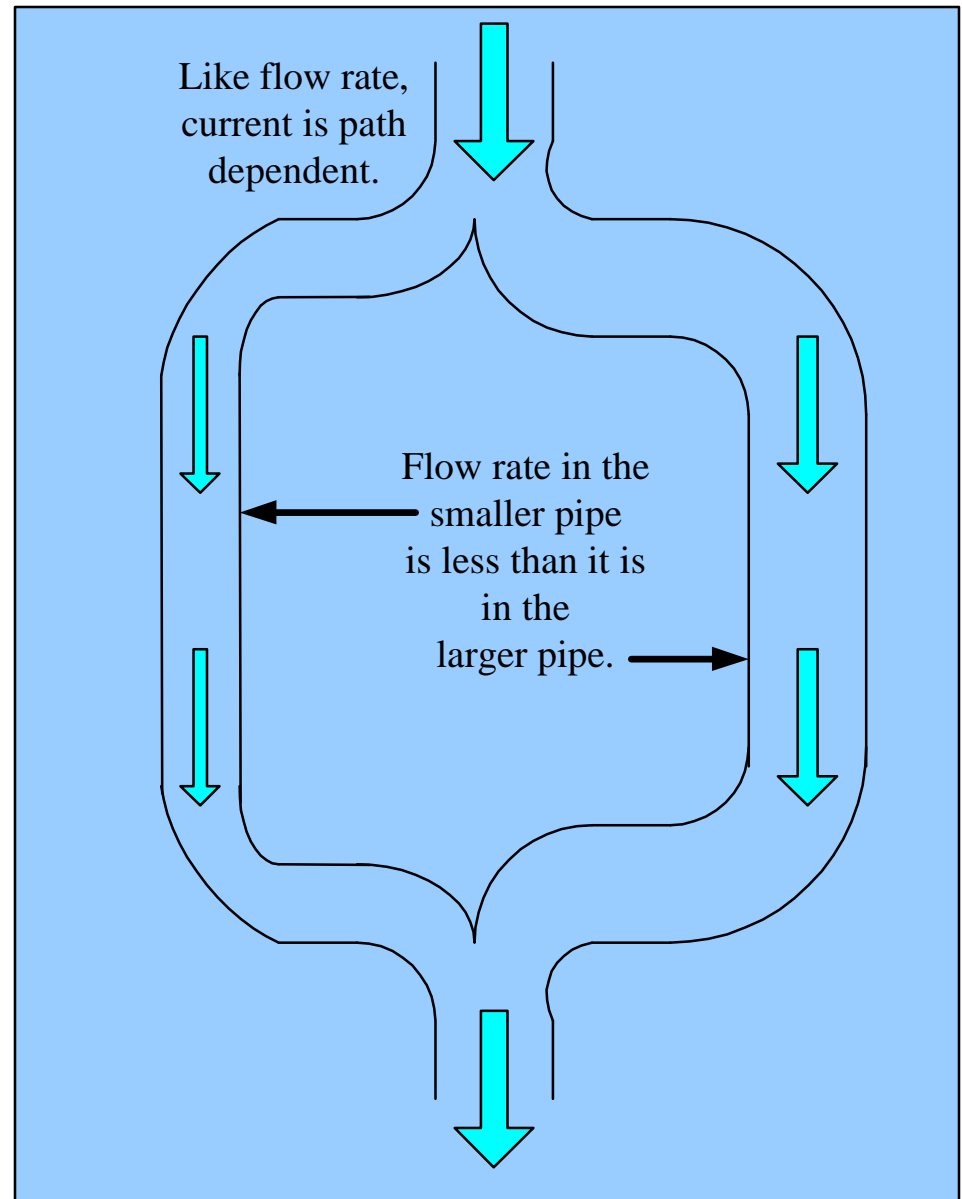If we have two pipes connecting two points, the flow rate through one pipe can be different from the flow rate through the other. The flow rate depends on the path.



...Voltage Across

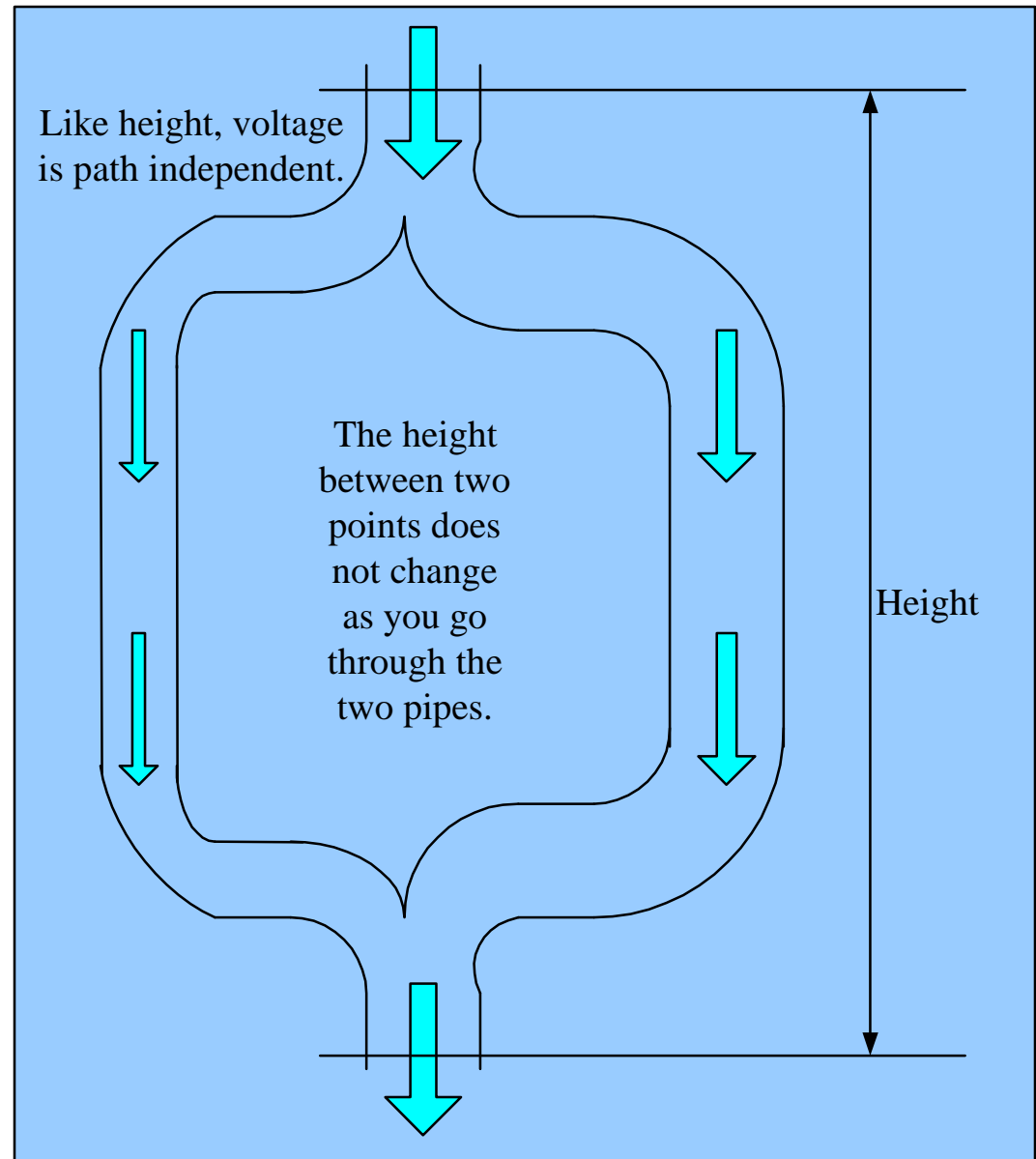No matter which path you follow, the height is the same across those two points. The height does not depend on the path



Polarities


- Polarity: the sign, of the voltages and currents we use.
- Which way is the current flowing?
Where is the potential higher?
- Two concepts are used:
 - Reference polarities
 - Actual polarities

Reference and Actual Polarities

- The reference polarity is a direction chosen for the purposes of keeping track.
- Reference polarity must be assigned.
- The actual polarity is the direction something is actually going.
 - If the actual polarity is the same direction as the reference polarity, we use a positive sign for the value of that quantity.
 - If the actual polarity is the opposite direction from the reference polarity, we use a negative sign for the value of that quantity.

Polarities for Currents

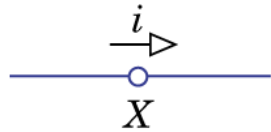
- For current, the reference polarity is given by an arrow.
- The actual polarity is indicated by a value that is associated with that arrow.



(a) Current reference arrow for equivalent positive charge transfer from left to right





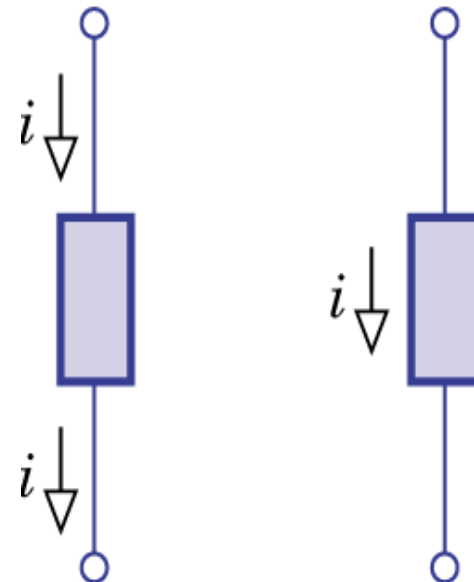(b) Actual current direction when i is negative



Polarities for Voltages

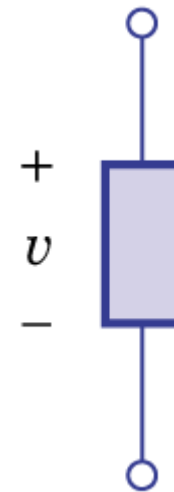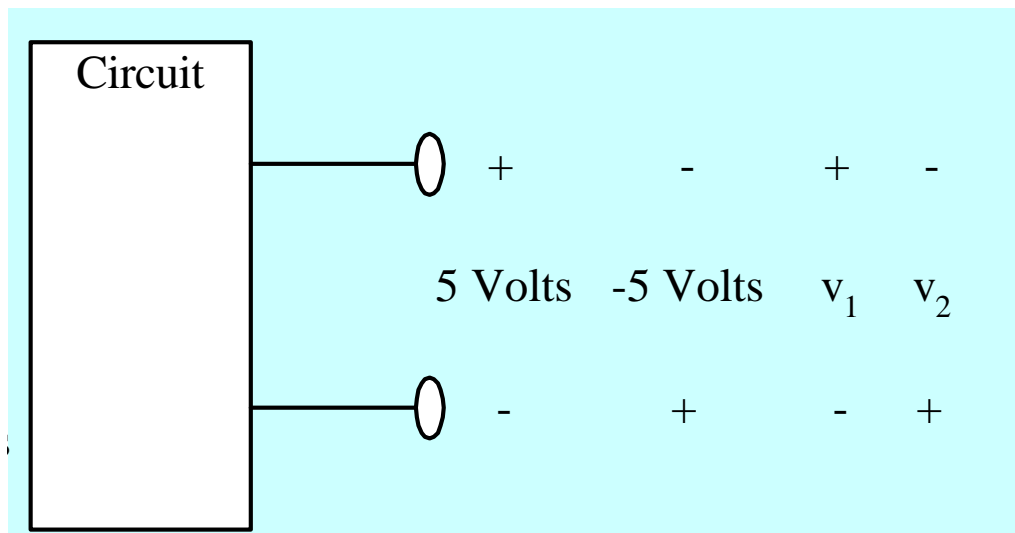- The reference polarity for voltage is given by a + symbol and a – symbol.
- The actual polarity is indicated by a value that is placed between the + and - symbols.
- The voltages v_1 and v_2 are not defined until the + and – symbols are shown.



Energy and Power
Source and Load (Polarity)

Overview

- Definitions of Energy and Power
- Sign Conventions for power direction
- Which way do the energy and power go (Active or Passive)?
- Hydraulic analogy

Joule Definition

- The unit for energy is the Joule [J].
- A Joule is a Newton-meter.
- In everything that we do in this class, energy will be conserved.
- Supply vs. Absorb: Active vs. Passive.

Power

- Power is the rate of change of the energy. It is the rate at which the energy is absorbed or delivered.
- Supply vs. Absorb: Active vs. Passive.

The diagram shows the equation $p = \frac{dw}{dt}$ centered in a light blue box. Three arrows point from descriptive text to parts of the equation: one from the left to the variable p , one from the top right to the numerator dw , and one from the bottom right to the denominator dt .

Power, typically in Watts [W]

Energy, typically in Joules [J]

Time, typically in seconds [s]

$$p = \frac{dw}{dt}$$

Power from Voltage and Current


Power can be found from the voltage and current, as shown below. Note that if voltage is given in [V], and current in [A], power will come out in [W].

$$p = \frac{dw}{dt} = \frac{dw}{dq} \times \frac{dq}{dt} = vi$$


Sign Convention – Definition

- The passive sign convention is when the reference polarity for the current is in the direction of the reference voltage
- The active sign convention is when the reference polarity for the current is in the direction of the reference voltage rise.

d

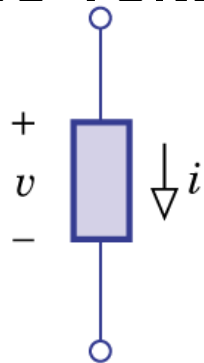

(a) Passive polarity convention

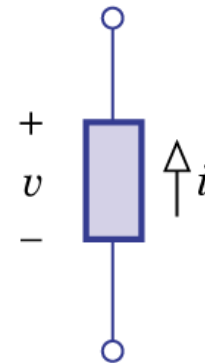


(b) Active polarity convention

Using Sign Conventions for Power Direction – The Rules

- When we use the passive sign convention to assign reference polarities, vi gives the power absorbed, and $-vi$ gives the power delivered.
- When we use the active sign convention to assign reference polarities, vi gives the power delivered, and $-vi$ gives the power absorbed.

Example of Determining the Power with Polarity

	Passive Convention	Active Convention
Power absorbed	$p_{abs} = vi$	$p_{abs} = -vi$
Power delivered	$p_{del} = -vi$	$p_{del} = vi$

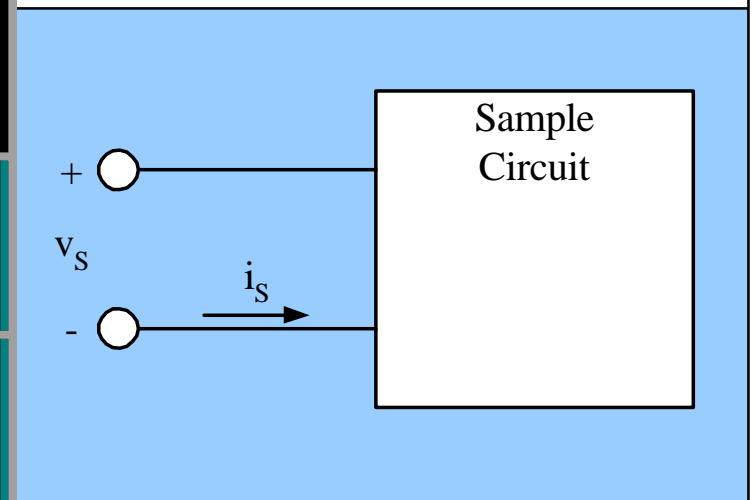

Hydraulic Analogy for Power Directions

- Imagine a waterfall.




The waterflow is in the direction of the drop in height. Thus, this is analogous to the passive sign convention.


$$p_{abs} = vi$$

Another Hydraulic Analogy

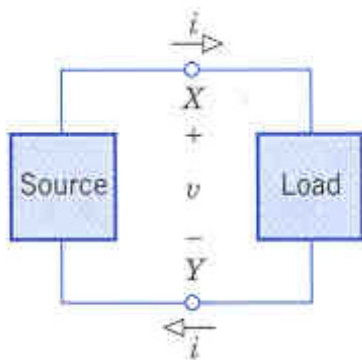- As Carlson puts it, “The pump (*source*) forces water flow (*current*) through pipes (*wires*) to drive the turbine (*load*). The water pressure (*potential*) is higher at the inlet port of the turbine than at the outlet.”



(a) Source-load circuit

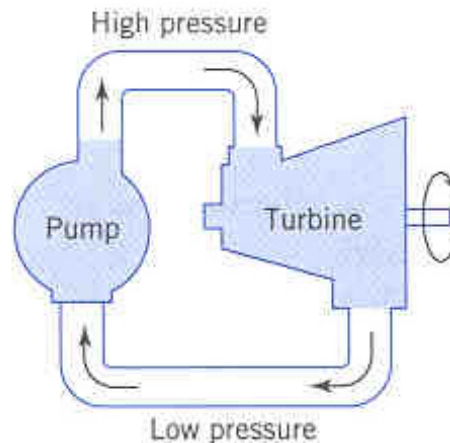

(b) Analogous hydraulic system

Figure 1.9

Note that the Source is given with reference polarities in the active convention, and the Load with reference polarities in the passive convention. As a result, in this case, since all quantities are positive, the Source delivers power, and the Load absorbs power.



Some Resistive Circuit Elements

Overview



- Independent voltage source and current source
- Resistors and Ohm's Law
- How to describe “behavior” of a circuit:
 - $v(t), i(t)$
 - i - v curve (v - i curve)

Voltage Sources

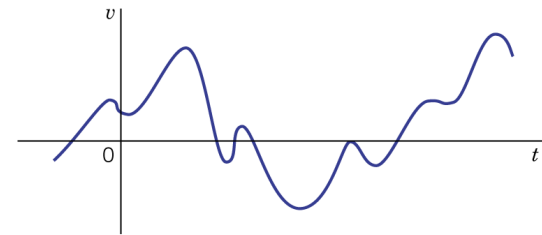
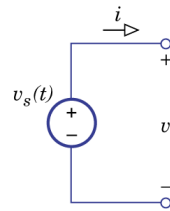
- A voltage source is a two-terminal circuit element that maintains a voltage across its terminals.
- The voltage value is the defining characteristic.
- Any value of the current can go through the voltage source (including zero).



(a) Ideal voltage source

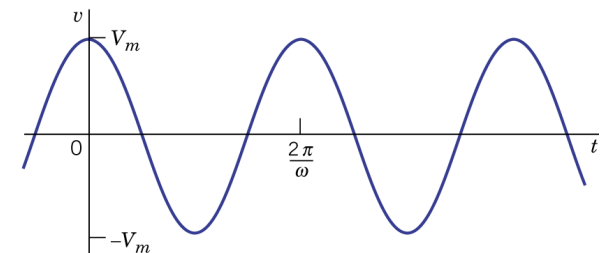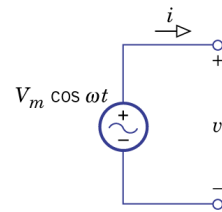


(b) AC voltage source

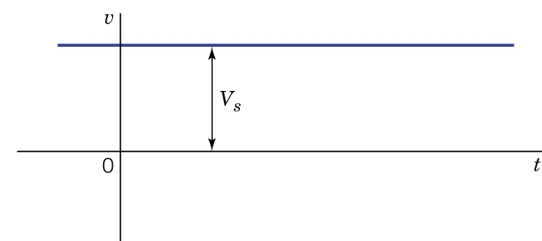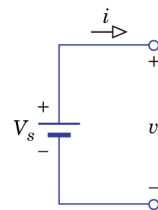

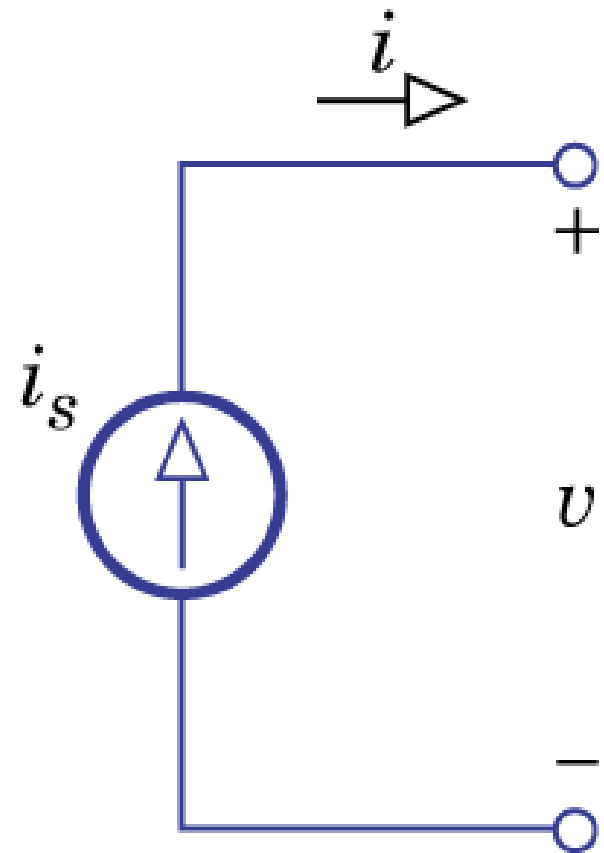
(c) Battery

Current Sources


- A current source is a two-terminal circuit element that maintains a current through its terminals.
- The current value is the defining characteristic.
- Any voltage can be across the current source (including zero)



Ideal Sources

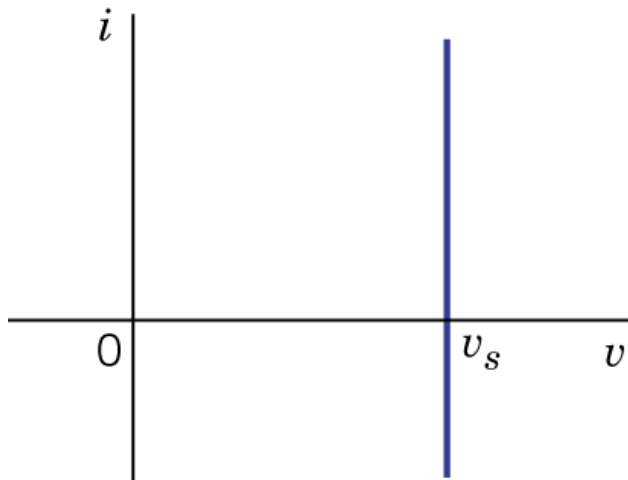

(a) Voltage source

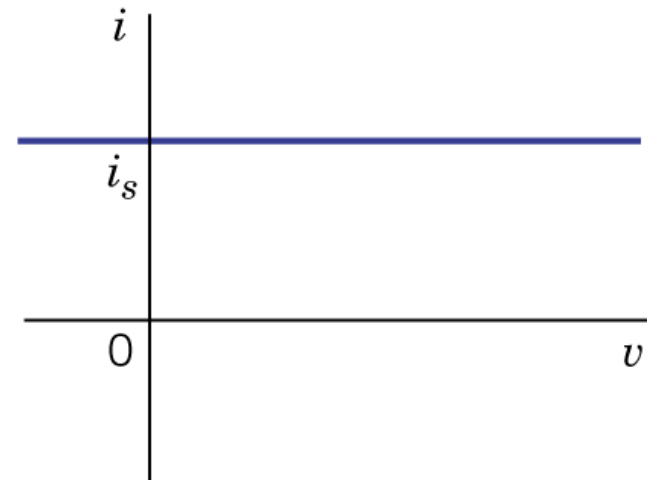


(b) Current source


i - v curve (v - i curve)

Ohm's Law and Resistors

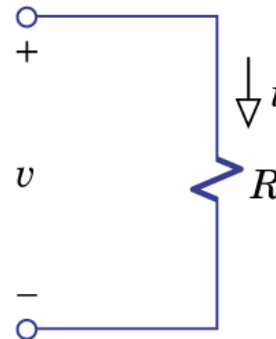- A (linear) resistor is a two terminal circuit element that has a constant ratio of the voltage across its terminals to the current through its terminals.
- Passive sign convention.



(a) Symbol

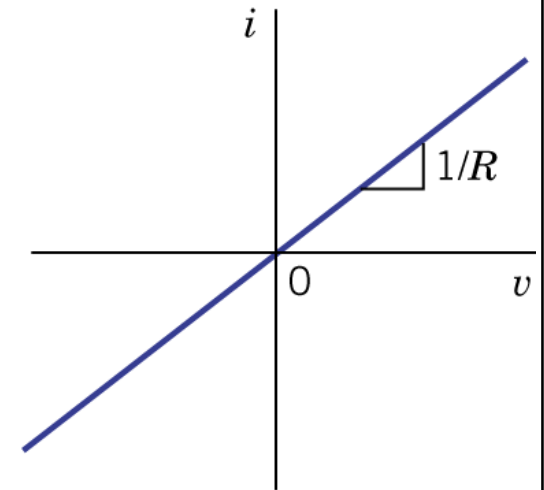

(b) i - v curve

Ohm's law:


$$R = \frac{v_R}{i_R}$$

Lumped Circuits

- Lumped-parameter models: spatially distributed property is lumped entirely at one point.
- EM wavelength is much larger than dimensions of the circuit.
- Only lumped circuits are considered in this course.



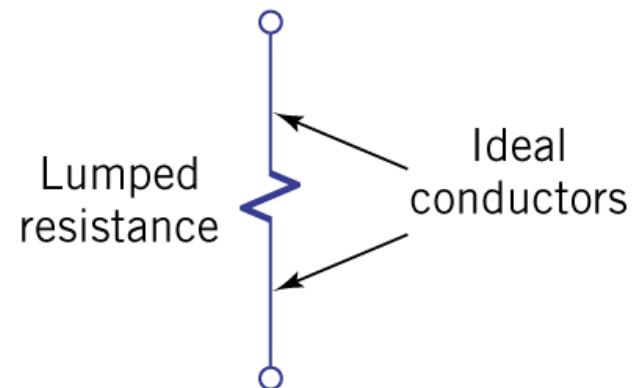(a) Resistance distributed between two terminals



(b) Lumped-parameter model



Lumped vs. Distributed

- Lumped circuit:
 - electromagnetic wavelength \gg largest dimension of the circuit
 - the respective locations of circuit elements are not important
- Distributed circuits
 - when the lumped approximation is not valid
 - examples: transmission lines (will be covered in the EM class)

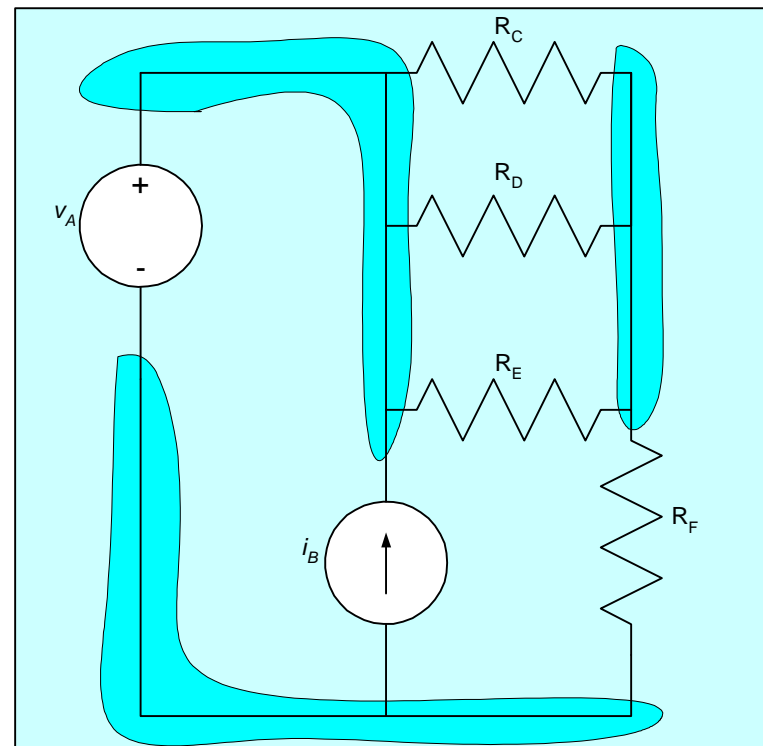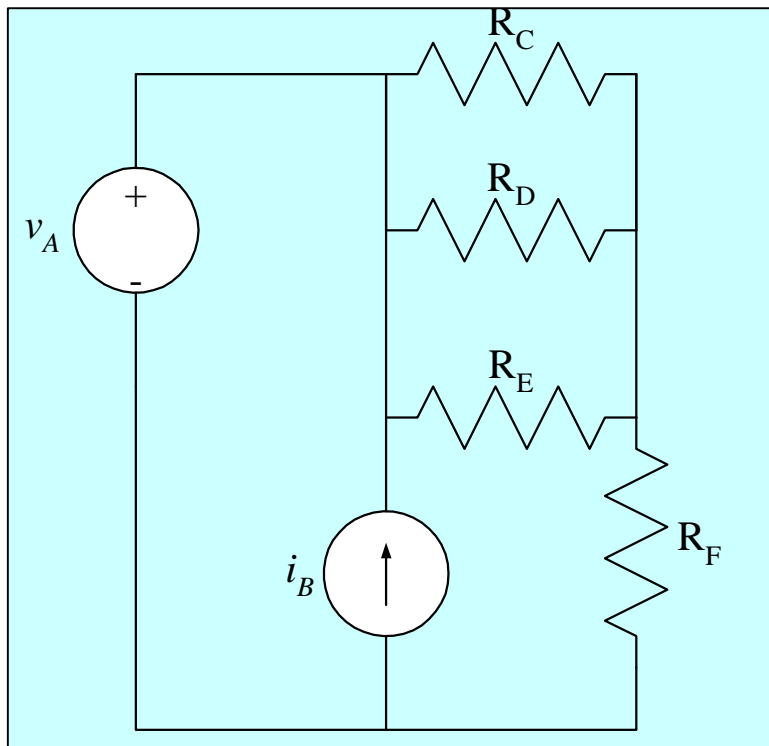1.4 Kirchhoff's Laws

Node


- Node: connection point of two or more circuit elements.



KCL (Node)

- Charge is conserved and does not accumulate at a node.
- Kirchhoff's current law (KCL): The sum of the currents leaving any node equals the sum of the currents entering that node.
- Elements in series carry the same current. (Dual with

KVL

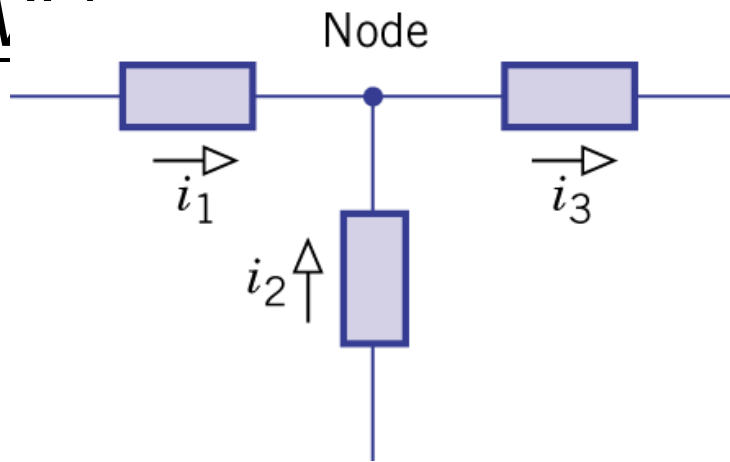


$$i_3 = i_1 + i_2$$

or

$$i_1 + i_2 - i_3 = 0$$

KCL (Supernode)

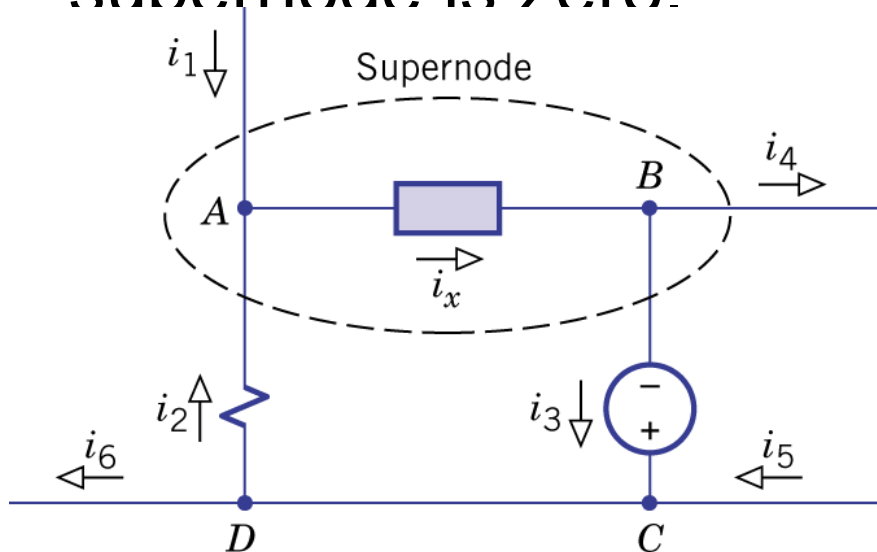- Supernode: any closed region contains two or more nodes and the wires intersected by the boundary are only intersected once (closed surface).
- The algebraic sum of all currents into any supernode is zero.





$$\left. \begin{array}{l}
 \text{Node A} \\
 \downarrow \\
 i_1 + i_2 - i_x = 0 \\
 i_x - i_3 - i_4 = 0 \\
 \uparrow \\
 \text{Node B}
 \end{array} \right\} \Rightarrow i_1 + i_2 - i_3 - i_4 = 0$$

Supernode


Loop

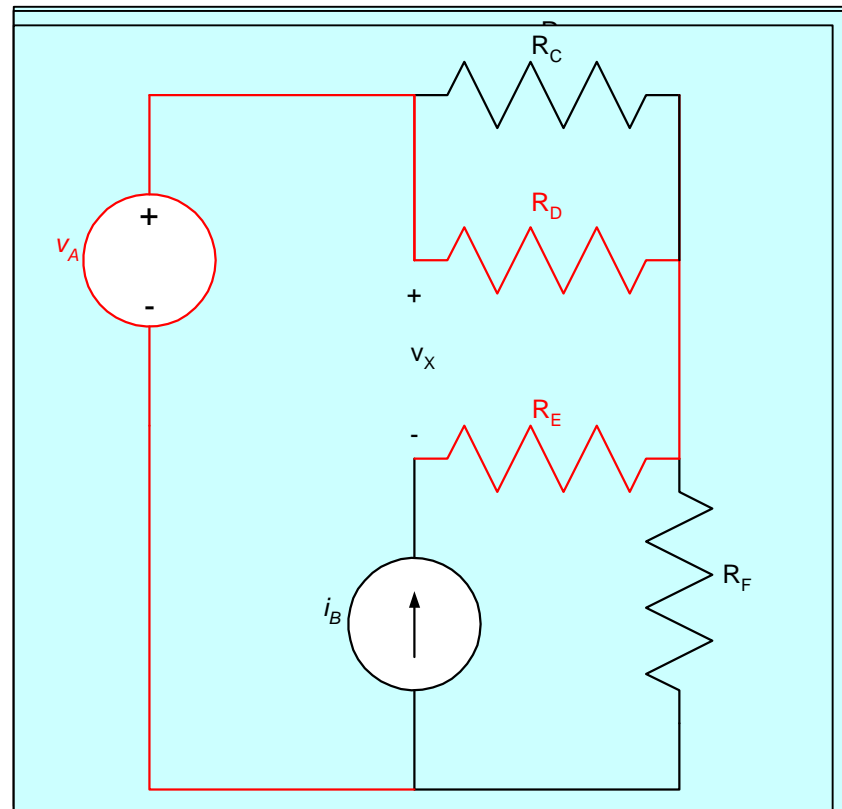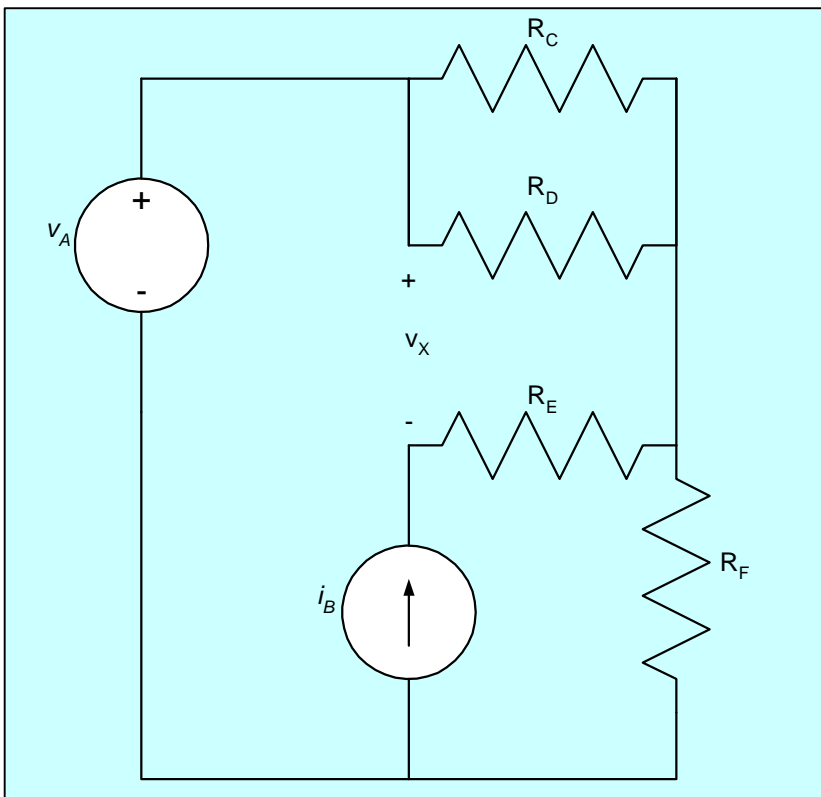- A loop is any path that goes from node to node, returns to the starting node and passing only once through each node.




KVL (Loop)

- Kirchoff's voltage law (KVL): the sum of voltage drop around a loop is the sum of voltage rise.
- The algebraic sum of all voltage drops around any loop equals zero.
- Elements in parallel have the same voltage across each one of them. (Dual with KCL)

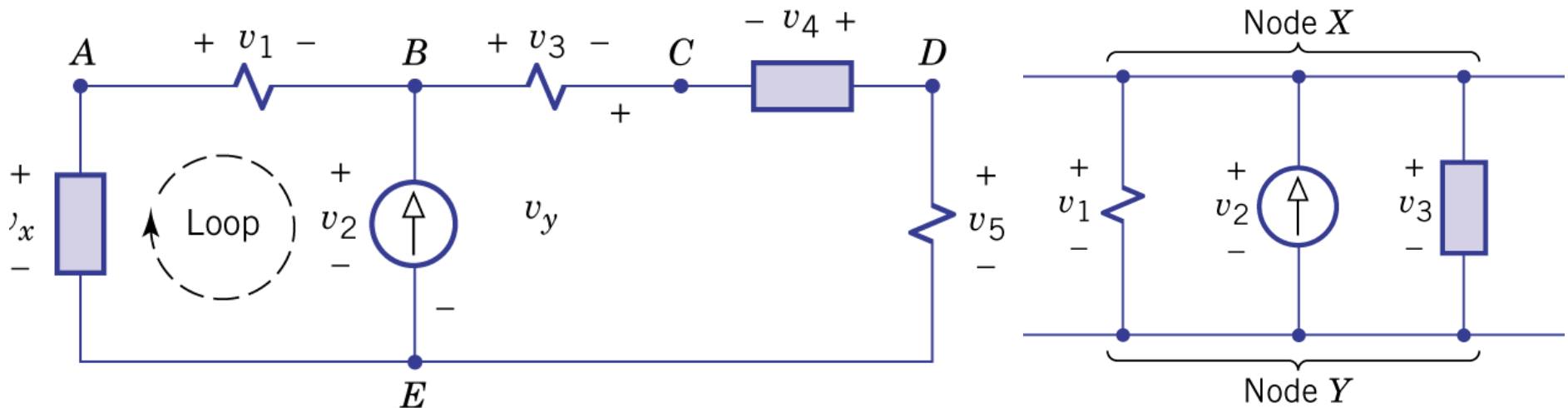

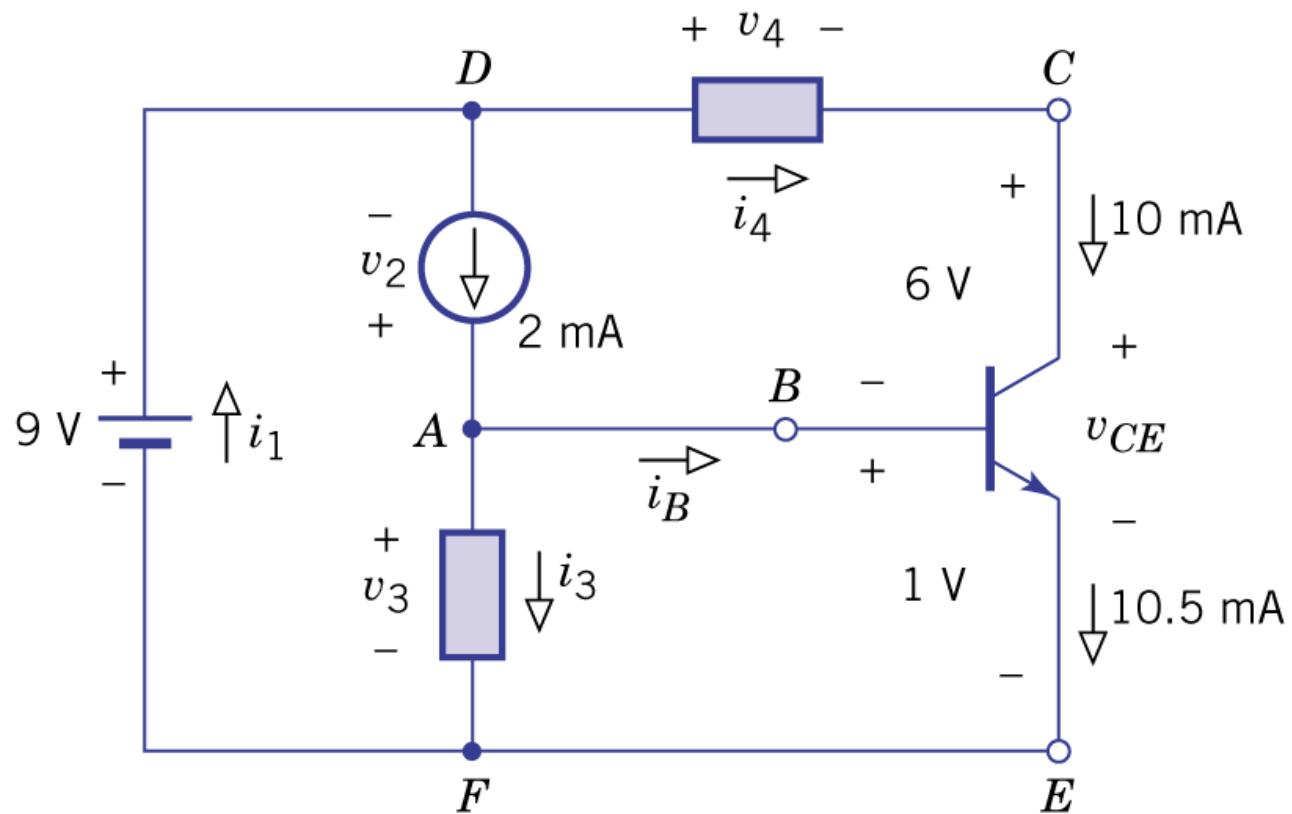Example 1.7

- Determine the remaining unknown circuit variables.



$$i_1 = 12\text{mA}$$


$$i_3 = 1.5\text{mA}$$

$$v_4 = 2\text{V}$$

$$v_2 = -8\text{V}$$

Elementary Circuit Analysis

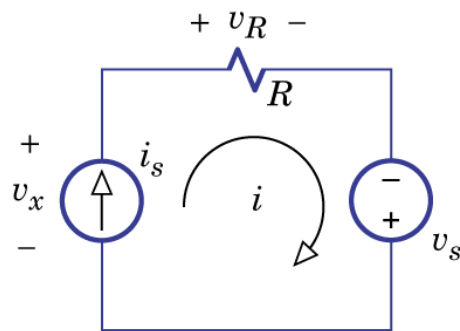
- Series
 - KCL: same loop current.
 - KVL is used for circuit analysis.



(a)

$$v_x = v_R - v_s$$


$$= Ri_s - v_s$$

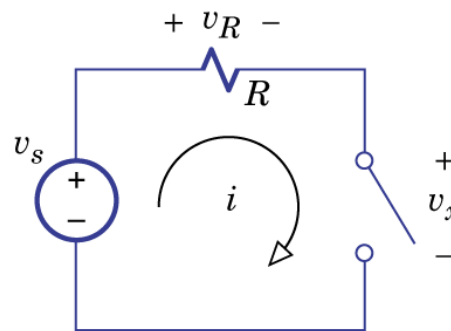

(b)

$$i = 0$$

$$v_R = 0, v_x = v_s$$

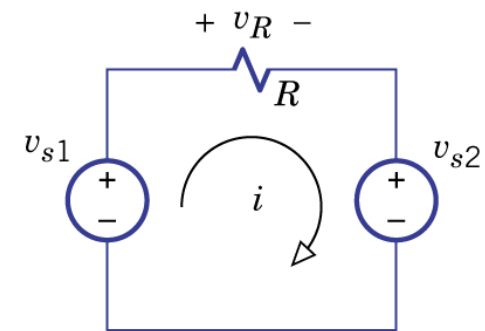


(c)

$$v_R = v_{s1} - v_{s2}$$

$$i = \frac{v_R}{R} = \frac{(v_{s1} - v_{s2})}{R}$$


Elementary Circuit Analysis

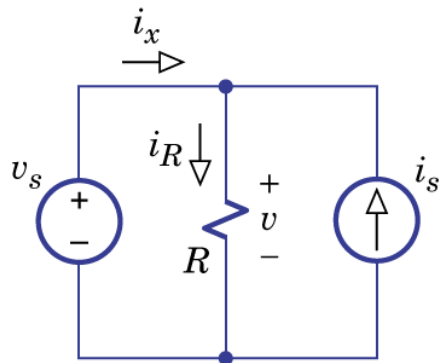- Parallel
 - KVL: same node voltage
 - KCL is used for circuit analysis




(a)
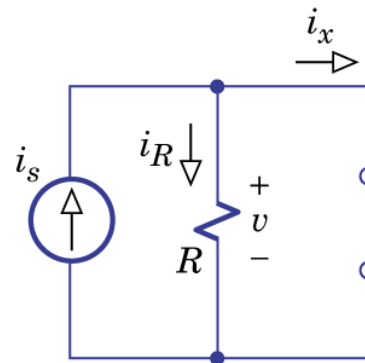
$$\begin{aligned} i_x &= i_R - i_s \\ &= Gv_s - i_s \end{aligned}$$



(b)

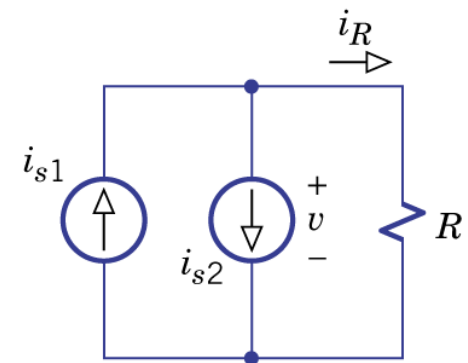
$$\begin{aligned} i_R &= 0 \\ i_x &= i_s \end{aligned}$$




(c)

$$\begin{aligned} i_R &= i_{s1} - i_{s2} \\ v &= i_R R = (i_{s1} - i_{s2})R \end{aligned}$$

Example 1.8

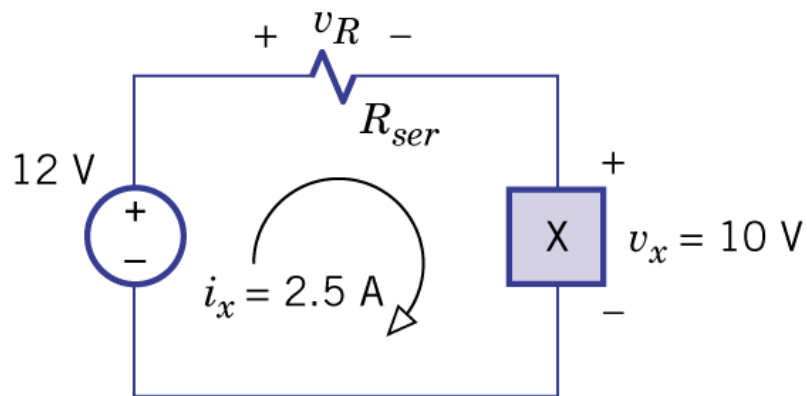

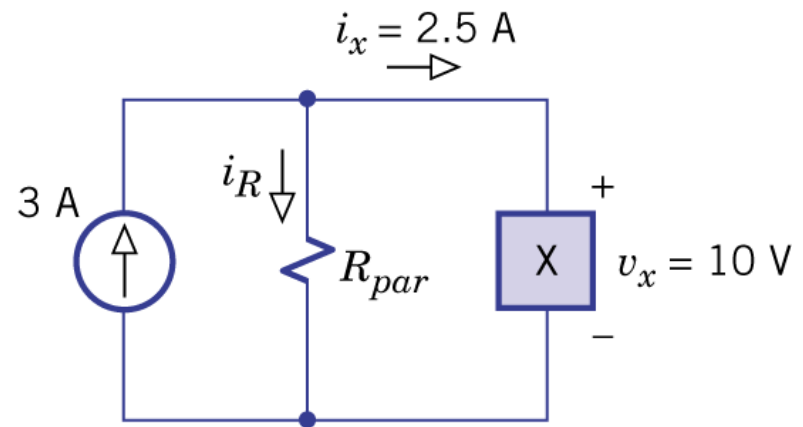(a) Electronic device with series voltage source and resistor



(b) Electronic device with parallel current source and resistor


- Operate at $v_x=10\text{V}$,
 $i_x=2.5\text{A}$
- Supplied by 12V or 3A
- A resistor is required
- Find R_{ser} and R_{par}

- $R_{ser}=(12-10)/2.5=0.8$
- $R_{par}=10/0.5=20$


Branch Variable Analysis

- Branch variable analysis: assign voltage or current associated with individual elements as immediate variables.

Example 1.9

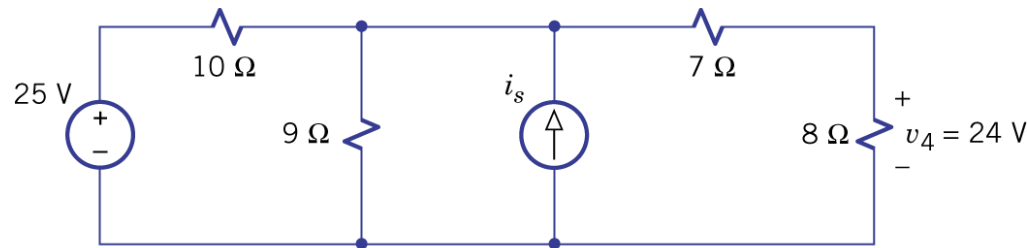


(a)

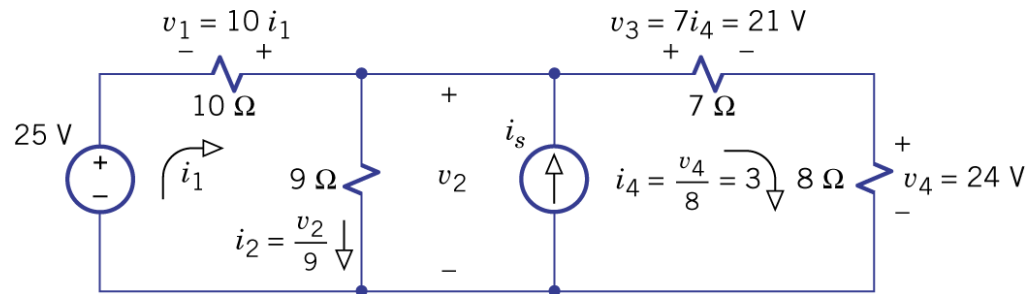

Absorbing -50W

Supplying 450W

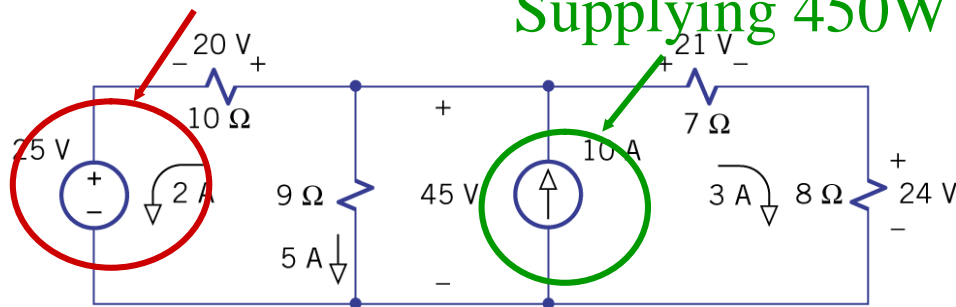

(c)


- Find i_s and the power supplied by the sources.

- $i_s = 3 + 5 + 2 = 10\text{A}$

- Total supplied power = $p_v + p_i = -50 + 450 = 400\text{W}$

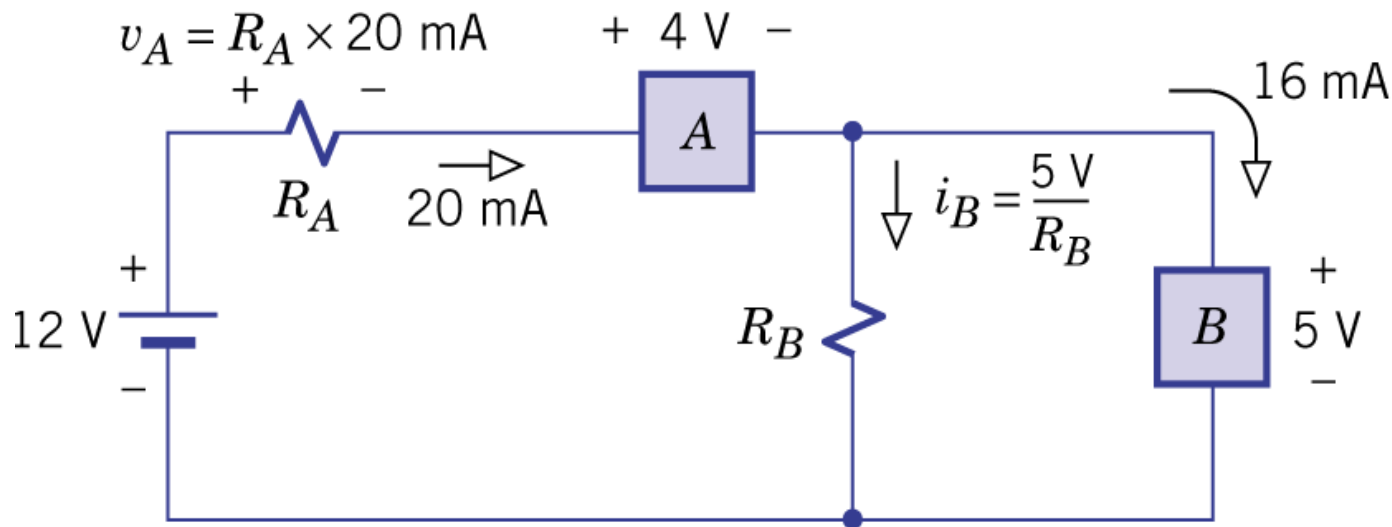Example 1.10

- Device A \rightarrow (4V, 20mA)
- Device B \rightarrow (5V, 16mA)
- Powered by a 12-V battery
- $R_A = 3V / 20mA = 150\Omega$
- $R_B = 5V / 4mA = 1.25k\Omega$



- More than one configuration.

Chapter 1: Problem Set

- 34, 37, 40, 47