

Chapter 13 Laplace Transform Analysis

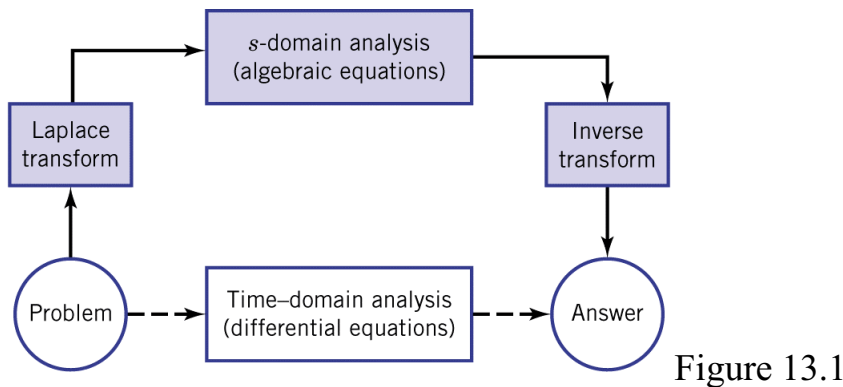


Figure 13.1

13.1 Laplace transforms

- s-domain phasor analysis: $x(t) = X_m e^{\sigma t} \cos(\omega t + \phi_x) \rightarrow$


$$\underline{X} = X_m \angle \phi_x.$$

- Laplace transform:


$$F(s) = L[f(t)] \equiv \int_0^{\infty} f(t) e^{-st} dt$$

- Three conditions:

- ✓ Unilateral (one-sided Laplace transform): Laplace transform holds for $t \geq 0$. Previous effects are included in the initial conditions at $t = 0^-$.
- ✓ Existence condition: $\lim_{t \rightarrow \infty} |f(t)| e^{-\sigma t} = 0$, $\sigma > \sigma_c$.
- ✓ The resulting transform is a function of s .

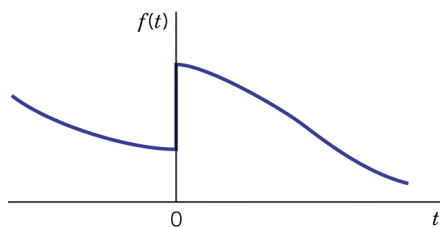

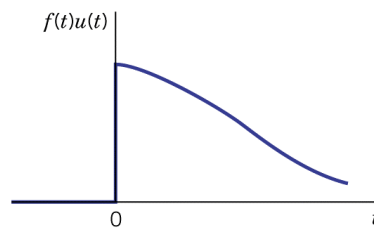(a) Waveform with discontinuity at $t = 0$



(b) One-sided waveform

Figure 13.2.

- Inverse Laplace transform for $t \geq 0$:

$$f(t) = L^{-1}[F(s)] \equiv \frac{1}{2\pi j} \int_{c-j\omega}^{c+j\omega} F(s)e^{st} ds, \quad c > \sigma_c.$$

- Inverse Laplace transform is usually done by partial fraction expansion (will be covered in section 13.2).

Example 13.1

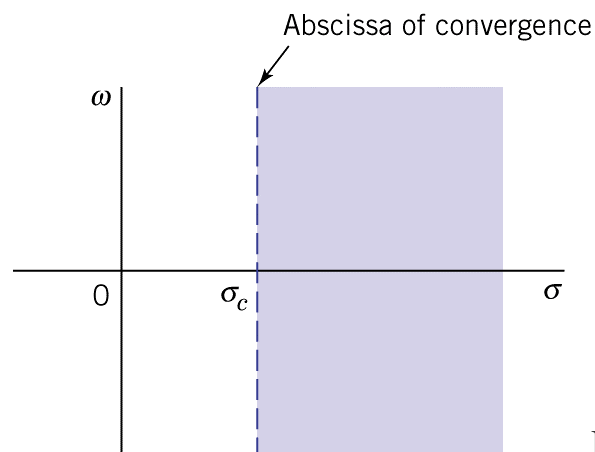


Figure 13.3.

Example 13.2

- Transform properties:
 - ✓ Linear combination:

- ✓ Multiplication by e^{-st} :

- ✓ Multiplication by t :

- ✓ Time delay:


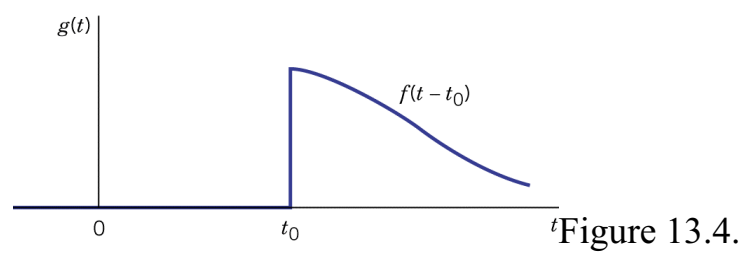



Figure 13.4.

✓ Differentiation and integration:

Example 13.3

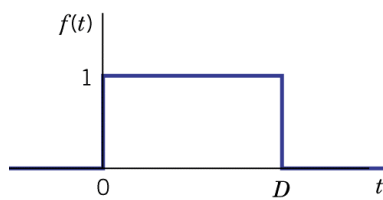

(a) Rectangular pulse

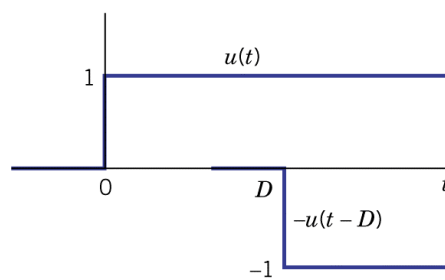

(b) Decomposition as two step functions

Figure 13.5.

Example 13.4

(Please refer to Tables 13.1 and 13.2.)

- Solution of differential equations using Laplace transform:
 - ✓ The transformation automatically incorporates the initial conditions.
 - ✓ Transformation converts linear differential equations to s -domain algebraic equations.
 - ✓ Transformation is **similar** to the s -domain phasor analysis. Denominator of the s -domain function includes the characteristic polynomial.
 - ✓ Inverse transformation is required to obtain the resultant time domain function.
 - ✓ First-order example:

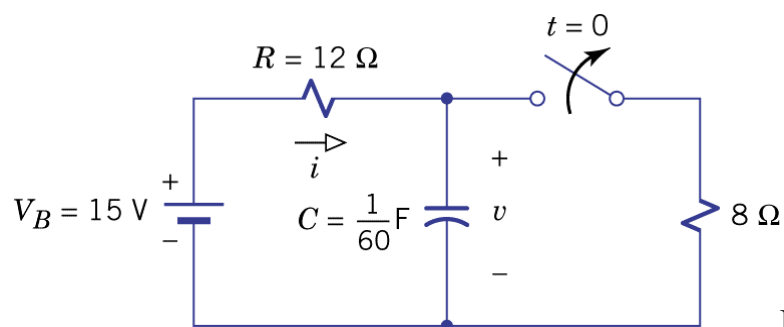


Figure 13.6.

✓ Second-order example:

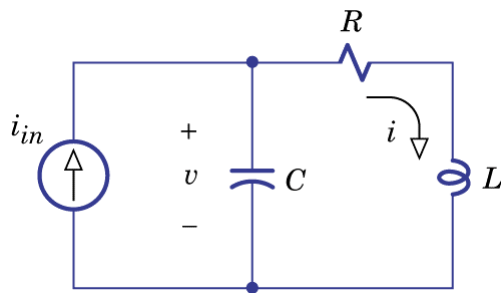


Figure 13.7.

13.2 Transform inversion

- Partial-fraction expansion of a strictly proper rational function

$$F(s) = \frac{N(s)}{D(s)} = \frac{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0}{s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}, \quad m \leq n-1.$$

- Three cases will be considered: distinct real poles, complex poles and repeated poles.
- Case 1: distinct real poles

(Heaviside's theorem, cover-up rule.)

Example 13.5: Inversion of a Third-Order Function

$$I(s) = \frac{I_1 s^2 + (R/L)I_1 s + I_2 / LC}{s[s^2 + (R/L)s + 1/LC]}$$

- Case 2: complex poles

$$D(s) = (s^2 + 2\alpha s + \omega_0^2)(s - s_3) \cdots (s - s_n)$$

Example 13.6: Inversion with Complex Poles
(method of the undetermined coefficients)

$$F(s) = \frac{15s^2 - 16s - 7}{(s + 2)(s^2 + 6s + 25)}$$

- Case 3: repeated poles

$$F(s) = G(s) + \frac{A_3}{s-s_3} + \dots + \frac{A_n}{s-s_n}$$

$$G(s) = \frac{A_{i1}}{s-s_i} + \frac{A_{i2}}{(s-s_i)^2}$$

Example 13.7: Inversion with a Triple Pole

$$F(s) = \frac{-s^2 - 2s + 14}{(s+4)^3(s+5)}$$

- Tim delay

Example 13.8: Inversion with Time Delay

- Initial-value theorem

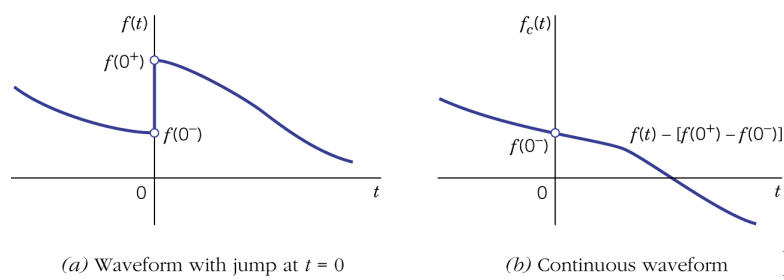


Figure 13.8.

- Final-value theorem

Example 13.9: Calculating Initial and Final Values

$$f(0^-) = 5, \quad F(s) = \frac{N(s)}{D(s)} = \frac{5s^3 - 1600}{s(s^3 + 18s^2 + 90s + 800)}$$

13.3 Transform circuit analysis

- Given a circuit with some initial state at $t = 0^-$ and an excitation $x(t)$ starting at $t = 0$, find the resulting behavior of any voltage or current $y(t)$ for $t \geq 0$.
- Zero-state response, natural response, forced response, zero-input response and complete response.
- Zero-state response: a circuit with no stored energy at $t = 0^-$.


- Step response:

$$x(t) = u(t) = 1, \quad t > 0$$


$$X(s) = 1/s$$

$$Y(s) = H(s) \times \frac{1}{s} = \frac{N_H(s)}{sP(s)}$$

Example 13.10: Step Response

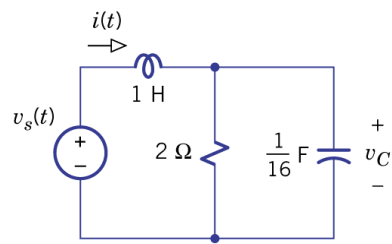

(a) Circuit for Example 13.10

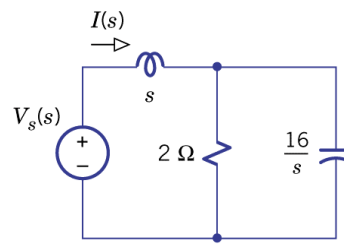

(b) *s*-domain diagram **Figure 13.9.**

- Zero-state AC response:

$$x(t) = X_m \cos(\beta t + \phi_x)$$

$$D_X(s) = s^2 + \beta^2$$

Example 13.11: Zero-State AC Response

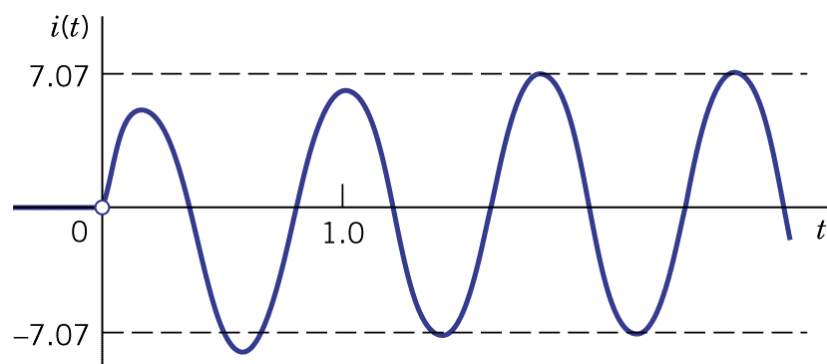


Figure 13.10.

- Natural response and forced response:

- Zero-input response: the excitation equals zero for $t \geq 0$ but the circuit contains stored energy at $t = 0^-$.

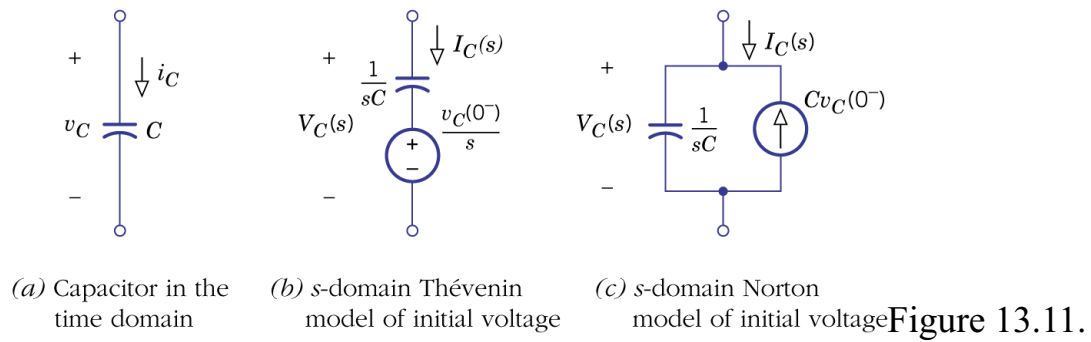


Figure 13.11.

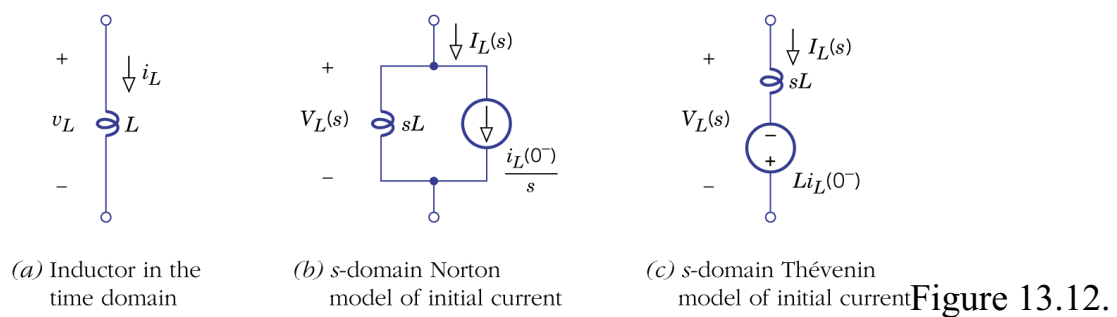


Figure 13.12.

Example 13.12: Calculating a Zero-Input Response

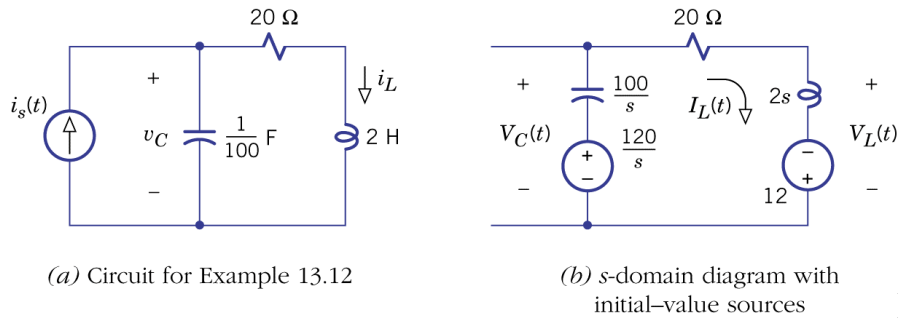


Figure 13.13.

- Complete response: complete response = zero-input response + zero-state response.

Example 13.13: Calculating a Complete Response

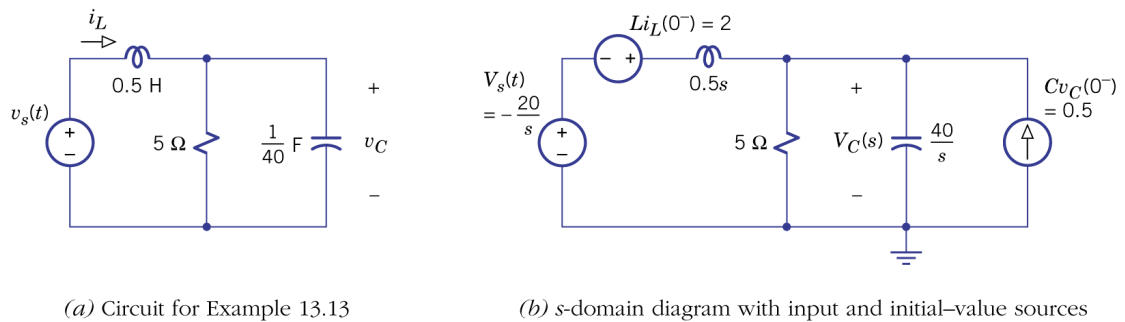


Figure 13.14.


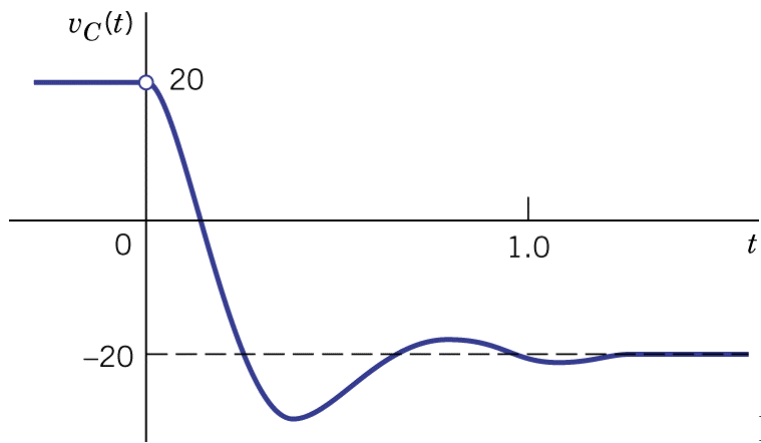


Figure 13.15.

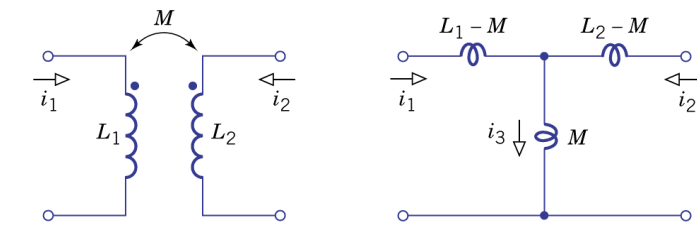13.4 Transform analysis with mutual inductance



(a) Magnetically coupled coils

(b) Tee model

Figure 13.16.



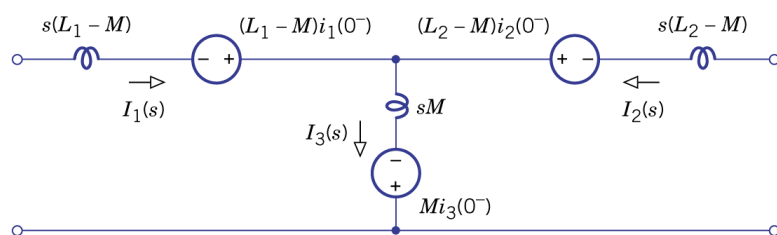


Figure 13.17.

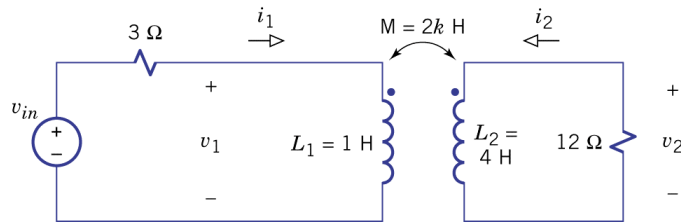
Example 13.14: Complete Response of a Transformer Circuit



(a) Transformer circuit

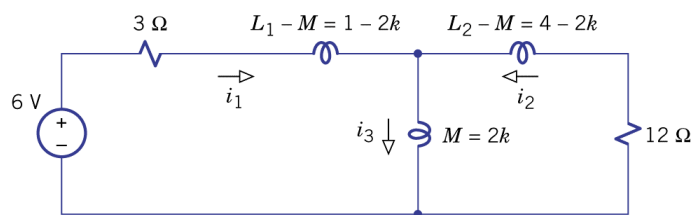


(b) Diagram with tee model for $t < 0$

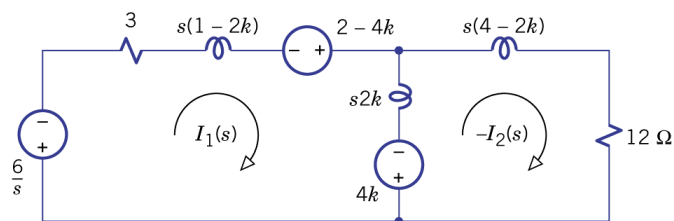


(c) s -domain diagram for $t \geq 0$ with input and initial-value sources **Figure 13.18.**

13.5 Impulses and convolution


- Impulses:

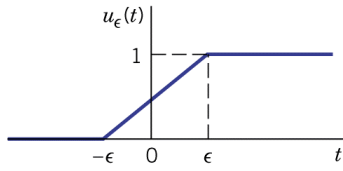


(a) Approximation of the unit step

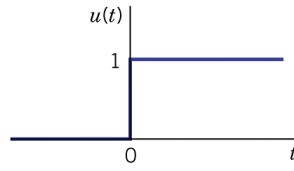

(b) Unit step function

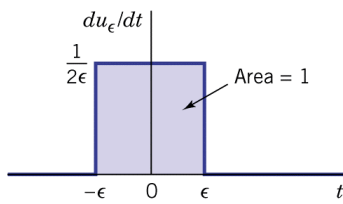

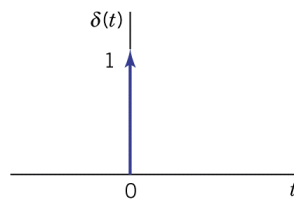(c) Approximation of the derivative of the unit step



(d) Unit impulse

Figure 13.18.


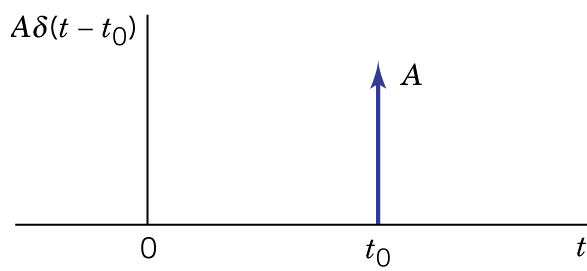



Figure 13.20.

- Sampling process:

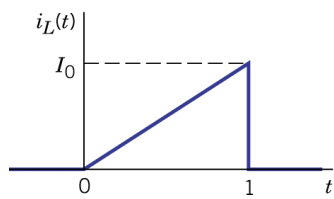Example 13.15: Discontinuous Inductor Current



(a) Inductor current waveform

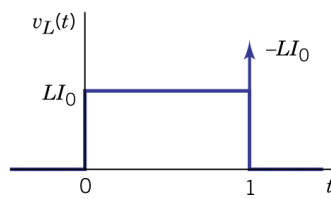

(b) Voltage waveform with an impulse

Figure 13.21.

- Transform with impulses

$$L[\delta(t)] = \int_{0^-}^{\infty} \delta(t) e^{-st} dt = e^{-st} \Big|_{t=0} = 1.$$

- As an example, the inverse transform of $\frac{3s}{s+2}$ is

- In general, the inverse of $F(s)$

$$F(s) = \frac{N(s)}{D(s)} = \frac{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0}{s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}$$

Example 13.16: Impulsive Zero-State Response

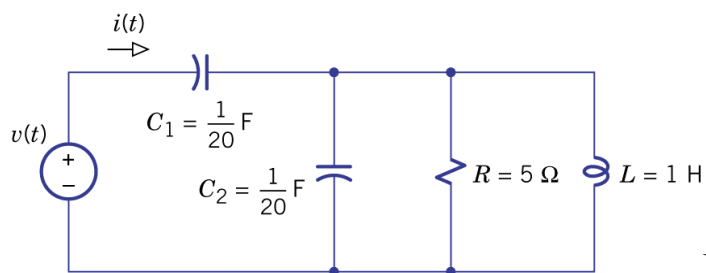



Figure 13.22.

- Convolution and impulse response.
- The convolution of $f(t)$ and $g(t)$:


$$f(t) * g(t) \equiv \int_{-\infty}^{\infty} f(\lambda)g(t - \lambda)d\lambda .$$

- Commutative property ($f(t) * g(t) \equiv g(t) * f(t)$):
- Distributive property ($f(t) * [g_1(t) + g_2(t)] \equiv [f(t) * g_1(t)] + [f(t) * g_2(t)]$):
- Replication property ($f(t) * \delta(t) \equiv f(t)$):


- Graphical interpretation:

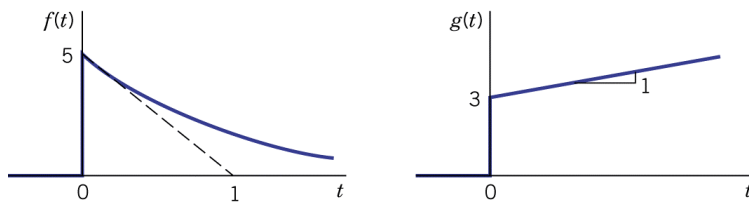

(a) Waveforms of $f(t)$ and $g(t)$

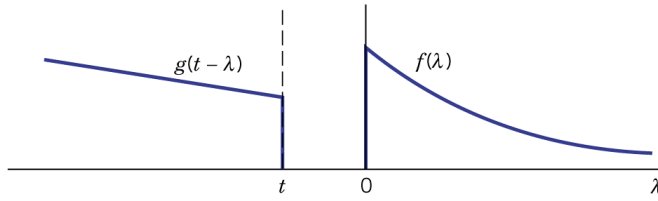

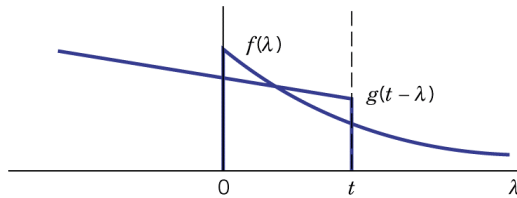(b) $f(\lambda)$ and $g(t-\lambda)$ with $t < 0$



(c) $f(\lambda)$ and $g(t-\lambda)$ with $t > 0$

Figure 13.23.

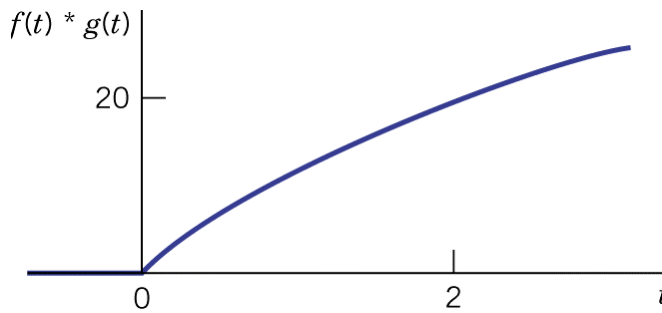



Figure 13.24.

- Convolution of two causal functions produces another causal function.


- Laplace transform of the convolution of causal functions:

$$L[f(t) * g(t)] = F(s)G(s)$$

$$L^{-1}[F(s)G(s)] = f(t) * g(t)$$

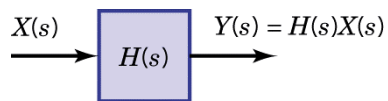


(a) s-domain block diagram

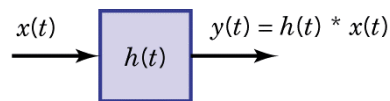

(b) Time-domain block diagram

Figure 13.25.

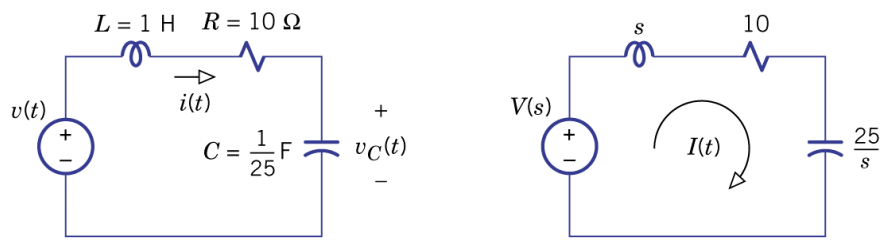
Example 13.17: Impulse Response and Pulse Response




(a) Circuit for Example 13.17

(b) s -domain diagram


Figure 13.26.

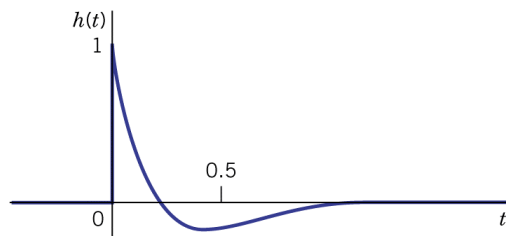


(a) Impulse response

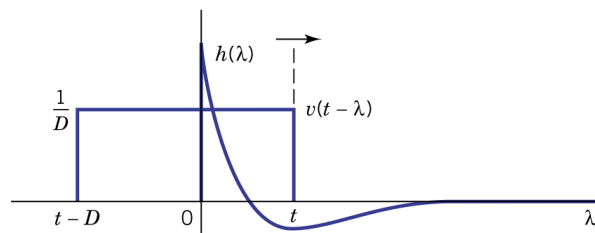

(b) Convolution with rectangular pulse

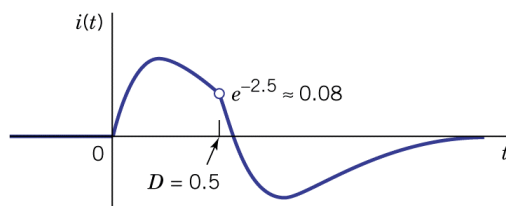

(c) Pulse response with $D = 0.5$

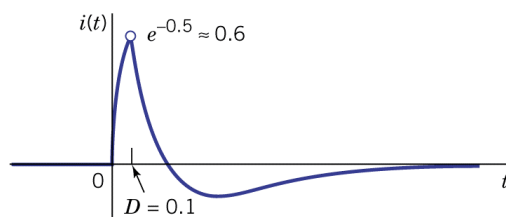

(d) Pulse response with $D = 0.1$

Figure 13.27.