

Chapter 14 Two-Port Networks

14.1 Two-ports and impedance parameters

- Two-port networks:

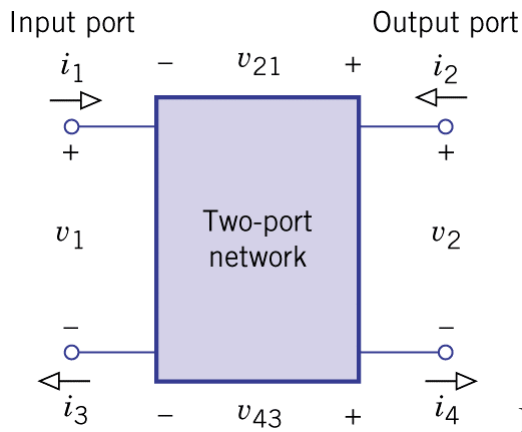


Figure 14.1.

- It is assumed that a two-port network contains no independent sources but may include controlled sources.


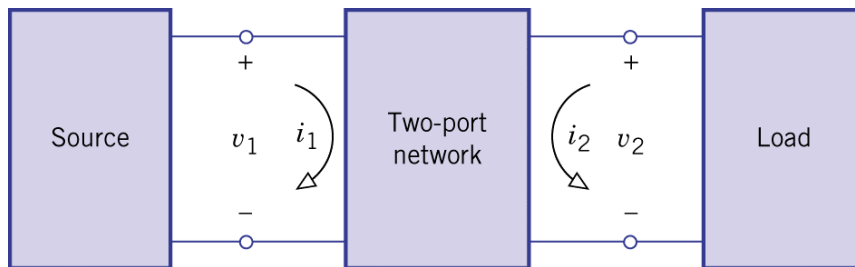


Figure 14.2.

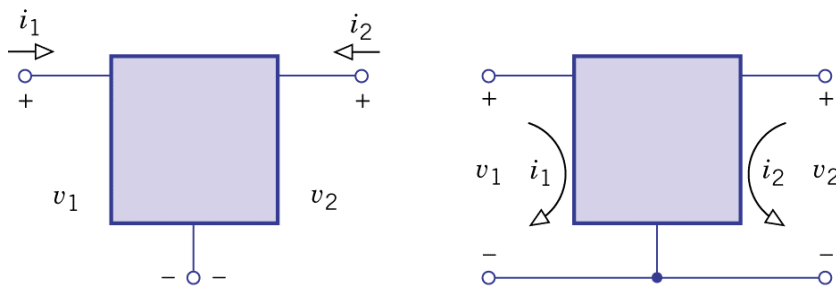- Three-terminal networks (with a common ground):



(a) Three-terminal network

(b) Two-port with common ground

Figure 14.3.

- Two-port in the s -domain:

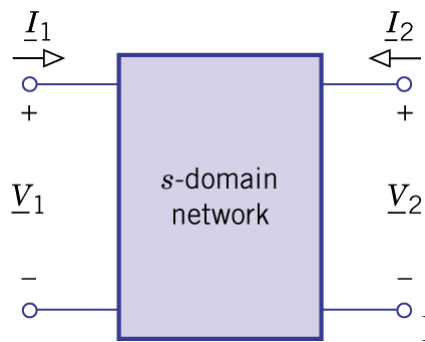


Figure 14.4.

- Impedance parameters: common ground two-port with current sources.


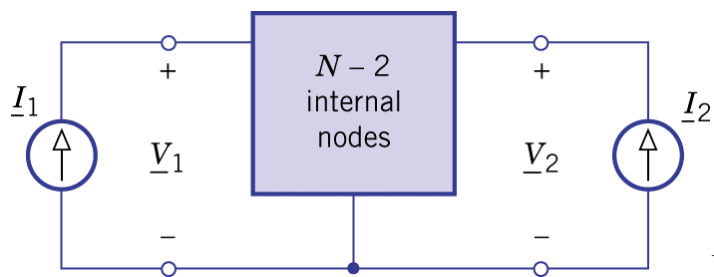


Figure 14.5.

$$\begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix}$$

- Open circuit impedance parameters:
- $z_{11} = \underline{V}_1 / \underline{I}_1 | \underline{I}_2 = 0$: input impedance with open output.
- $z_{12} = \underline{V}_1 / \underline{I}_2 | \underline{I}_1 = 0$: reverse transfer impedance with open output.
- $z_{21} = \underline{V}_2 / \underline{I}_1 | \underline{I}_2 = 0$: forward transfer impedance with open output.
- $z_{22} = \underline{V}_2 / \underline{I}_2 | \underline{I}_1 = 0$: output impedance with open input.

- Equivalent s -domain diagram:

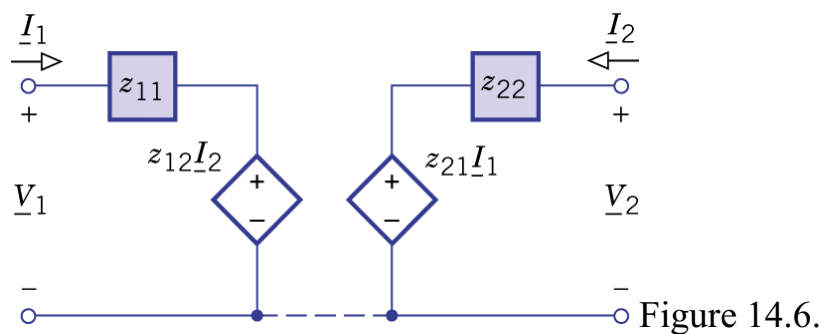

- Indirect method for finding z parameters: Treat \underline{I}_1 and \underline{I}_2 as source currents and use standard analysis techniques.
- Direct method for finding z parameters: open circuit techniques.
- Existence test: independent current sources may be connected to the input and output ports without violating KCL.

Example 14.1: z Parameters by the Indirect Method



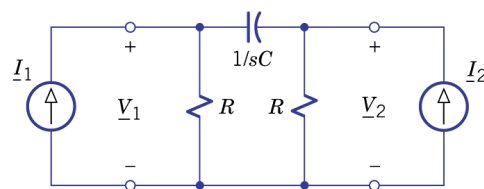
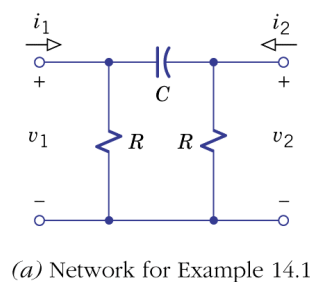


Figure 14.7.

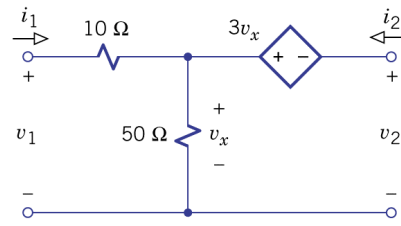
Example 14.2: z Parameters by the Direct Method



(a) Network for Example 14.2

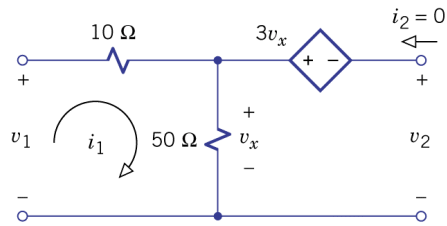


(b) Open-output diagram

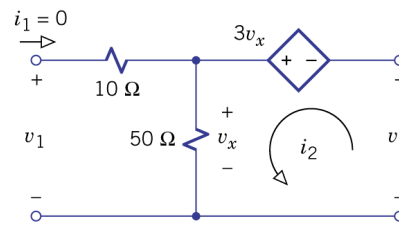


(c) Open-input diagram

Figure 14.8.

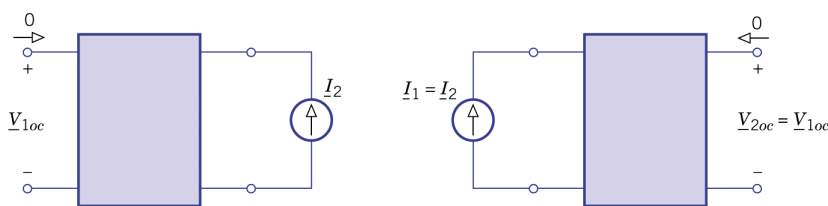- Reciprocal networks: $z_{12} = z_{21}$.
- Reciprocal theorem:




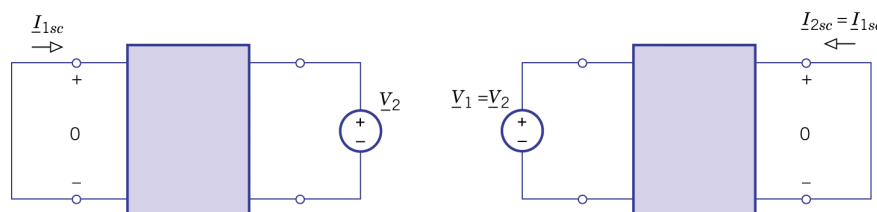(a) Interchanging open circuit and current source




(b) Interchanging short circuit and voltage source

Figure 14.10.

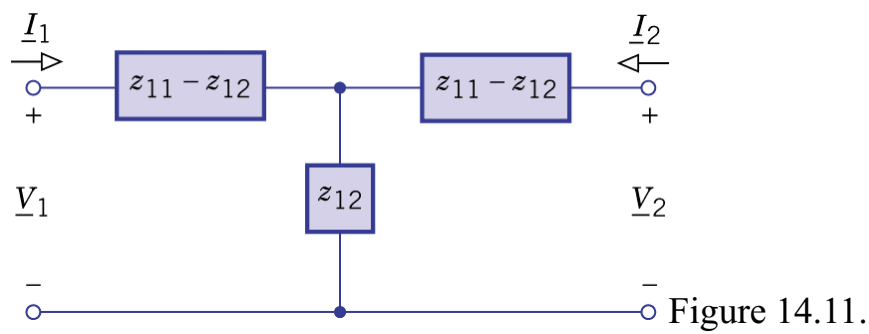

- A linear circuit that contains no controlled sources will be reciprocal.

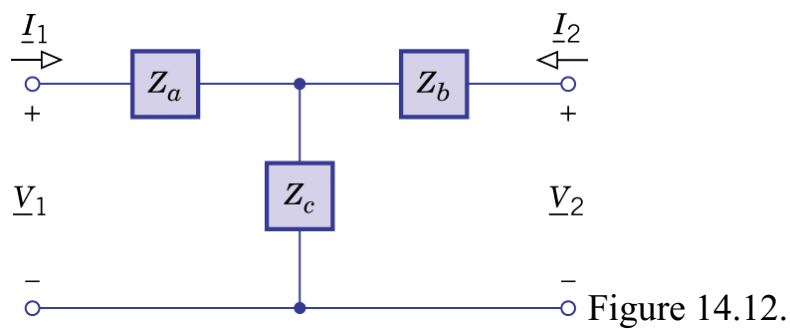Example 14.3: z Parameters of a Tee Network




14.2 Admittance, hybrid, and transmission parameters,


- Admittance parameters (y parameters): dual of the impedance parameters.

$$\begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix}$$

- Short circuit admittance parameters:
- $y_{11} = \underline{I}_1 / \underline{V}_1 | \underline{V}_2 = 0$: input admittance with shorted output.
- $y_{12} = \underline{I}_1 / \underline{V}_2 | \underline{V}_1 = 0$: reverse transfer admittance with shorted output.
- $y_{21} = \underline{I}_2 / \underline{V}_1 | \underline{V}_2 = 0$: forward transfer admittance with shorted output.
- $y_{22} = \underline{I}_2 / \underline{V}_2 | \underline{V}_1 = 0$: output admittance with shorted input.
- Existence test: independent current sources may be connected to the input and output ports without violating KVL.

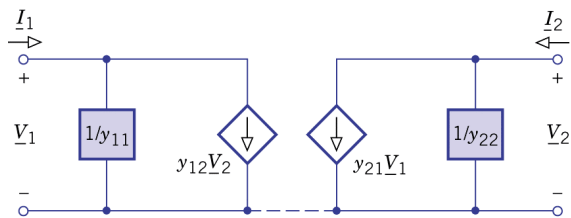

(a) y -parameter model

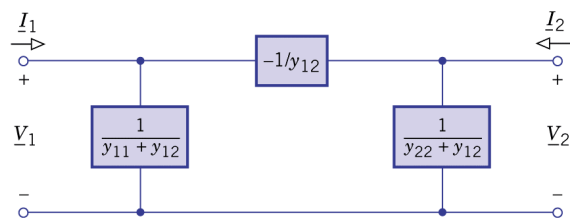


(b) Tee model for reciprocal two-port


Figure 14.14.

- The y parameters can be found by the indirect and the direct method.

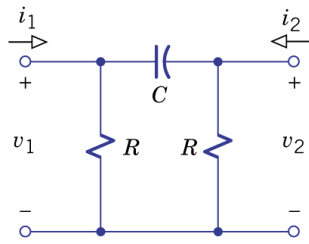Example 14.4 y Parameters by the Indirect Method




(a) Network for Example 14.4

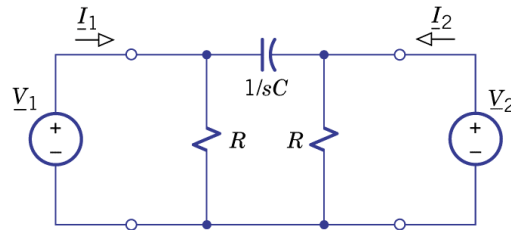


(b) s -domain diagram with voltage sources **Figure 14.15**

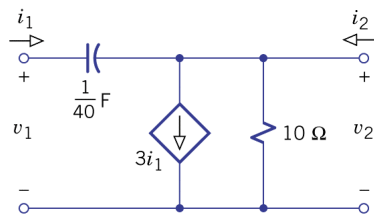
Example 14.5 y Parameters by the Direct Method



(a) Network for Example 14.5

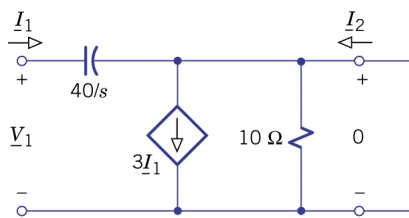

(b) Shorted-output diagram

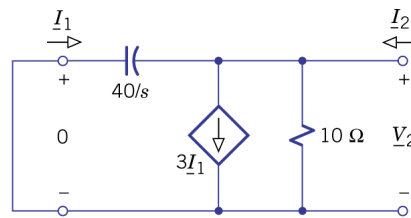


(c) Shorted-input diagram

Figure 14.16


- Hybrid parameters (h parameters):

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

- Hybrid parameters:
- $h_{11} = \underline{V}_1 / \underline{I}_1 | \underline{V}_2 = 0$: input impedance with shorted output.
- $h_{12} = \underline{V}_1 / \underline{V}_2 | \underline{I}_1 = 0$: reverse voltage ratio with open input.
- $h_{21} = \underline{I}_2 / \underline{I}_1 | \underline{V}_2 = 0$: forward current ratio with shorted output.
- $h_{22} = \underline{I}_2 / \underline{V}_2 | \underline{I}_1 = 0$: output admittance with open input.
- Existence test: an independent current sources may be connected to the input port and an independent voltage source may be connected to the output port without violating KCL and KVL.

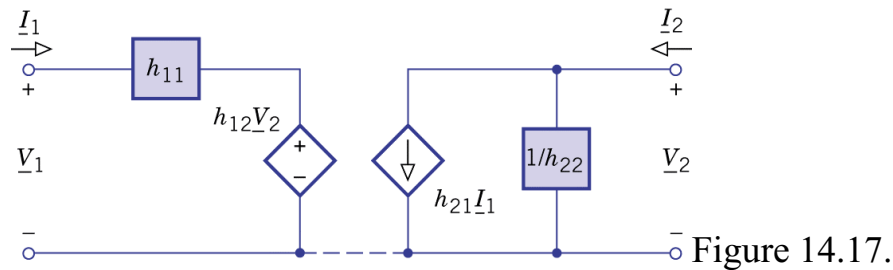

Example 14.6 Calculating h parameters

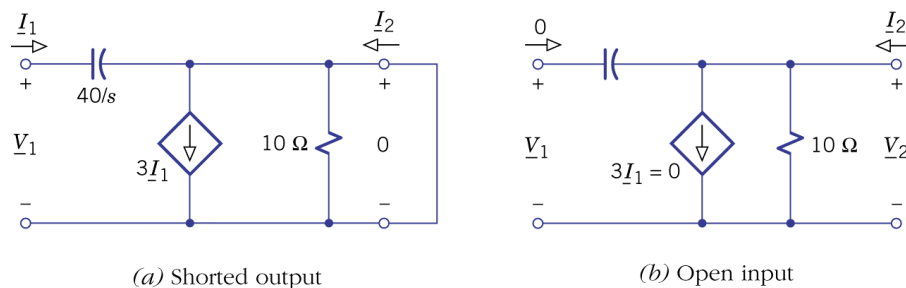

- Transmission parameters ($ABCD$ parameters):

$$\begin{bmatrix} \underline{V}_1 \\ \underline{I}_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} \underline{V}_2 \\ -\underline{I}_2 \end{bmatrix}$$

- Transmission parameters:
- $A = \underline{V}_1 / \underline{V}_2 | \underline{I}_2 = 0$.

- $B = -\underline{V}_1 / \underline{I}_2 | \underline{V}_2 = 0$.
- $C = \underline{I}_1 / \underline{V}_2 | \underline{I}_2 = 0$.
- $D = -\underline{I}_1 / \underline{I}_2 | \underline{V}_2 = 0$.
- A : reverse voltage ratio with open output.
- $-B$: reverse transfer impedance with shorted output.
- C : reverse transfer admittance with open output.
- $-D$: reverse current ratio with shorted output.
- Existence test: the $ABCD$ parameters exist only if $\underline{V}_{2oc} \neq 0$ and $\underline{I}_{2sc} \neq 0$.

Example 14.7 Calculating $ABCD$ Parameters

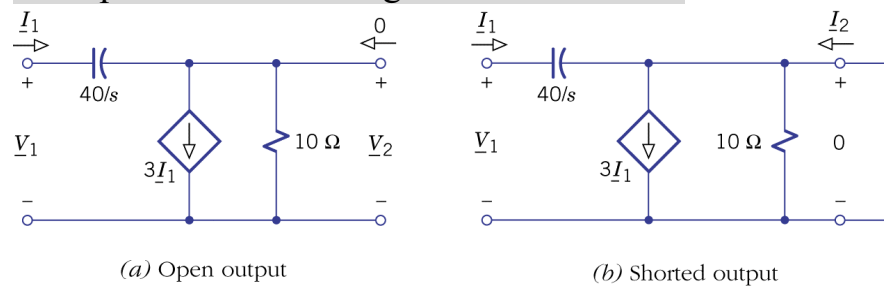


Figure 14.19.


- Parameter conversion: with one set of parameters for a particular two-port, other sets of parameters can be obtained if they exist.

(Table 14.1 Two-port equations)

- The conversion between z and y can be done by matrix inversion.
- Conversions involving hybrid or transmission parameters need to be done by algebraic manipulation.

(Table 14.2 Parameter conversions)

Example 14.8 Parameters of a Tee Network

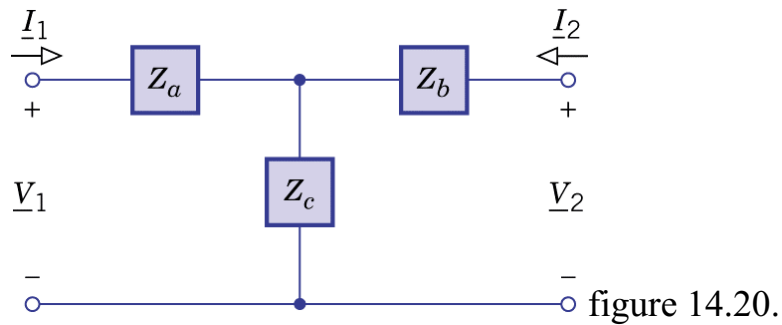

14.3 Circuit analysis with two-ports

- Terminated two-ports: A two-port is terminated with a source and a load. The source may be replaced by a Thevenin or Norton model and the load may be replaced by an equivalent impedance.
- Typical network functions:
 - ✓ Voltage transfer function: $H_v(s) \equiv \underline{V}_2 / \underline{V}_1$.
 - ✓ Current transfer function: $H_i(s) \equiv \underline{I}_2 / \underline{I}_1$.

✓ Equivalent input impedance: $Z_i(s) \equiv \underline{V}_1 / \underline{I}_1$.

✓ Equivalent output impedance: $Z_o(s) \equiv \underline{V}_2 / \underline{I}_2 \Big|_{\underline{V}_s = 0}$.

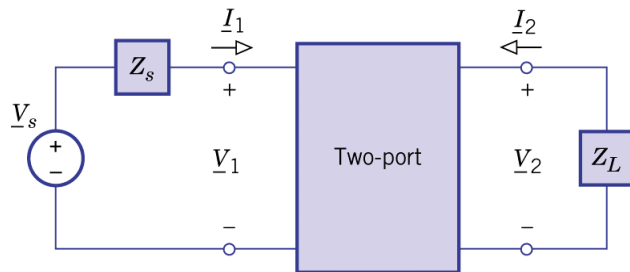


Figure 14.21.

(Table 14.3 Relations for Terminated Two-Ports)

Example 14.9 Calculating a Transfer Function

Example 14.10 A Mid-Frequency Transistor Amplifier

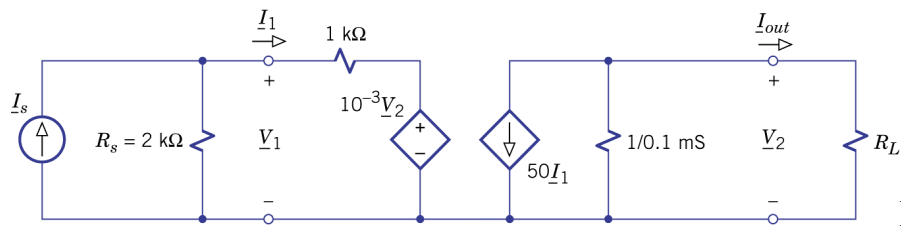


Figure 14.22.

- Interconnected two-ports (assuming the interconnection does not change the properties of individual two-ports).
- Cascade connection:

$$\underline{V}_{1b} = \underline{V}_{2a}, \quad \underline{I}_{1b} = -\underline{I}_{2a}.$$

$$[T]_{cas} = [T]_a [T]_b.$$

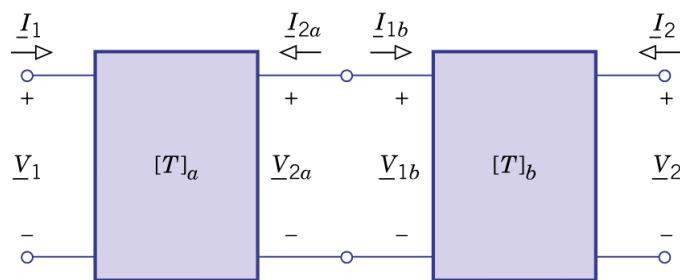


Figure 14.24.

Example 14.11 A Cascade Amplifier


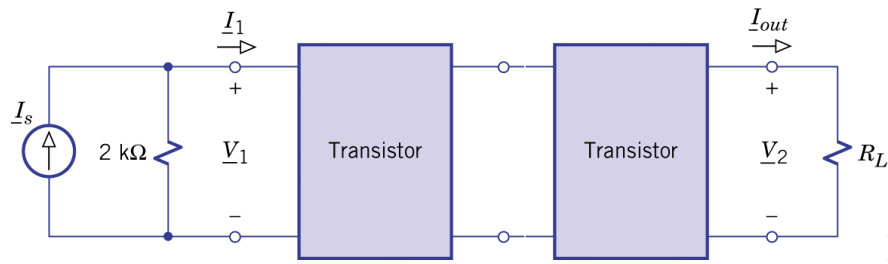


Figure 14.25.

- Series and parallel connections

$$[z]_{ser} = [z]_a + [z]_b$$

$$[y]_{par} = [y]_a + [y]_b$$

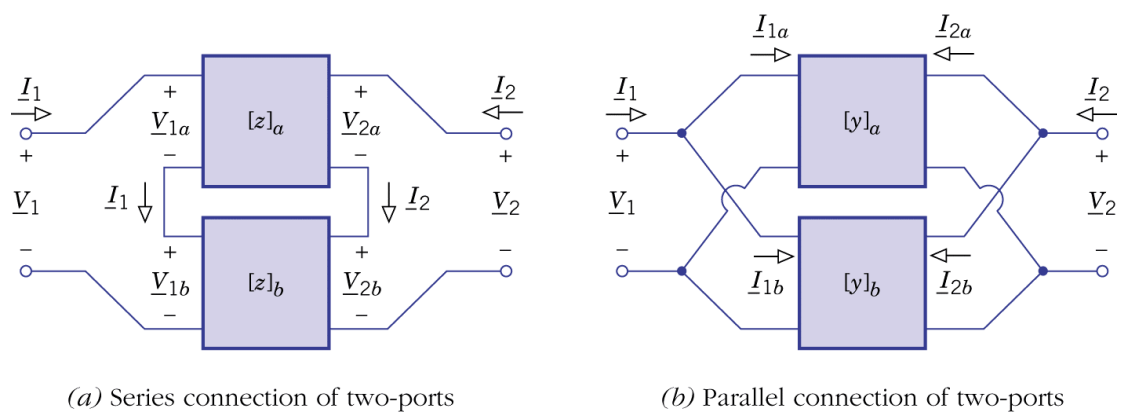

(a) Series connection of two-ports

(b) Parallel connection of two-ports

Figure 14.26.

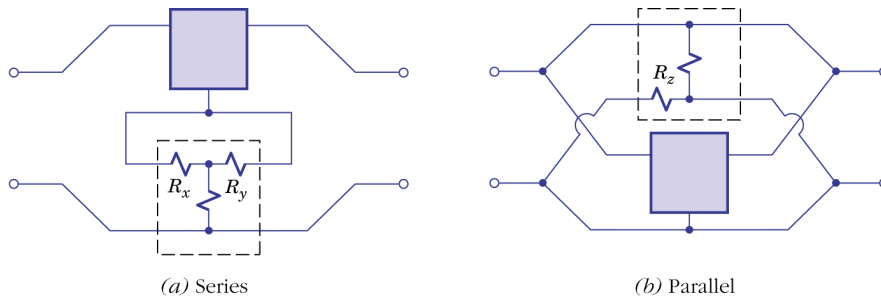


Figure 14.27.


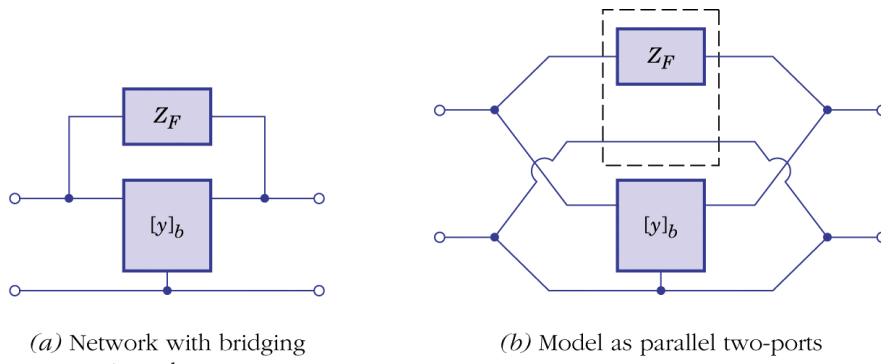


Figure 14.28.

Example 14.12 A High-Frequency Amplifier

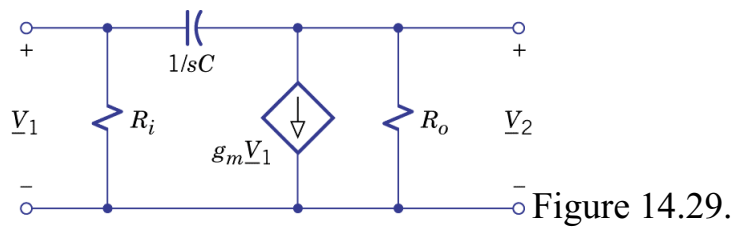

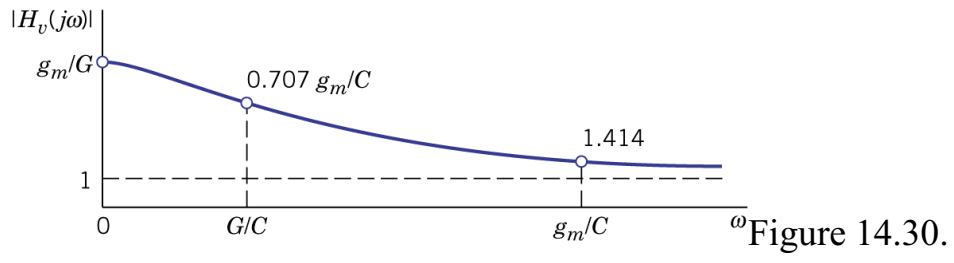


Figure 14.30.