

# Chapter 5


## Steady-State Sinusoidal Analysis

# Chapter 5

## Steady-State Sinusoidal Analysis

1. Identify the frequency, angular frequency, peak value, rms value, and phase of a sinusoidal signal.
2. Solve steady-state ac circuits using phasors and complex impedances.

3. Compute power for steady-state ac circuits.
4. Find Thévenin and Norton equivalent circuits.
5. Determine load impedances for maximum power transfer.
6. Solve balanced three-phase circuits.

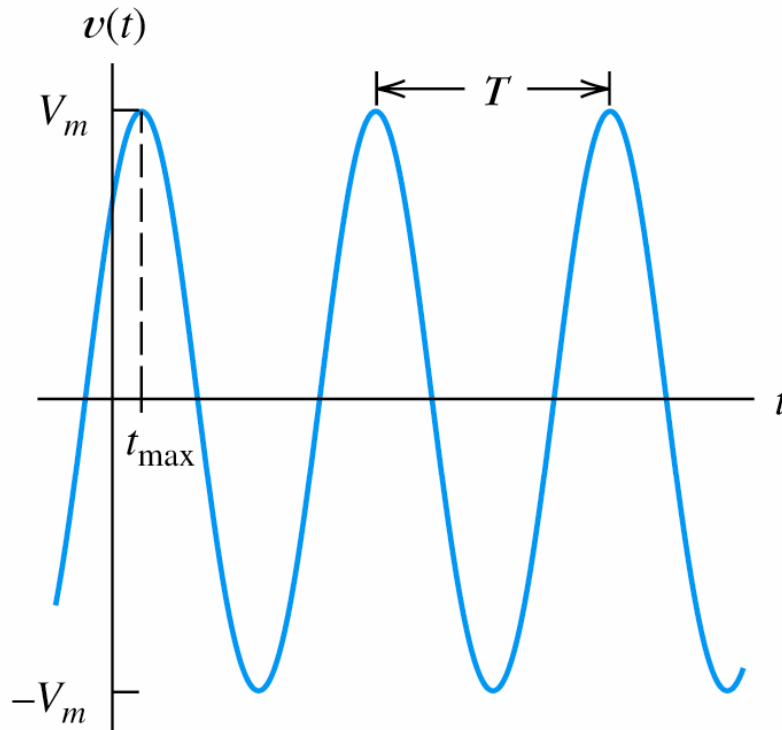

**Figure 5.1** A sinusoidal voltage waveform given by  $v(t) = V_m \cos(\omega t + \theta)$ .

Note: Assuming that  $\theta$  is in degrees, we have  $t_{\max} = \frac{-\theta}{360} \times T$ .

For the waveform shown,  $\theta$  is  $-45^\circ$ .

# SINUSOIDAL CURRENTS AND VOLTAGES

$V_m$  is the **peak value**

$\omega$  is the **angular frequency** in radians  
per second

$\theta$  is the **phase angle**

$T$  is the **period**

**Frequency**

$$f = \frac{1}{T}$$

**Angular frequency**

$$\omega = \frac{2\pi}{T}$$

$$\omega = 2\pi f$$

$$\sin(z) = \cos(z - 90^\circ)$$

# Root-Mean-Square Values

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \quad I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$P_{\text{avg}} = \frac{V_{\text{rms}}^2}{R}$$


$$P_{\text{avg}} = I_{\text{rms}}^2 R$$
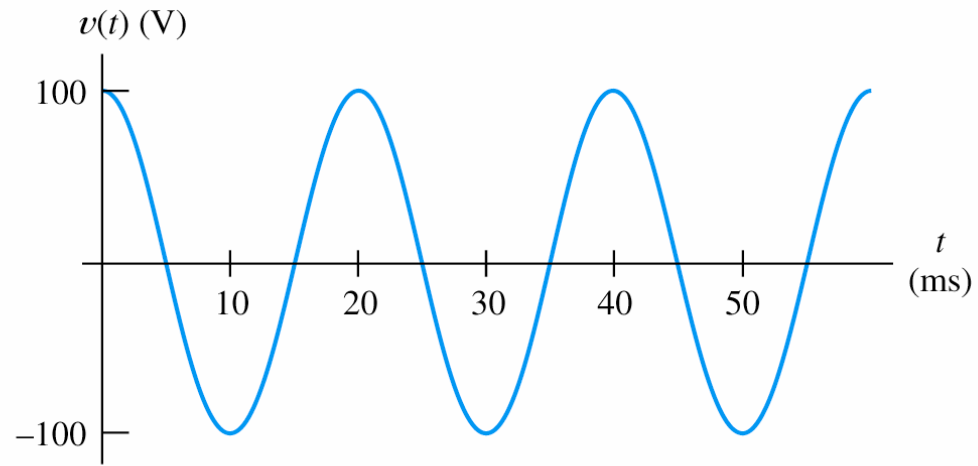
# RMS Value of a Sinusoid


$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

The rms value for a sinusoid is the peak value divided by the square root of two. This is not true for other periodic waveforms such as square waves or triangular waves.





(a)

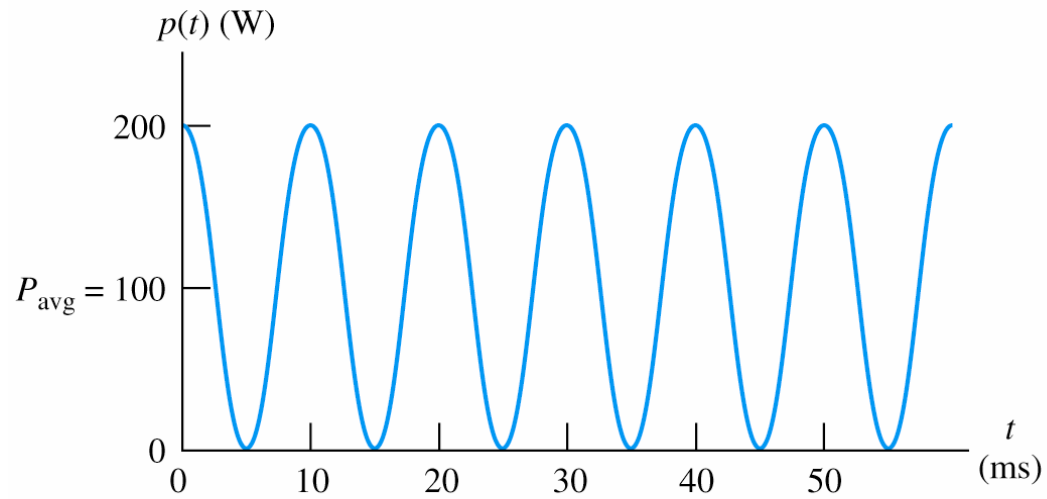

(b)

**Figure 5.2** Voltage and power versus time for Example 5.1.

# Phasor Definition

Time function :  $v_1(t) = V_1 \cos(\omega t + \theta_1)$

Phasor :  $\mathbf{V}_1 = V_1 \angle \theta_1$

# Adding Sinusoids Using Phasors

Step 1: Determine the phasor for each term.

Step 2: Add the phasors using complex arithmetic.

Step 3: Convert the sum to polar form.

Step 4: Write the result as a time function.

# Using Phasors to Add Sinusoids

$$v_1(t) = 20 \cos(\omega t - 45^\circ)$$


$$v_2(t) = 10 \cos(\omega t + 60^\circ)$$

$$\mathbf{V}_1 = 20 \angle -45^\circ$$

$$\mathbf{V}_2 = 10 \angle -30^\circ$$

$$\begin{aligned}\mathbf{V}_s &= \mathbf{V}_1 + \mathbf{V}_2 \\ &= 20\angle -45^\circ + 10\angle -30^\circ \\ &= 14.14 - j14.14 + 8.660 - j5 \\ &= 23.06 - j19.14 \\ &= 29.97\angle -39.7^\circ\end{aligned}$$

$$v_s(t) = 29.97 \cos(\omega t - 39.7^\circ)$$

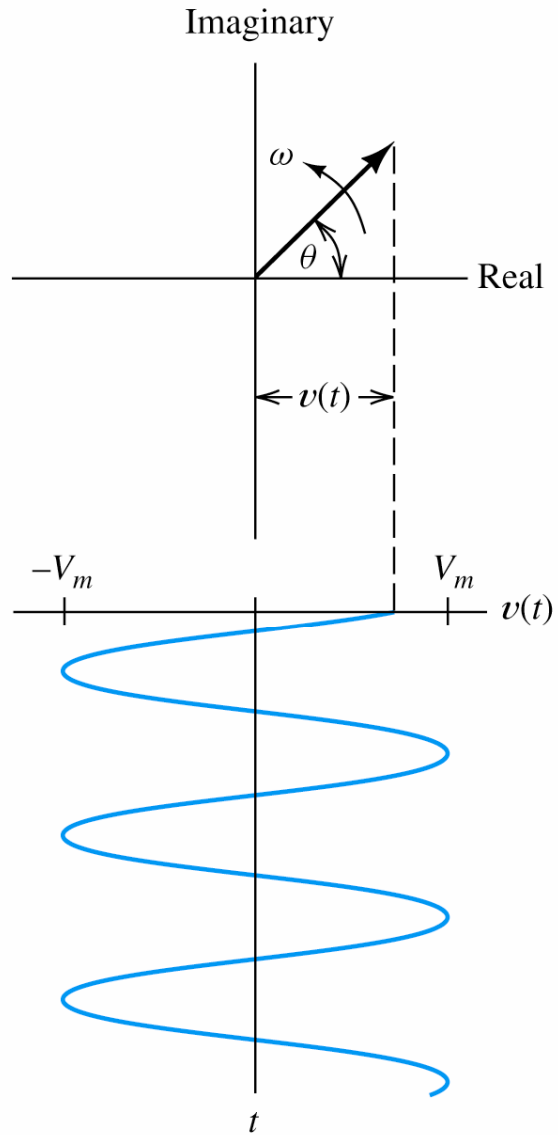

**Figure 5.4** A sinusoid can be represented as the real part of a vector rotating counterclockwise in the complex plane.

Sinusoids can be visualized as the real-axis projection of vectors rotating in the complex plane. The phasor for a sinusoid is a snapshot of the corresponding rotating vector at  $t = 0$ .


# Phase Relationships

To determine phase relationships from a phasor diagram, consider the phasors to rotate counterclockwise. Then when standing at a fixed point, if  $\mathbf{V}_1$  arrives first followed by  $\mathbf{V}_2$  after a rotation of  $\theta$ , we say that  $\mathbf{V}_1$  leads  $\mathbf{V}_2$  by  $\theta$ . Alternatively, we could say that  $\mathbf{V}_2$  lags  $\mathbf{V}_1$  by  $\theta$ . (Usually, we take  $\theta$  as the smaller angle between the two phasors.)




To determine phase relationships between sinusoids from their plots versus time, find the shortest time interval  $t_p$  between positive peaks of the two waveforms. Then, the phase angle is


$\theta = (t_p/T) \times 360^\circ$ . If the peak of  $v_1(t)$  occurs first, we say that  $v_1(t)$  leads  $v_2(t)$  or that  $v_2(t)$  lags  $v_1(t)$ .

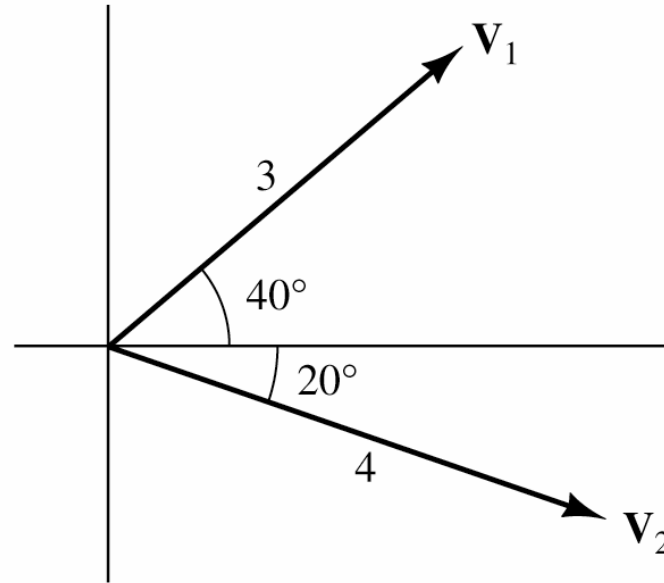


**Figure 5.5** Because the vectors rotate counterclockwise,  $v_1$  leads  $v_2$  by  $60^\circ$  (or, equivalently,  $v_2$  lags  $v_1$  by  $60^\circ$ .)

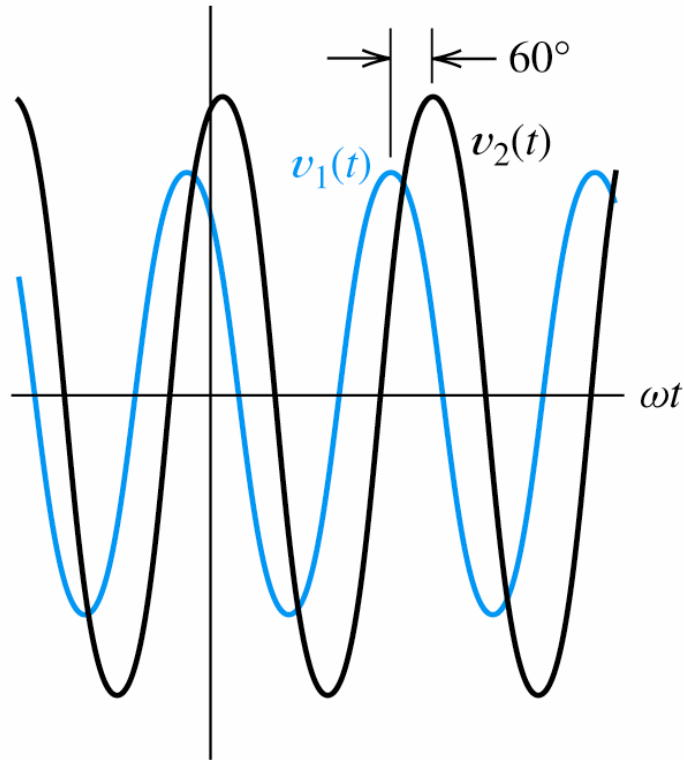

**Figure 5.6** The peaks of  $v_1(t)$  occur  $60^\circ$  before the peaks of  $v_2(t)$ . In other words,  $v_1(t)$  leads  $v_2(t)$  by  $60^\circ$ .

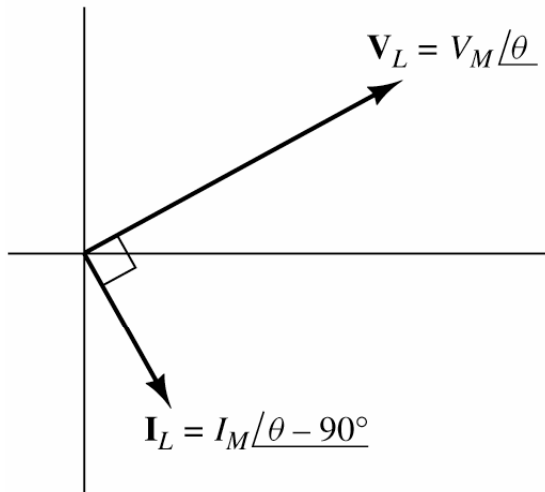

(a) Phasor diagram

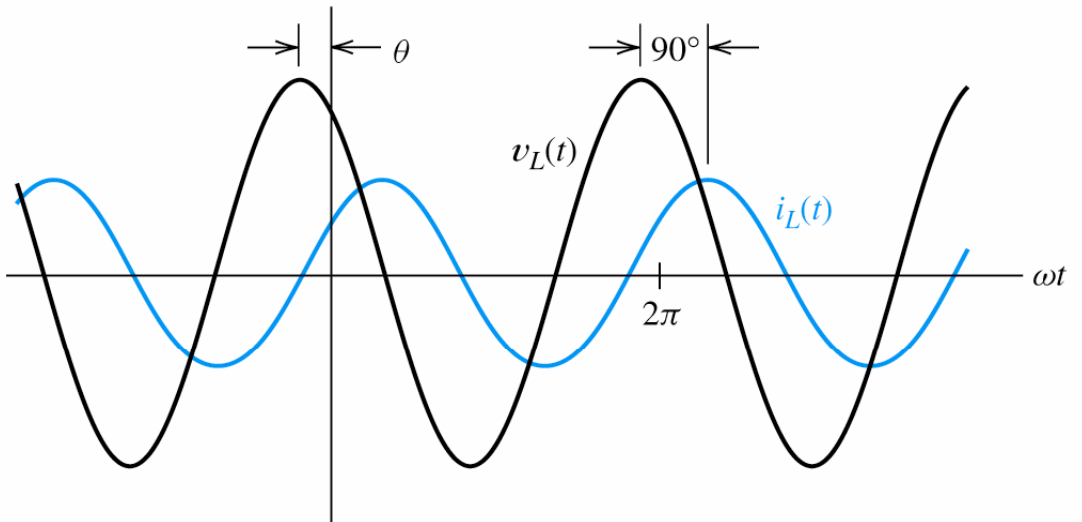

(b) Current and voltage versus time


**Figure 5.7** Current lags voltage by  $90^\circ$  in a pure inductance.

# COMPLEX IMPEDANCES


$$\mathbf{V}_L = j\omega L \times \mathbf{I}_L$$

$$Z_L = j\omega L = \omega L \angle 90^\circ$$

$$\mathbf{V}_L = Z_L \mathbf{I}_L$$

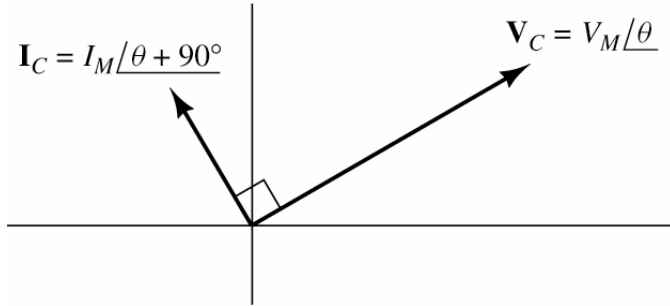


(a) Phasor diagram

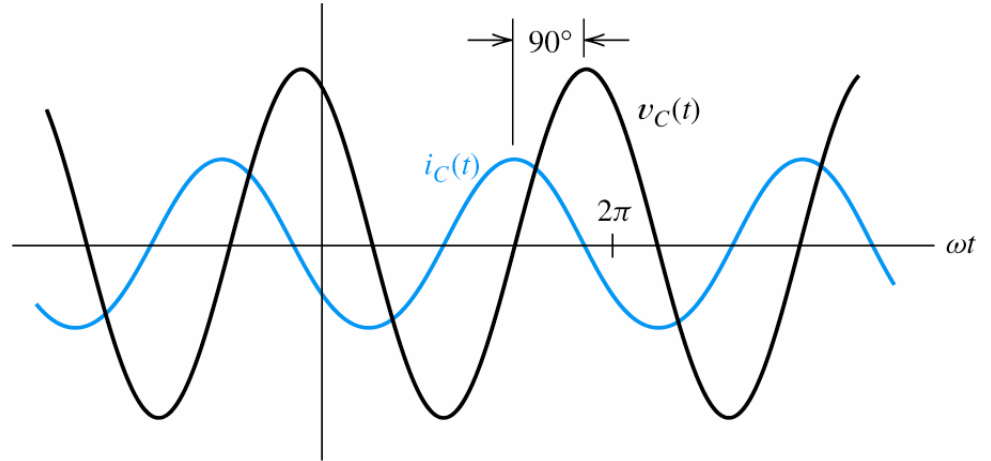

(b) Current and voltage versus time

**Figure 5.8** Current leads voltage by  $90^\circ$  in a pure capacitance.

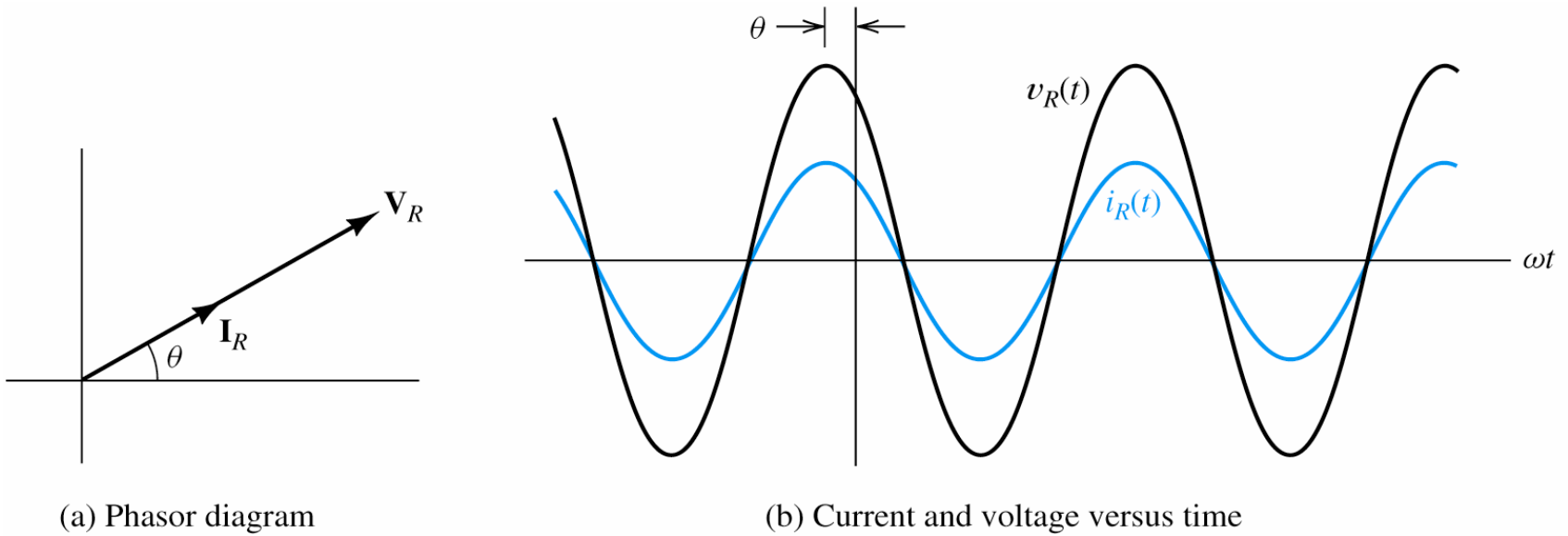


**Figure 5.9** For a pure resistance, current and voltage are in phase.

$$\mathbf{V}_C = Z_C \mathbf{I}_C$$


$$Z_C = -j \frac{1}{\omega C} = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$$

$$\mathbf{V}_R = R \mathbf{I}_R$$




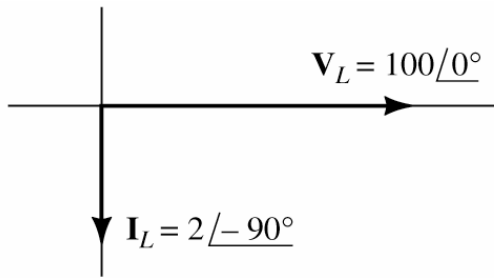

(a) Exercise 5.6 (0.25 H inductance)

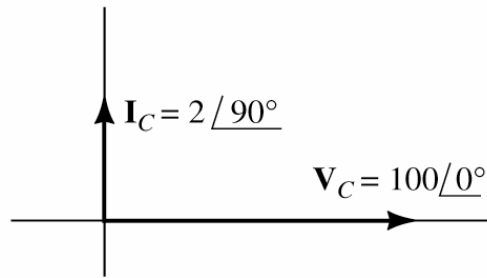

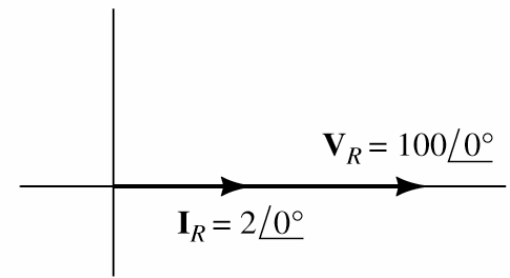(b) Exercise 5.7 (100  $\mu$ F capacitance)



(c) Exercise 5.8 (50  $\Omega$  resistance)

**Figure 5.10** Answers for Exercises 5.6, 5.7, and 5.8. The scale has been expanded for the currents compared to the voltages so the current phasors can be easily seen.

# Kirchhoff's Laws in Phasor Form

We can apply KVL directly to phasors. The sum of the phasor voltages equals zero for any closed path.


The sum of the phasor currents entering a node must equal the sum of the phasor currents leaving.

# **Circuit Analysis Using Phasors and Impedances**


- 1. Replace the time descriptions of the voltage and current sources with the corresponding phasors. (All of the sources must have the same frequency.)**

**2.** Replace inductances by their complex impedances  $Z_L = j\omega L$ . Replace capacitances by their complex impedances  $Z_C = 1/(j\omega C)$ . Resistances have impedances equal to their resistances.

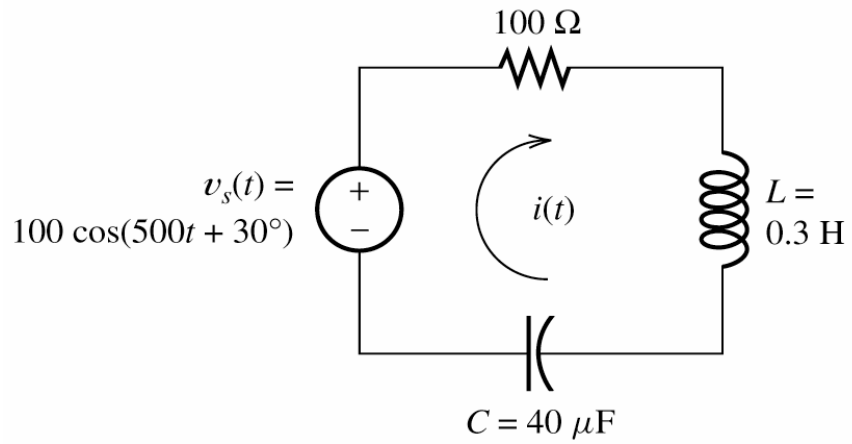**3.** Analyze the circuit using any of the techniques studied earlier in Chapter 2, performing the calculations with complex arithmetic.




(a)

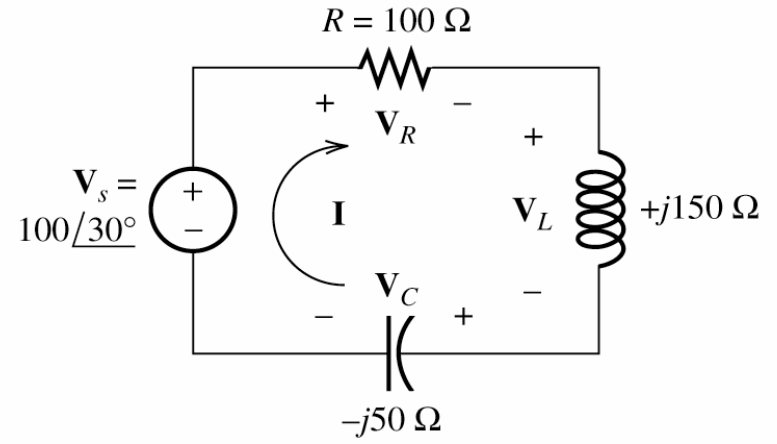


(b)


**Figure 5.11** Circuit for Example 5.3.

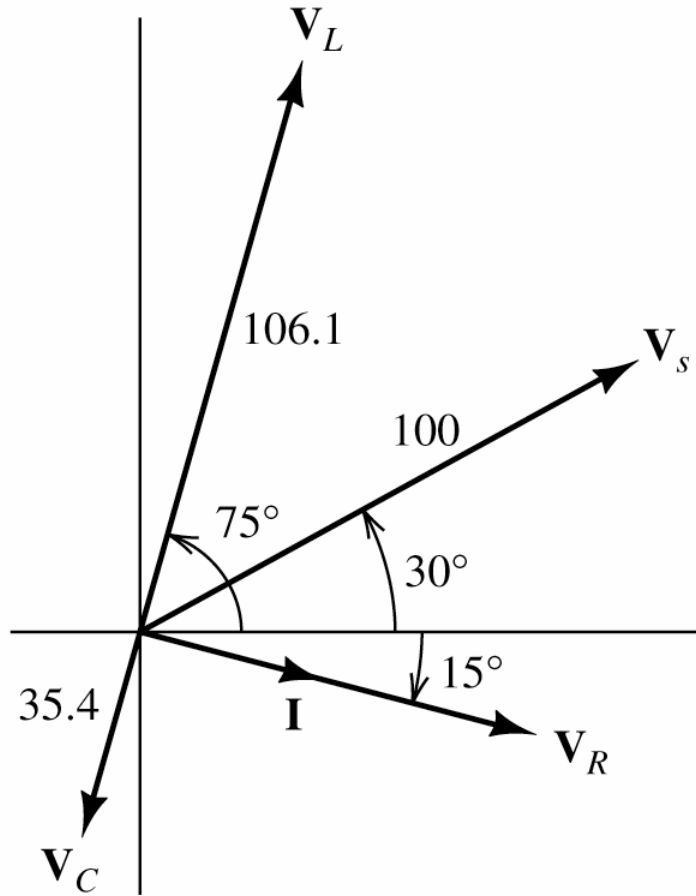


**Figure 5.12** Phasor diagram for Example 5.3.

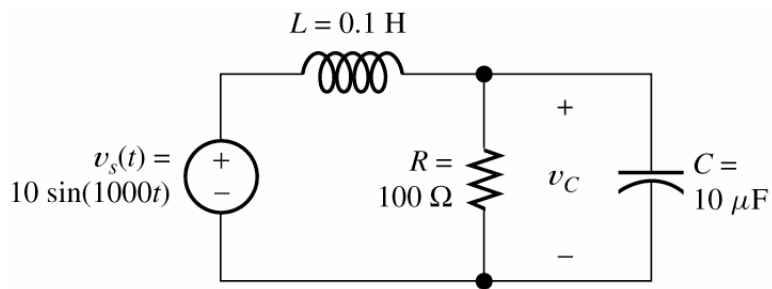

(a)

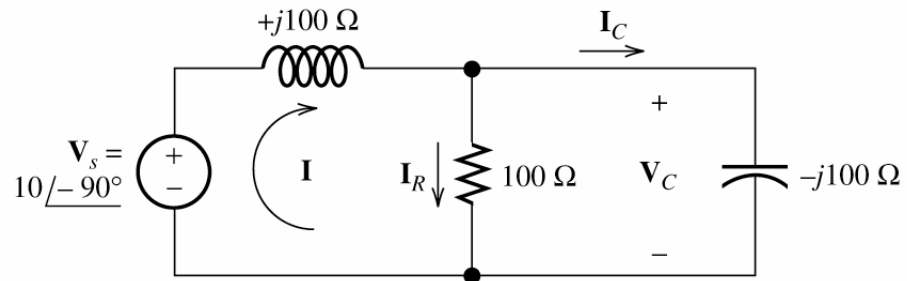


(b)

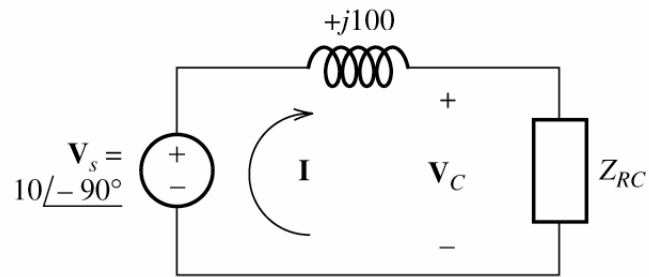


(c)

**Figure 5.13** Circuit for Example 5.4.

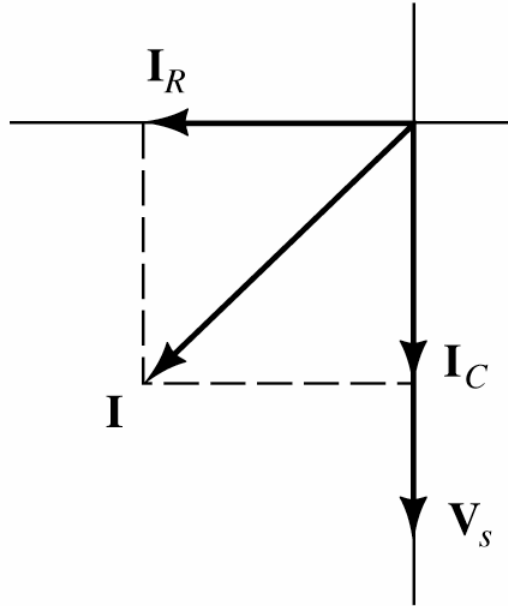


**Figure 5.14** Phasor diagram for Example 5.4.

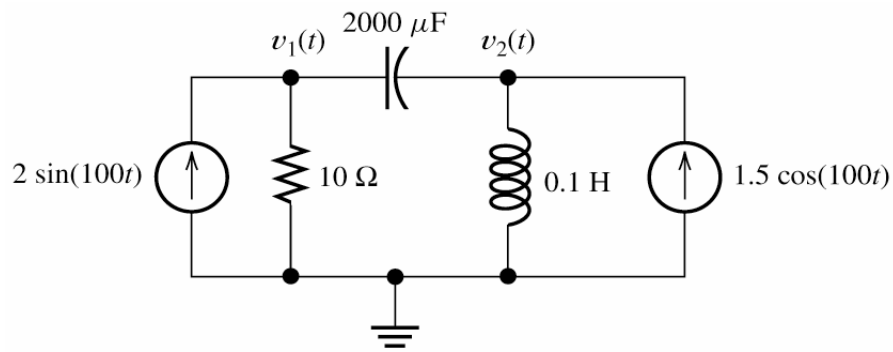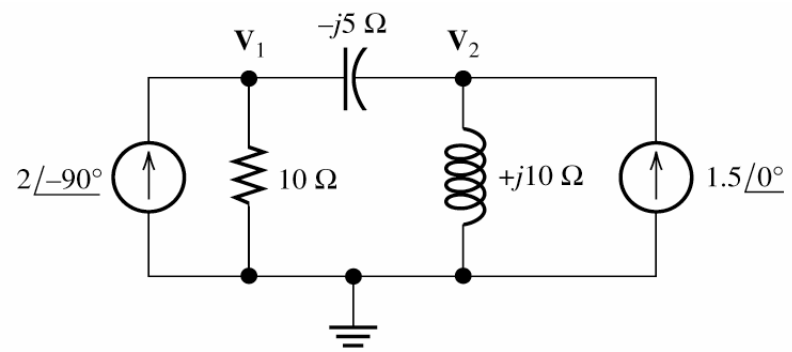




(a)




(b)

**Figure 5.15** Circuit for Example 5.5.

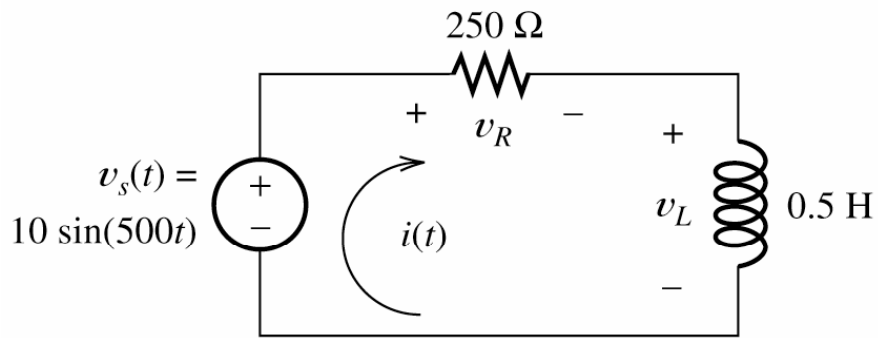


(a)

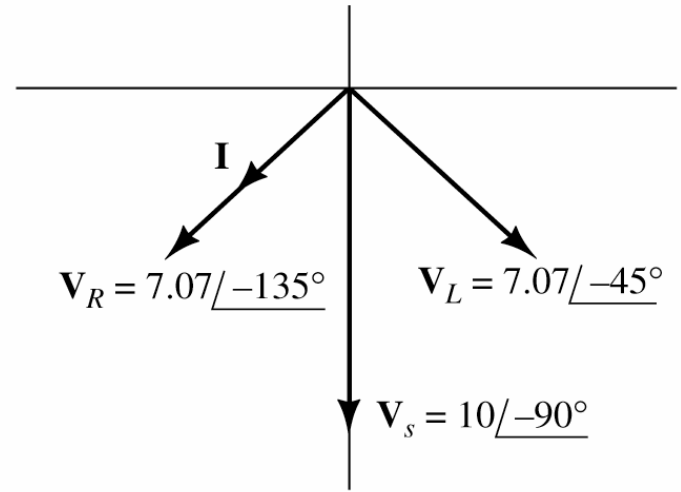


(b)


**Figure 5.16** Circuit and phasor diagram for Exercise 5.9.

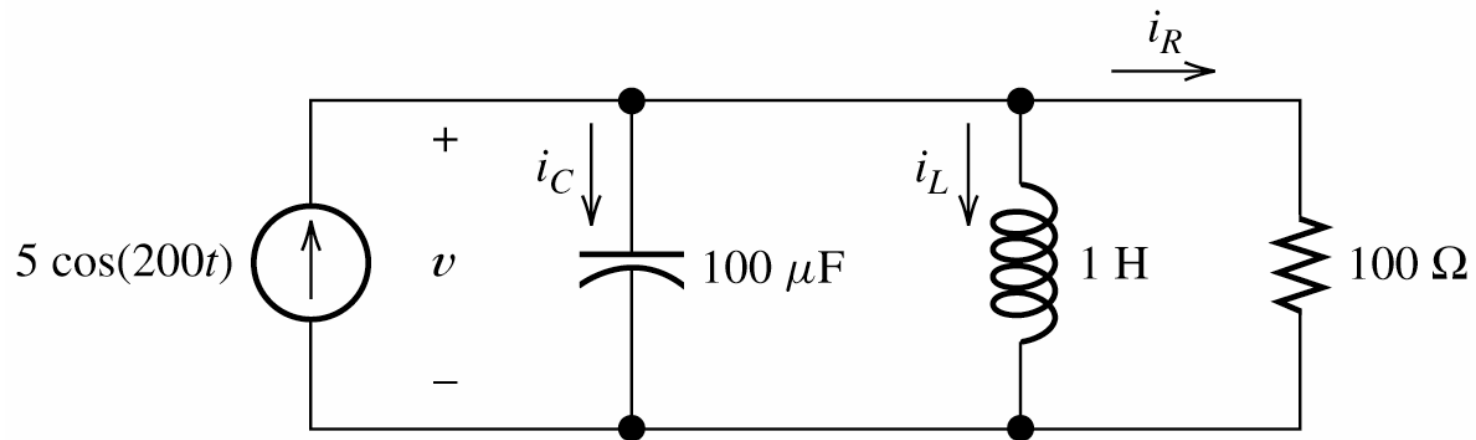


**Figure 5.17** Circuit for Exercise 5.10.

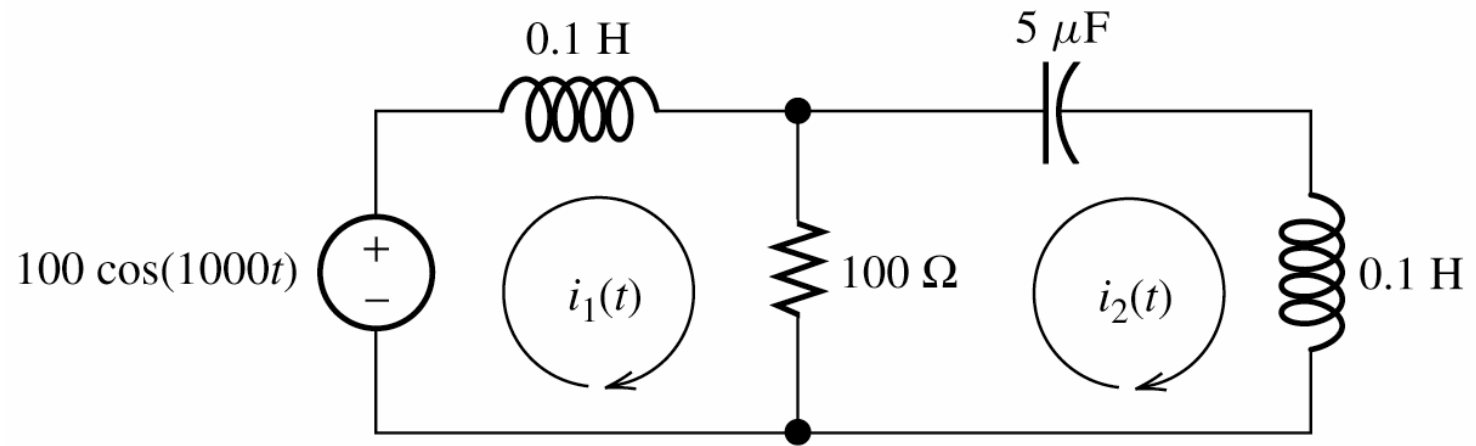


**Figure 5.18** Circuit for Exercise 5.11.

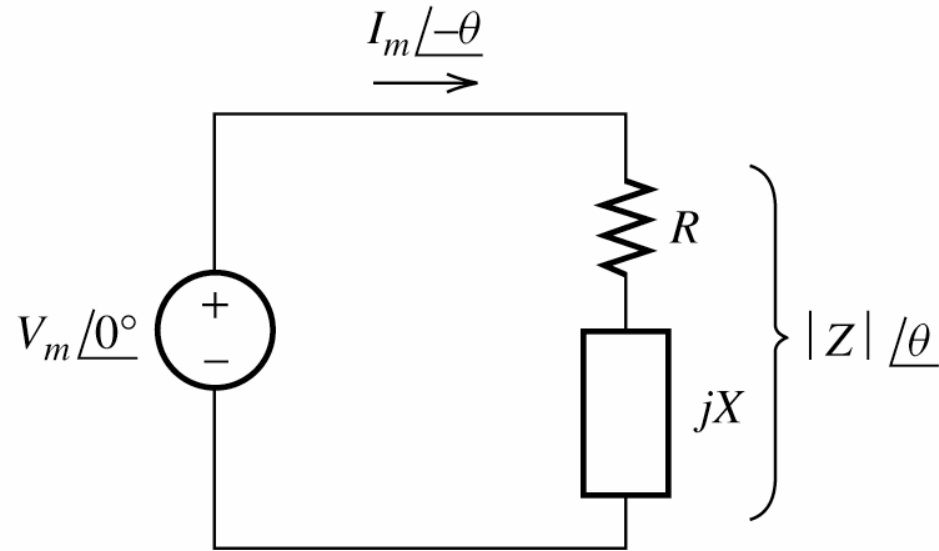

**Figure 5.19** A voltage source delivering power to a load impedance  $Z = R + jX$ .

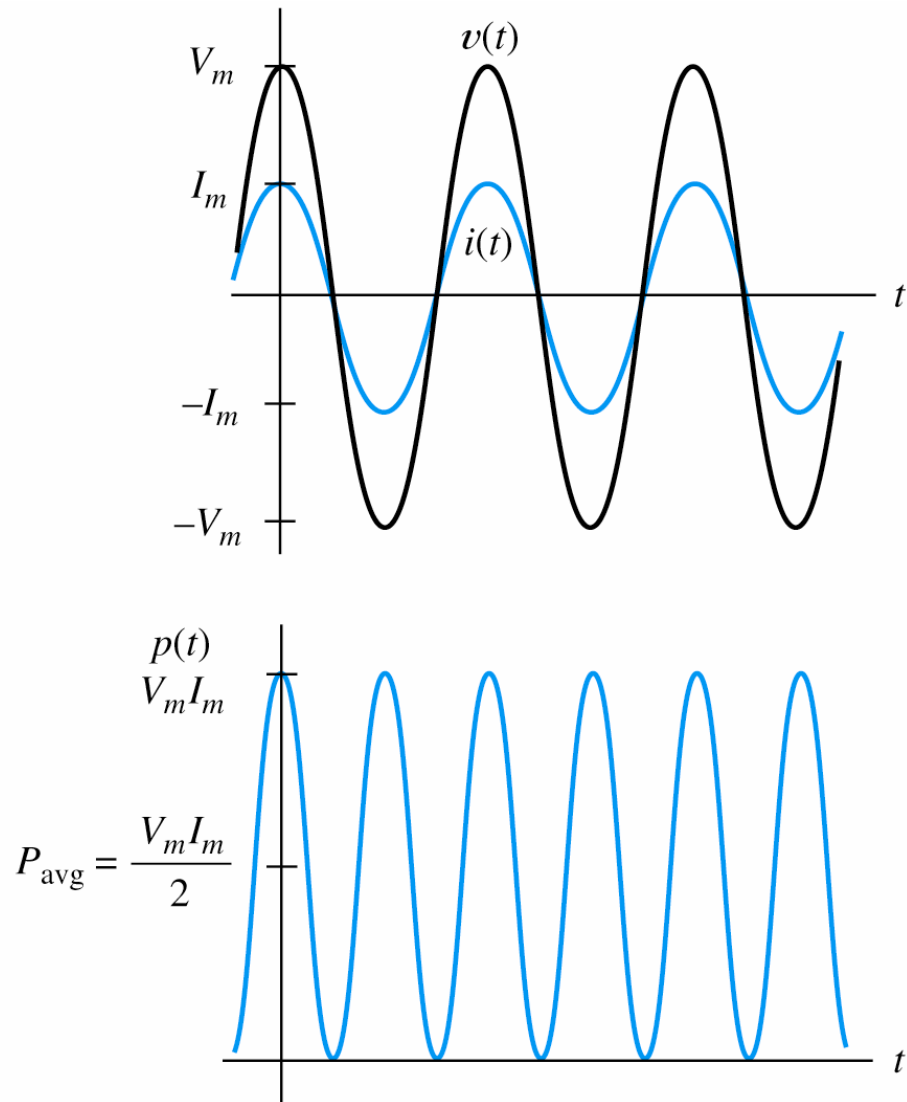

**Figure 5.20** Current, voltage, and power versus time for a purely resistive load.

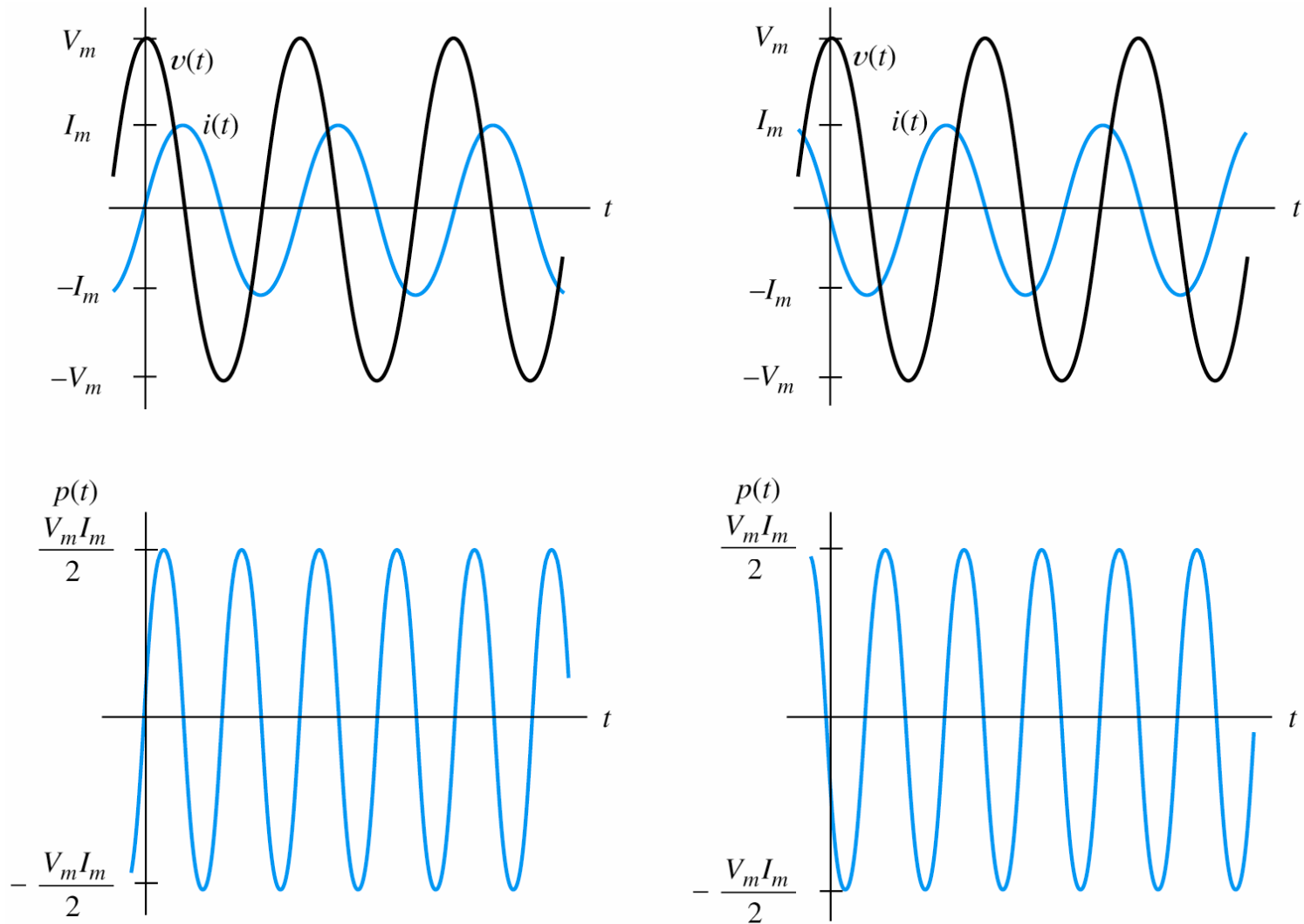

(a) Pure inductive load

(b) Pure capacitive load

**Figure 5.21** Current, voltage, and power versus time for pure energy-storage elements.

# AC Power Calculations

$$P = V_{\text{rms}} I_{\text{rms}} \cos(\theta)$$

$$\text{PF} = \cos(\theta)$$

$$\theta = \theta_v - \theta_i$$

$$Q = V_{\text{rms}} I_{\text{rms}} \sin(\theta)$$



$$\text{apparent power} = V_{\text{rms}} I_{\text{rms}}$$


$$P^2 + Q^2 = (V_{\text{rms}} I_{\text{rms}})^2$$

$$P = I_{\text{rms}}^2 R$$


$$P = \frac{V_{R\text{rms}}^2}{R}$$

$$Q = I_{\text{rms}}^2 X$$

$$Q = \frac{V_{X\text{rms}}^2}{X}$$

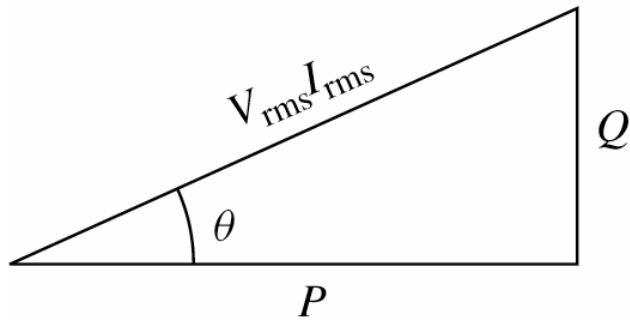


(a) Inductive load ( $\theta$  positive)

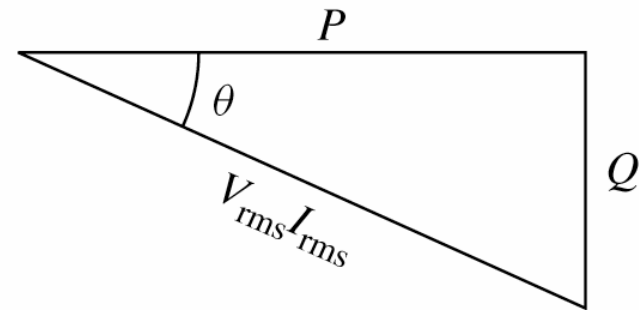


(b) Capacitive load ( $\theta$  negative)


**Figure 5.22** Power triangles for inductive and capacitive loads.

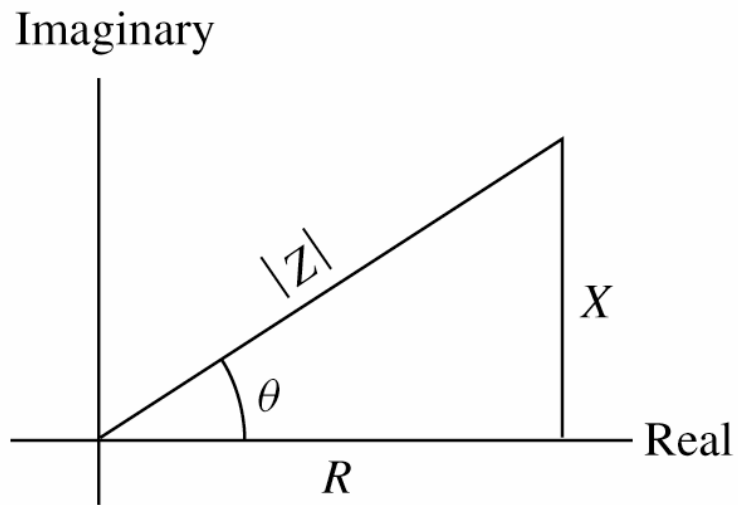


**Figure 5.23** The load impedance in the complex plane.

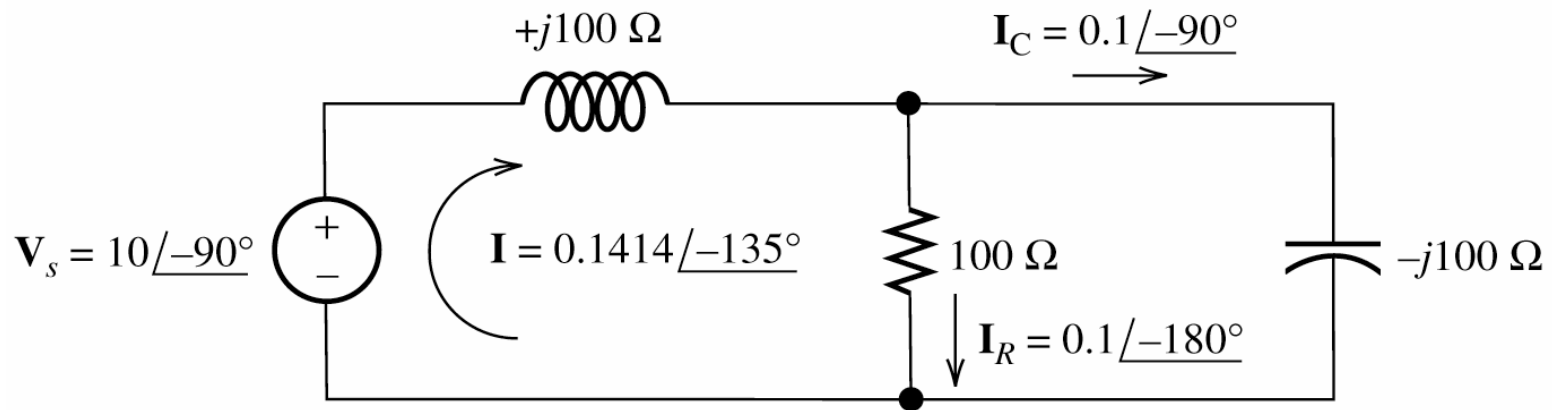


**Figure 5.24** Circuit and currents for Example 5.6.

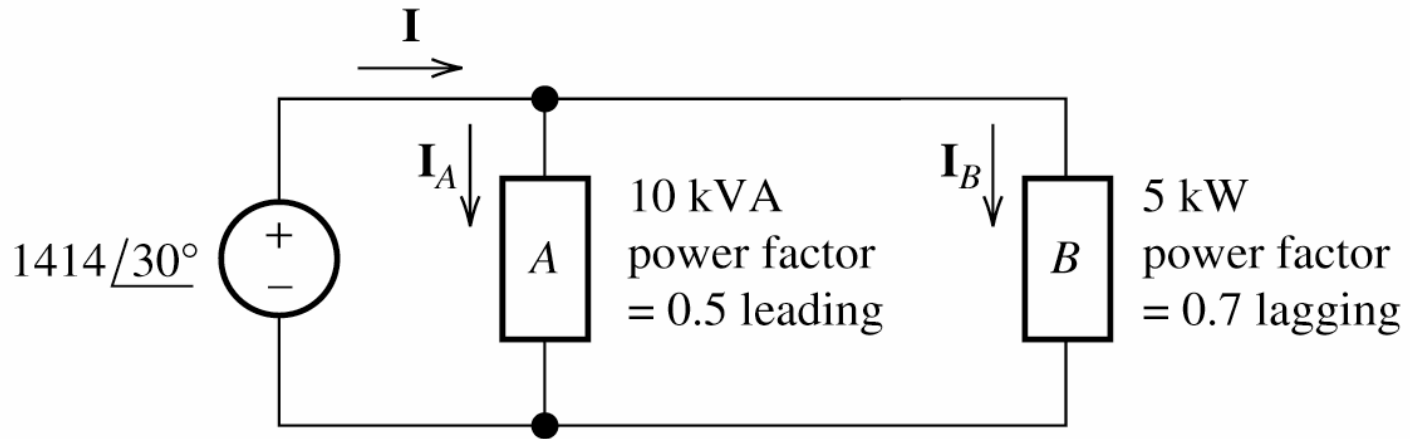

**Figure 5.25** Circuit for Example 5.7.

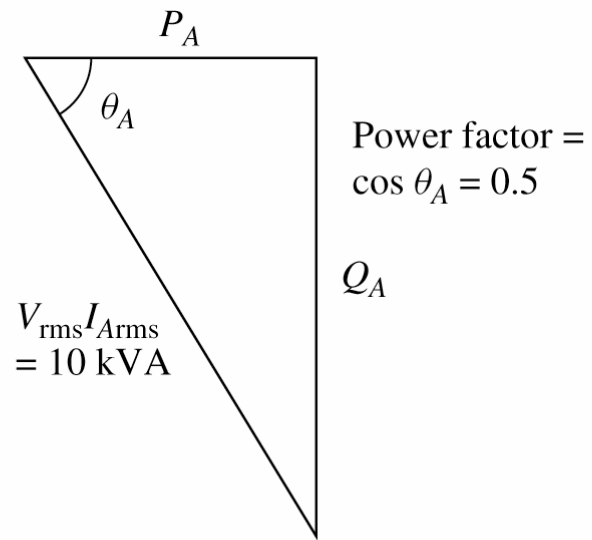


(a)

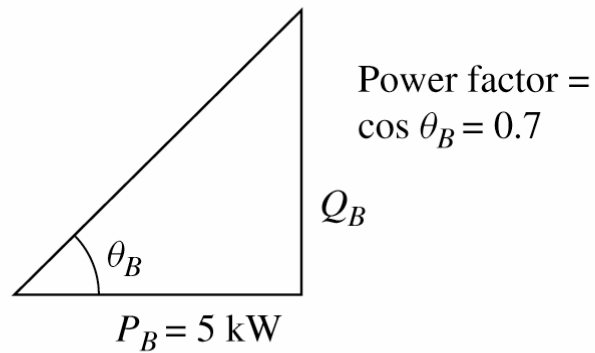


(b)

**Figure 5.26** Power triangles for loads *A* and *B* of Example 5.7.

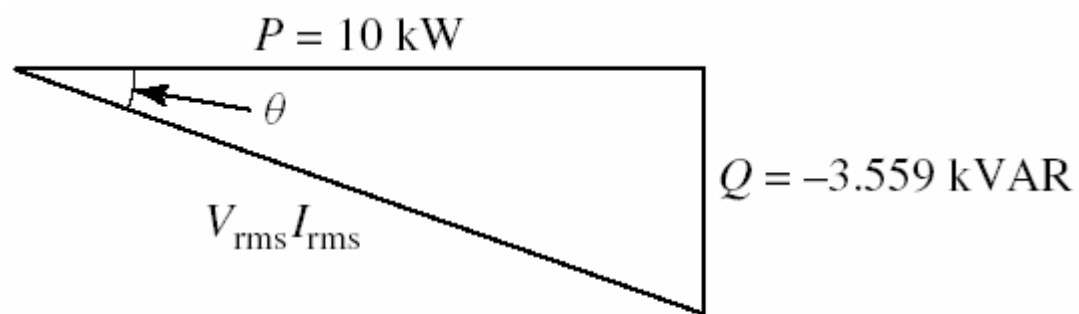


**Figure 5.27** Power triangle for the source of Example 5.7.

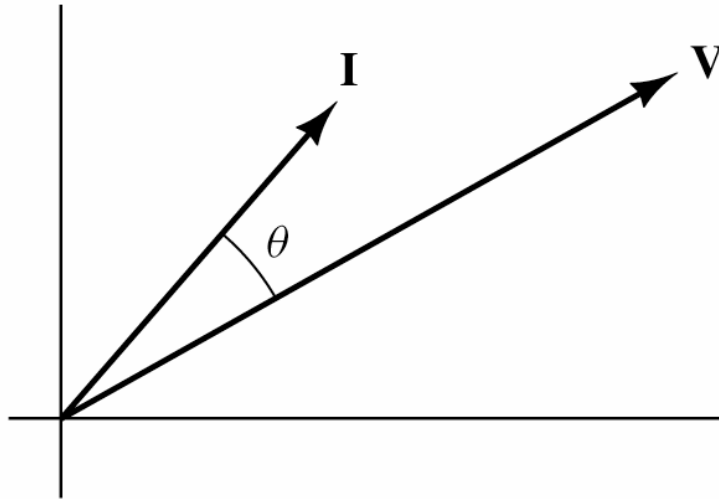


**Figure 5.28** Phasor diagram for Example 5.7.



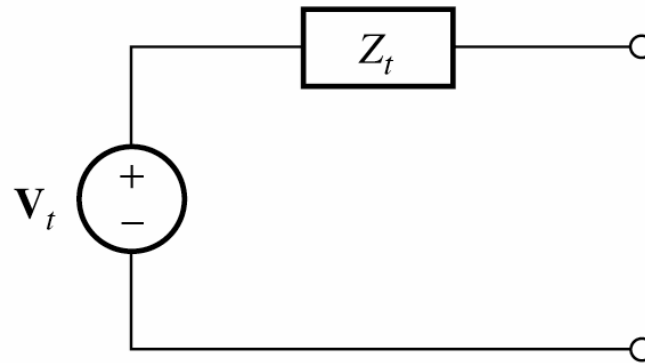

**Figure 5.29** The Thévenin equivalent for an ac circuit consists of a phasor voltage source  $\mathbf{v}_t$  in series with a complex impedance  $Z_t$ .

# THÉVENIN EQUIVALENT CIRCUITS

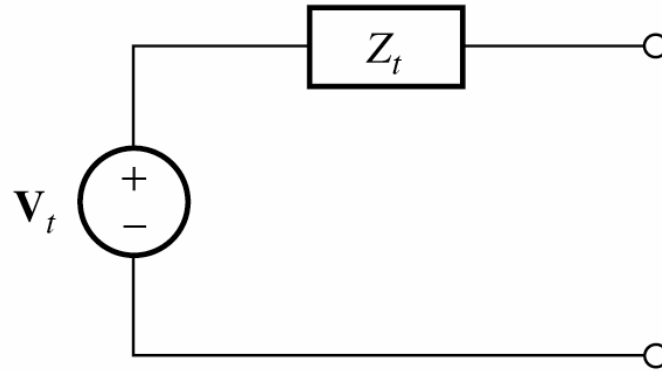

**Figure 5.29** The Thévenin equivalent for an ac circuit consists of a phasor voltage source  $v_t$  in series with a complex impedance  $Z_t$ .

The Thévenin voltage is equal to the open-circuit phasor voltage of the original circuit.


$$\mathbf{V}_t = \mathbf{V}_{oc}$$

We can find the Thévenin impedance by zeroing the independent sources and determining the impedance looking into the circuit terminals.


The Thévenin impedance equals the open-circuit voltage divided by the short-circuit current.

$$Z_t = \frac{\mathbf{V}_{oc}}{\mathbf{I}_{sc}} = \frac{\mathbf{V}_t}{\mathbf{I}_{sc}}$$


$$\mathbf{I}_n = \mathbf{I}_{sc}$$

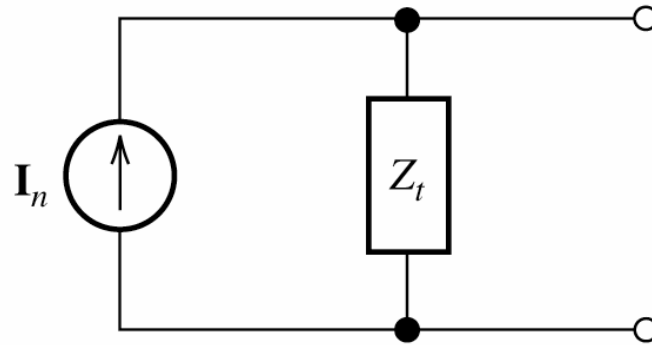


**Figure 5.30** The Norton equivalent circuit consists of a phasor current source  $I_n$  in parallel with the complex impedance  $Z_t$ .

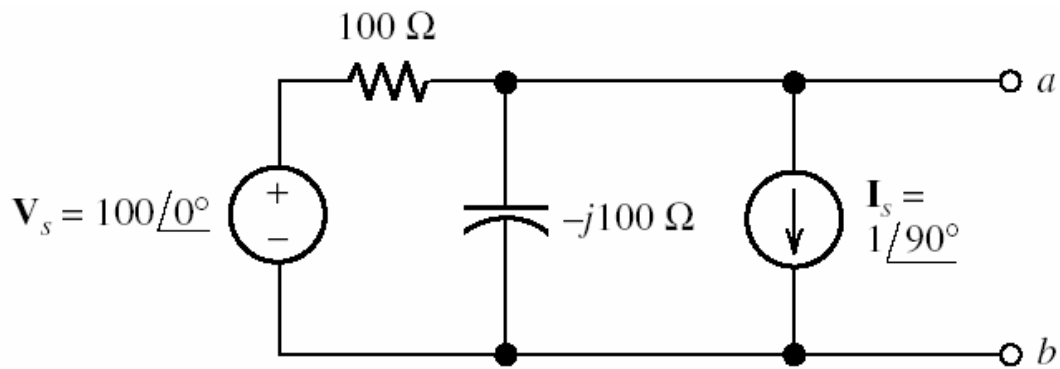

(a) Original circuit

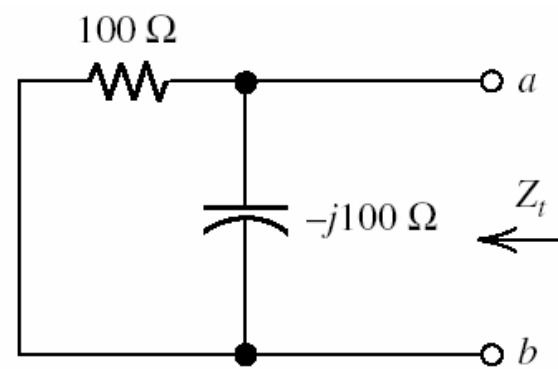


(b) Circuit with the sources zeroed

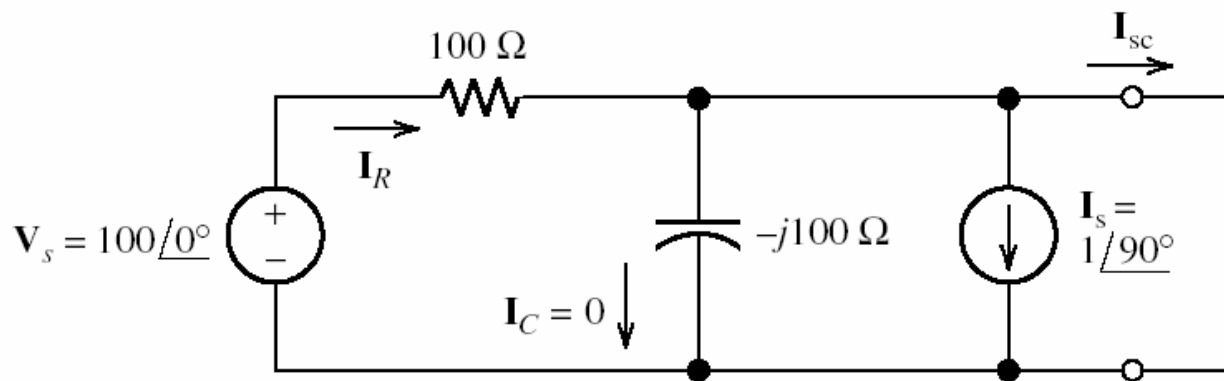


(c) Circuit with a short circuit

Figure 5.31 Circuit of Example 5.9.

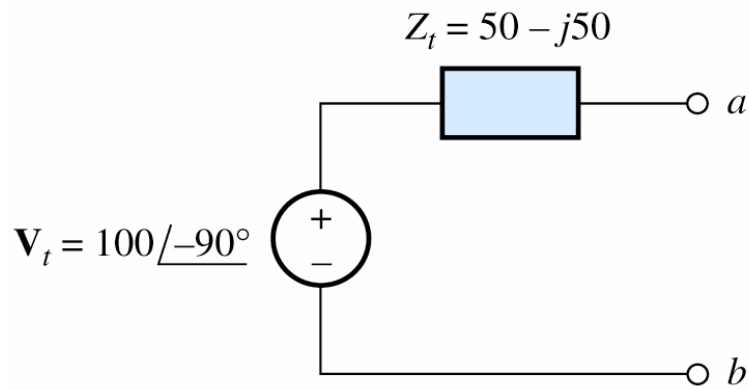


(a) Thévenin equivalent

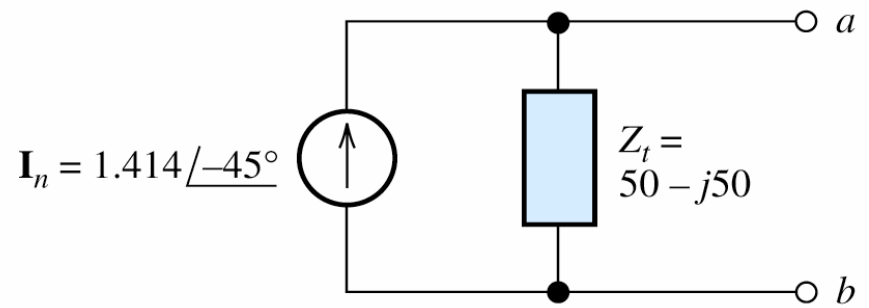

(b) Norton equivalent

**Figure 5.32** Thévenin and Norton equivalents for the circuit of Figure 5.31a.

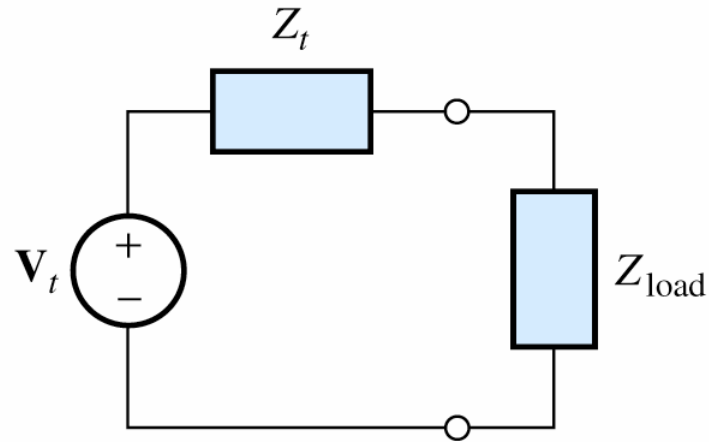


**Figure 5.33** The Thévenin equivalent of a two-terminal circuit delivering power to a load impedance.



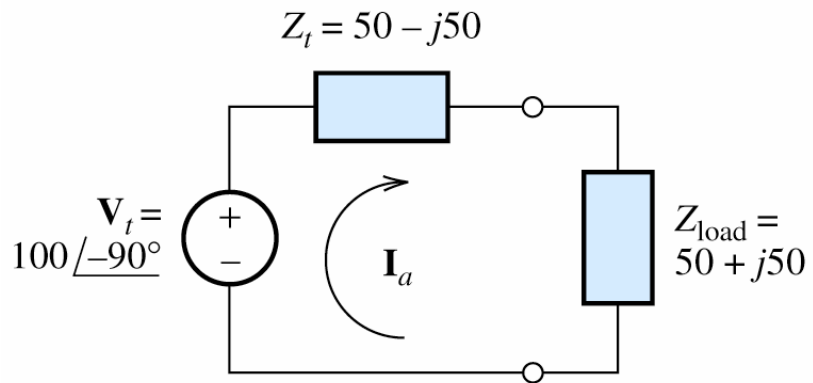
# Maximum Average Power Transfer

If the load can take on any complex value, maximum power transfer is attained for a load impedance equal to the complex conjugate of the Thévenin impedance.

If the load is required to be a pure resistance, maximum power transfer is attained for a load resistance equal to the magnitude of the Thévenin impedance.




(a)

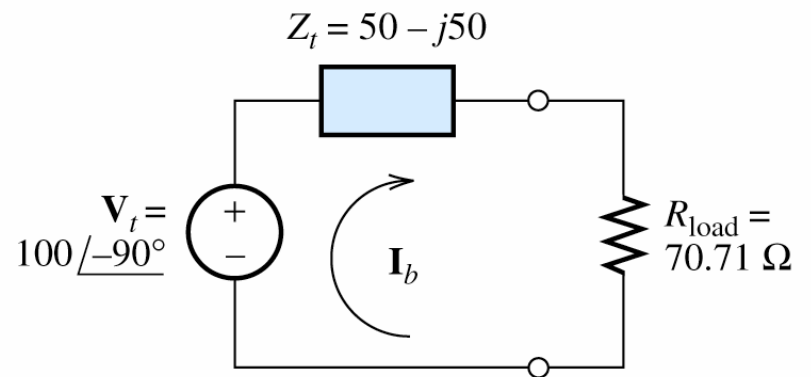

(b)


**Figure 5.34** Thévenin equivalent circuit and loads of Example 5.10.

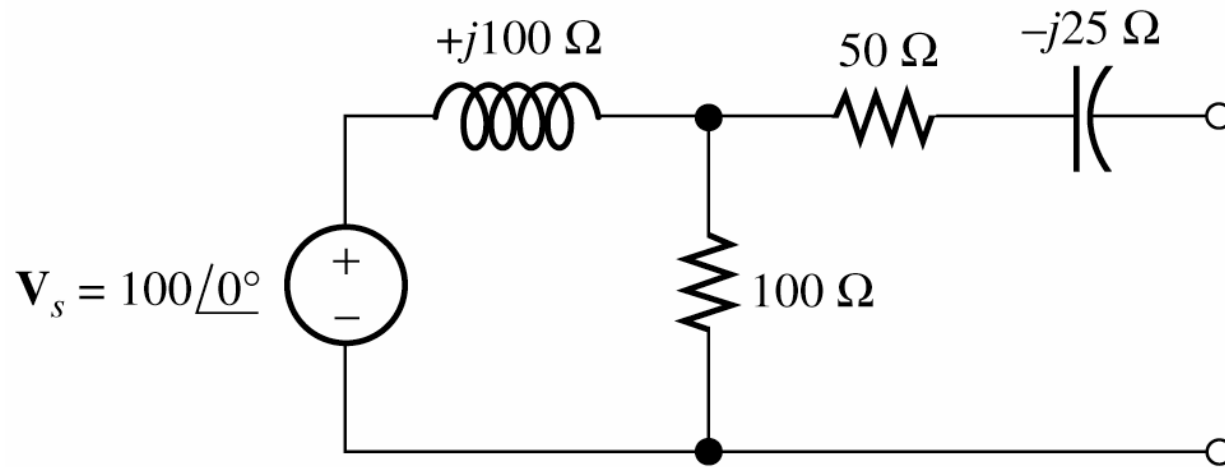


**Figure 5.35** Circuit of Exercises 5.14 and 5.15.
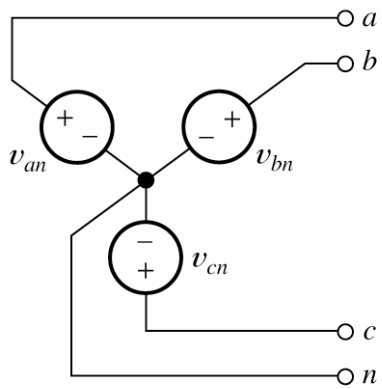
# **BALANCED THREE-PHASE CIRCUITS**


Much of the power used by business and industry is supplied by three-phase distribution systems. Plant engineers need to be familiar with three-phase power.



(a) Three-phase source

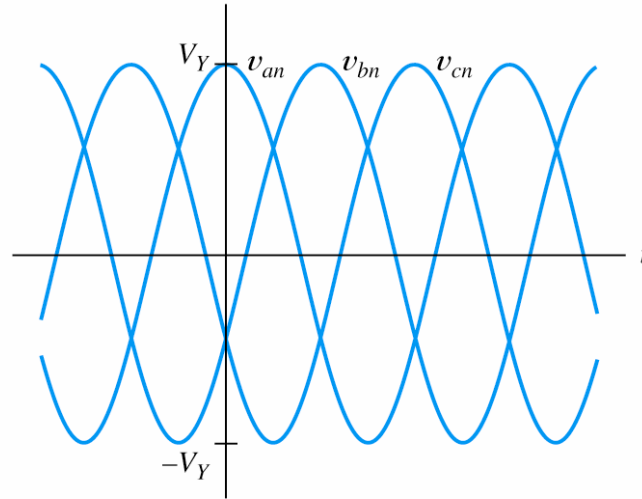

(b) Voltages versus time

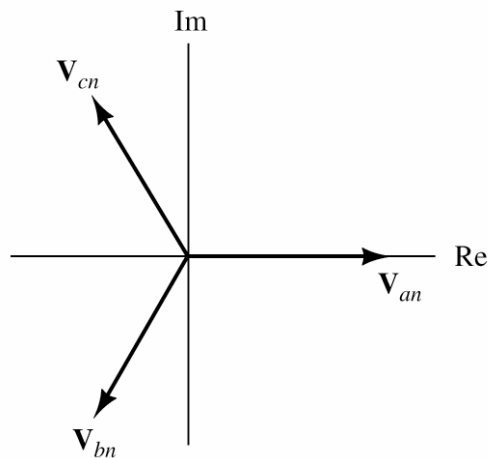


(c) Phasor diagram

**Figure 5.36** A balanced three-phase voltage source.

# Phase Sequence

Three-phase sources can have either a positive or negative phase sequence.

The direction of rotation of certain three-phase motors can be reversed by changing the phase sequence.

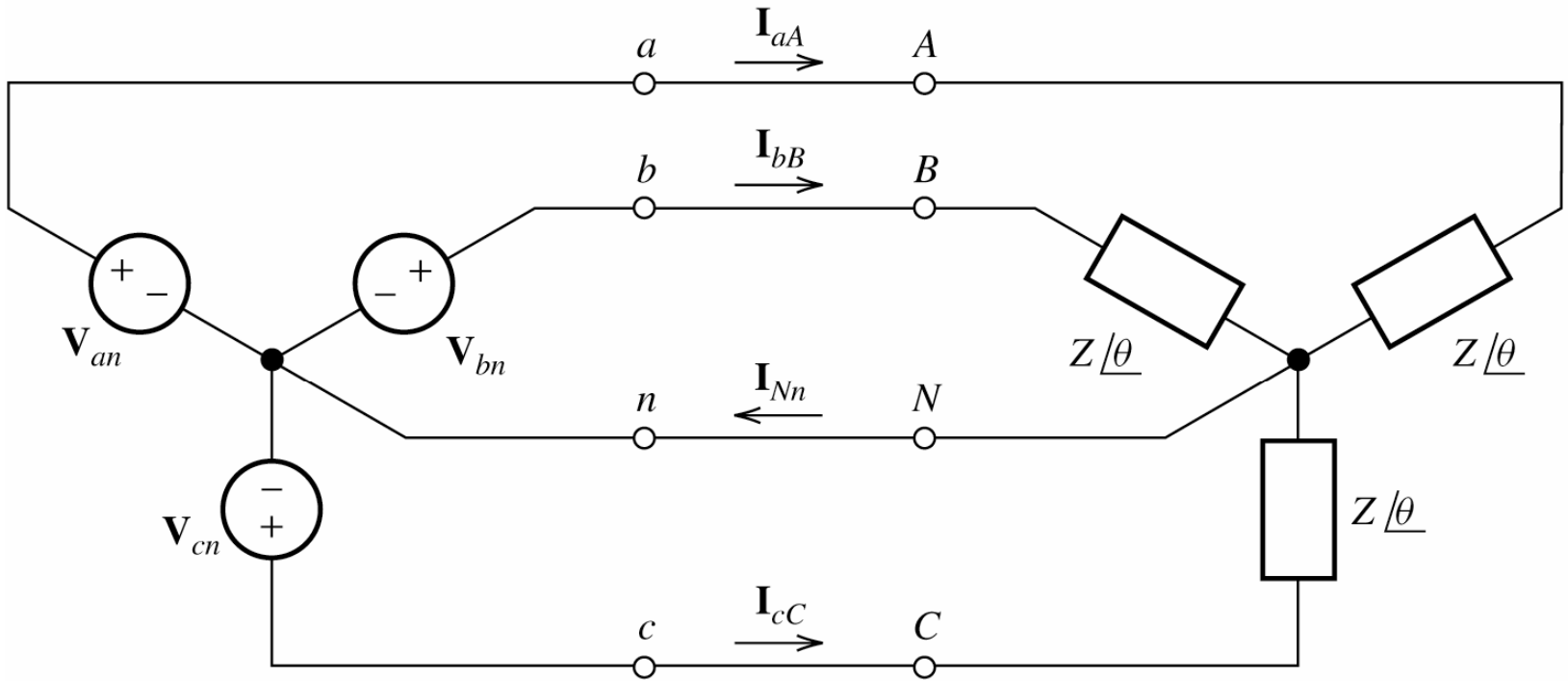


**Figure 5.37** A three-phase wye-wye connection with neutral.

# Wye–Wye Connection

Three-phase sources and loads can be connected either in a wye configuration or in a delta configuration.

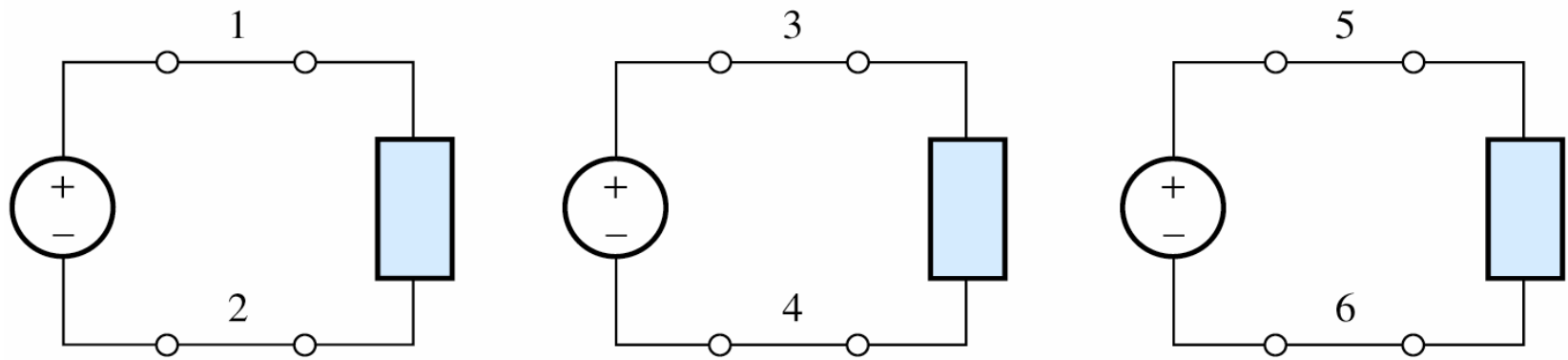The key to understanding the various three-phase configurations is a careful examination of the wye–wye circuit.

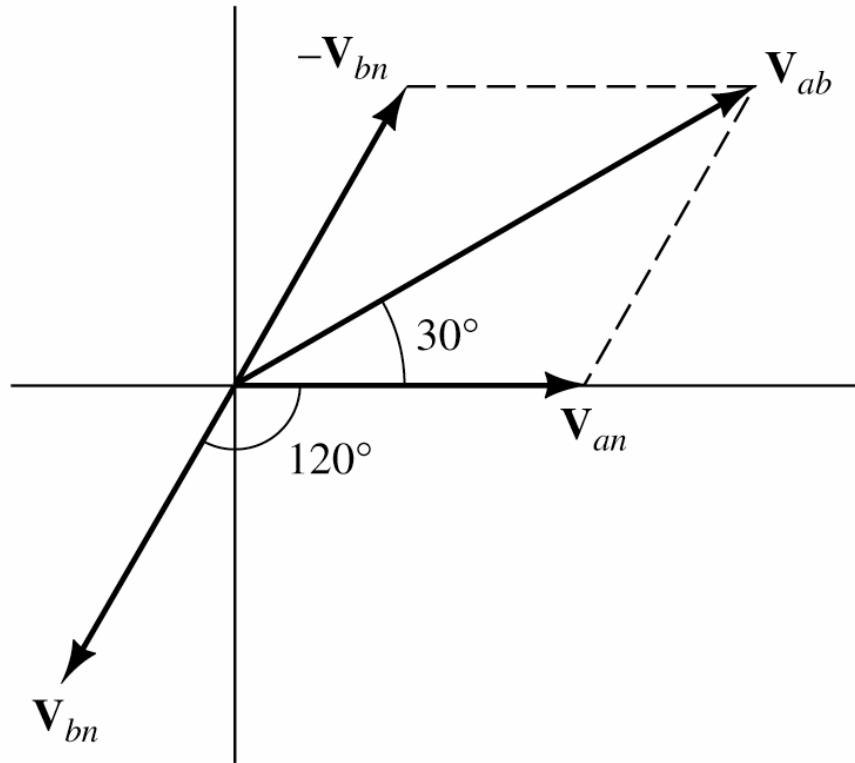





**Figure 5.38** Six wires are needed to connect three single-phase sources to three loads. In a three-phase system, the same power transfer can be accomplished with three wires.

$$P_{\text{avg}} = p(t) = 3V_{Y\text{rms}}I_{L\text{rms}} \cos(\theta)$$


$$Q = 3 \frac{V_Y I_L}{2} \sin(\theta) = 3V_{Y\text{rms}}I_{L\text{rms}} \sin(\theta)$$



**Figure 5.39** Phasor diagram showing the relationship between the line-to-line voltage  $v_{ab}$  and the line-to-neutral voltages  $v_{an}$  and  $v_{bn}$ .

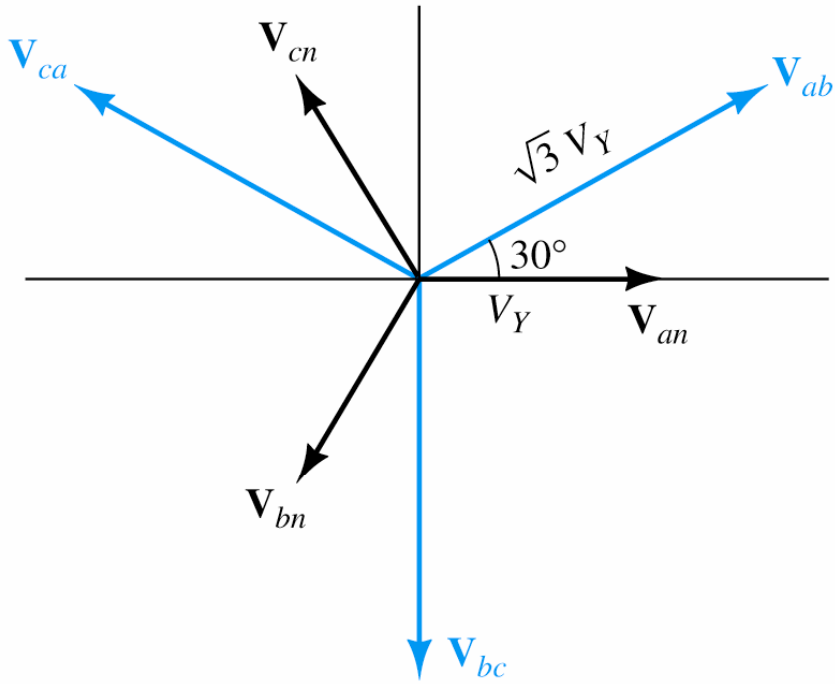


(a) All phasors starting from the origin

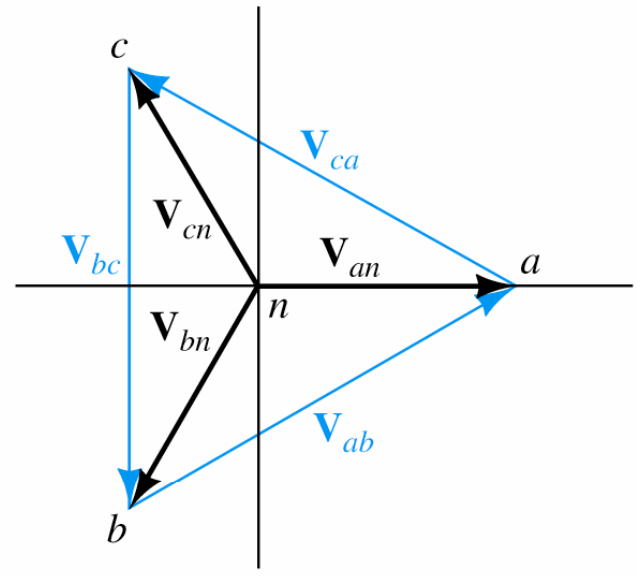


(b) A more intuitive way to draw the phasor diagram

**Figure 5.40** Phasor diagram showing line-to-line voltages and line-to-neutral voltages.

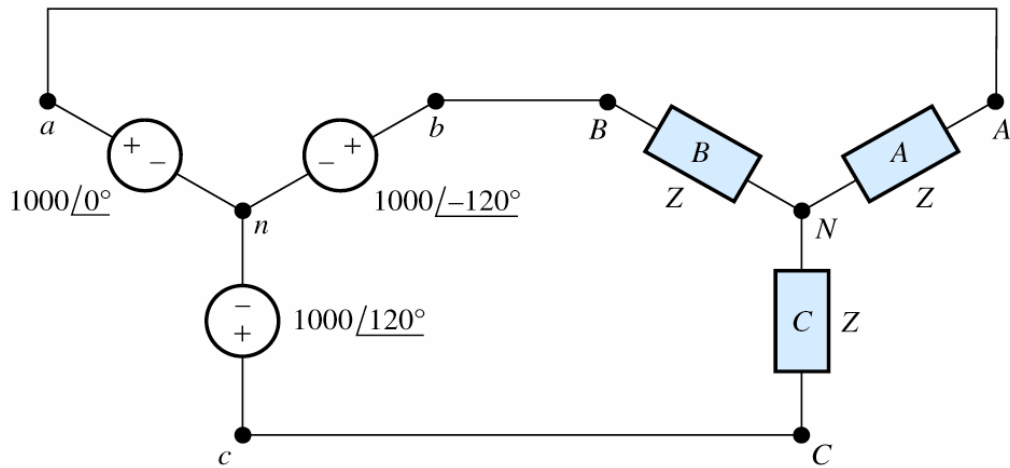


(a) Circuit diagram

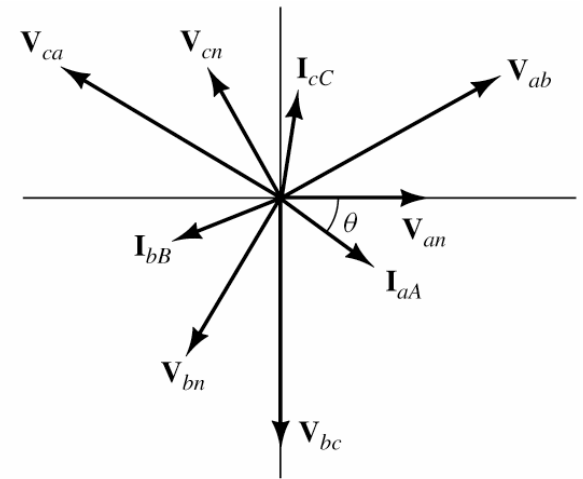


(b) Phasor diagram


**Figure 5.41** Circuit and phasor diagram for Example 5.11.

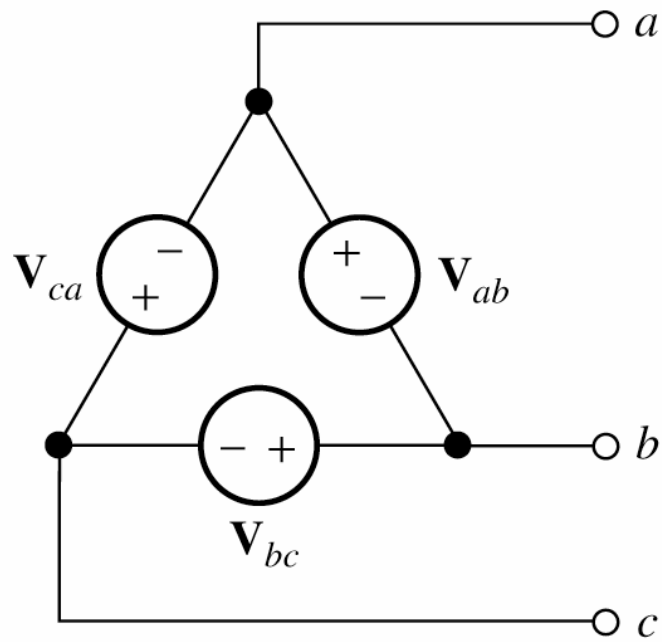

**Figure 5.42** Delta-connected three-phase source.

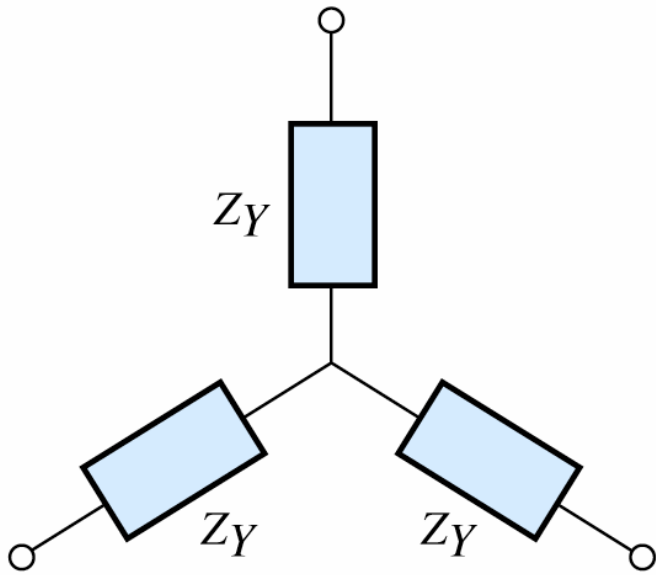


(a) Wye-connected load

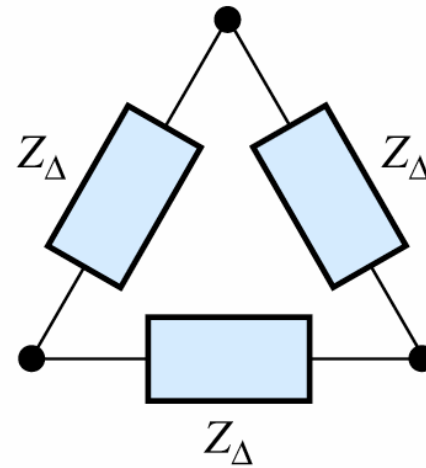


(b) Delta-connected load

**Figure 5.43** Loads can be either wye-connected or delta-connected.

$$Z_{\Delta} = 3Z_Y$$

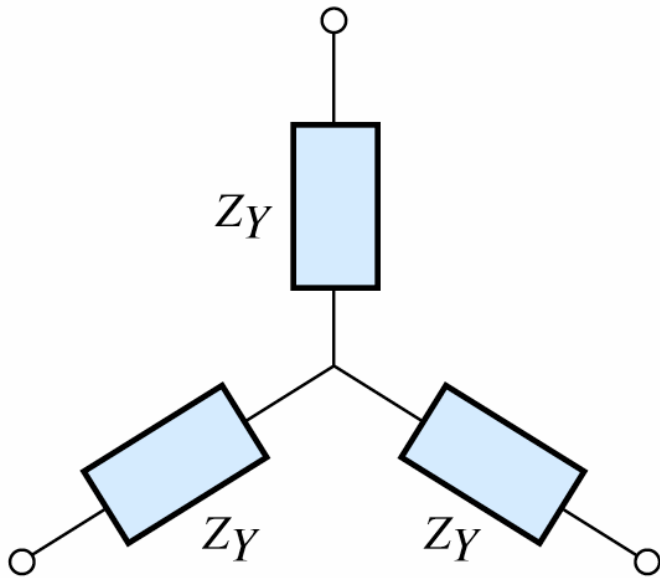


(a) Wye-connected load

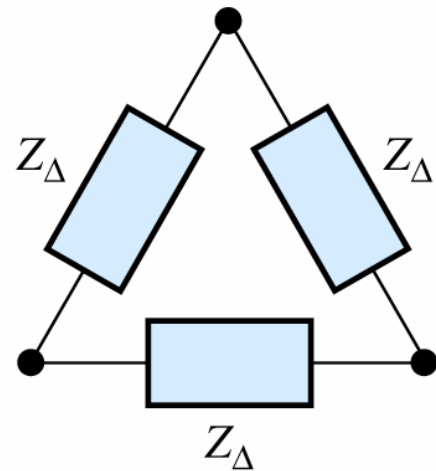


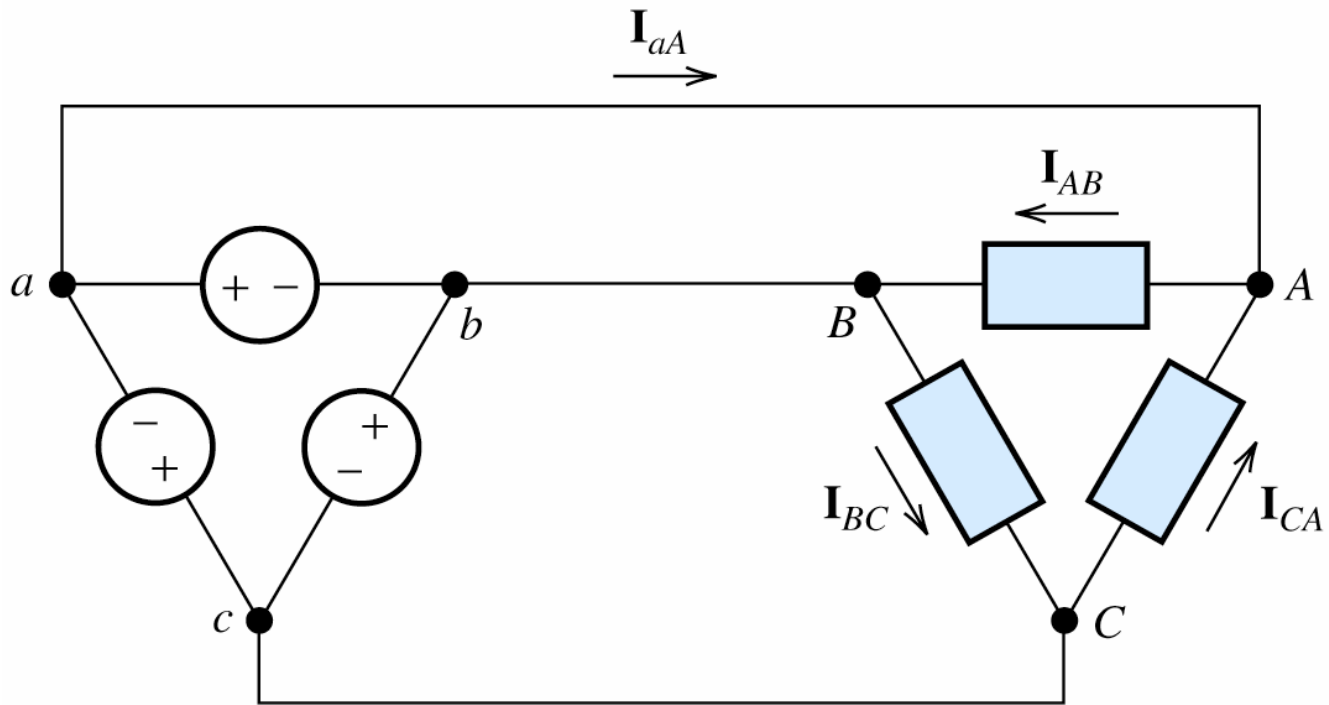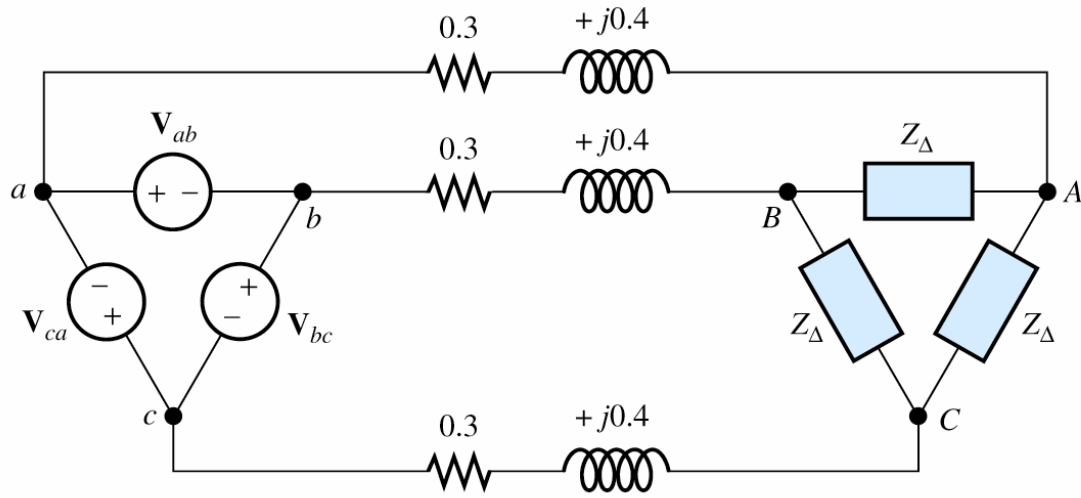(b) Delta-connected load

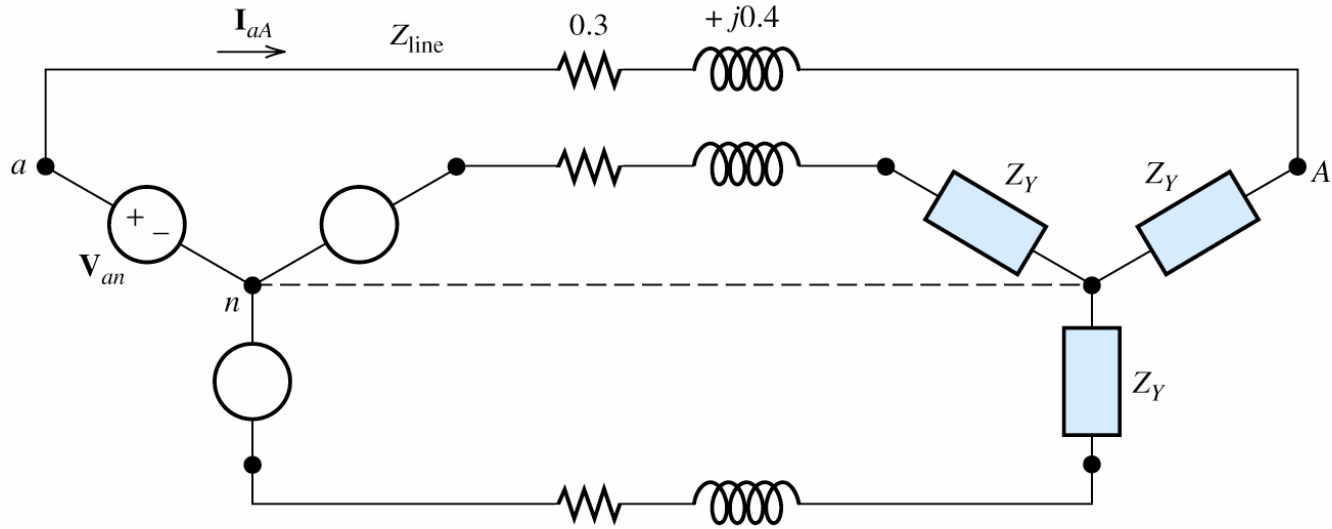




**Figure 5.44** A delta-connected source delivering power to a delta-connected load.



(a) Original circuit



(b) Wye-connected equivalent circuit

**Figure 5.45** Circuit of Example 5.12.