CHAPTER 1

P1.6* The reference direction for i_{ab} points from a to b. Because i_{ab} has a negative value, the current is equivalent to positive charge moving opposite to the reference direction. Finally since electrons have negative charge, they are moving in the reference direction (i.e., from a to b).

For a constant (dc) current, charge equals current times the time interval. Thus, $Q = (5 \text{ A}) \times (3 \text{ s}) = 15 \text{ C}.$

P1.14* (a)
$$P = -v_a i_a = -20$$
 W Energy is being supplied by the element.
(b) $P = v_b i_b = 50$ W Energy is being absorbed by the element.
(c) $P = -v_c i_c = 40$ W Energy is being absorbed by the element.

P1.19* Energy =
$$\frac{\text{Cost}}{\text{Rate}} = \frac{\$40}{0.1 \$/\text{kWh}} = 400 \text{ kWh}$$

$$P = \frac{\text{Energy}}{\text{Time}} = \frac{400 \text{ kWh}}{30 \times 24 \text{ h}} = 555.5 \text{ W} \qquad I = \frac{P}{V} = \frac{555.5}{120} = 4.630 \text{ A}$$

Reduction = $\frac{40}{555.5} \times 100\% = 7.20\%$

- P1.23 The current supplied to the electronics is i = p/v = 50/12.6 = 3.968 A. The ampere-hour rating of the battery is the operating time to discharge the battery multiplied by the current. Thus, the operating time is T = 100/i = 25.2 hours. The energy delivered by the battery is W = pT = 50(25.2) = 1260 wh = 1.26 kWh. Neglecting the cost of recharging, the cost of energy for 300 discharge cycles is $Cost = 75/(300 \times 1.26) = 0.1984$ \$/kWh.
- **P1.28*** At the node joining elements A and B, we have $i_a + i_b = 0$. Thus, $i_a = -2$ A. For the node at the top end of element C, we have $i_b + i_c = 3$. Thus, $i_c = 1$ A. Finally, at the top right-hand corner node, we have $3 + i_e = i_d$. Thus, $i_d = 4$ A. Elements A and B are in series.

P1.33 We are given $v_a = 5 V$, $v_b = 7 V$, $v_f = -10 V$, and $v_h = 6 V$. Applying KVL, we find

$$\begin{aligned}
 & V_{d} = V_{a} + V_{b} = 12 \, V & V_{c} = -V_{a} - V_{f} - V_{h} = -1 \, V \\
 & V_{e} = -V_{a} - V_{c} + V_{d} = 8 \, V & V_{g} = V_{e} - V_{h} = 2 \, V \\
 & V_{b} = V_{c} + V_{e} = 7 \, V
 \end{aligned}$$

P1.48*



As shown above, the 2 A current circulates clockwise through all three elements in the circuit. Applying KVL, we have

$$V_c = V_R + 10 = 5i_R + 10 = 20$$
 V

 $P_{current-source} = -v_c i_R = -40$ W. Thus, the current source delivers power.

 $P_{R} = (i_{R})^{2}R = 2^{2} \times 5 = 20$ W. The resistor absorbs power.

 $P_{voltage-source} = 10 \times i_R = 20$ W. The voltage source absorbs power.

P1.57*



Applying KVL around the outside of the circuit:

$$V_{\rm s} = 3i_{\rm s} + 4 + 2 = 15 \,\rm V$$