

CHAPTER 3

P3.5*

$$i = C \frac{dv}{dt}$$

$$\frac{dv}{dt} = \frac{i}{C} = \frac{100 \times 10^{-6}}{2000 \times 10^{-6}} = 0.05 \text{ V/s}$$


$$\Delta t = \frac{\Delta v}{dv/dt} = \frac{100}{0.05} = 2000 \text{ s}$$

P3.6 $Q = CV = 5 \times 10^{-6} \times 10^3 = 5 \text{ mC}$

$$W = \frac{1}{2} CV^2 = \frac{1}{2} \times 5 \times 10^{-6} \times (10^3)^2 = 2.5 \text{ J}$$


$$P = \frac{\Delta W}{\Delta t} = \frac{2.5}{10^{-6}} = 2.5 \text{ MW}$$

P3.11

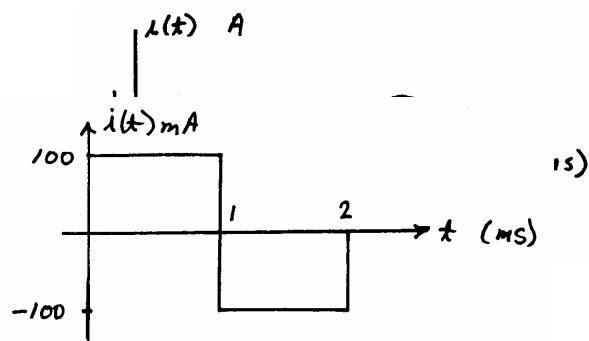


$$v(t) = \frac{1}{C} \int_0^t i(t) dt + v(0)$$

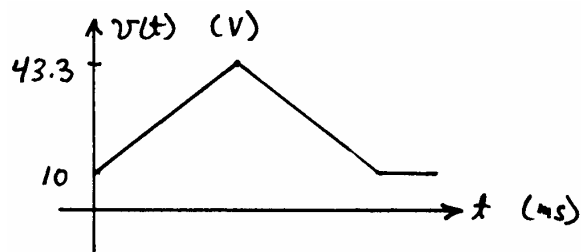
$$v(t) = 0.333 \times 10^6 \int_0^t i(t) dt + 10$$



$$p(t) = v(t)i(t)$$

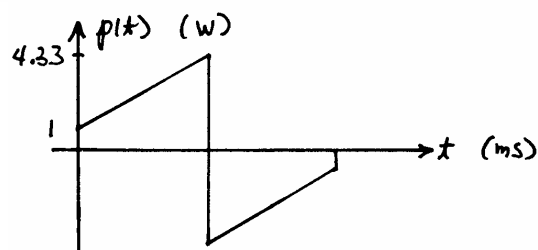

$$w(t) = \frac{1}{2} CV^2(t)$$

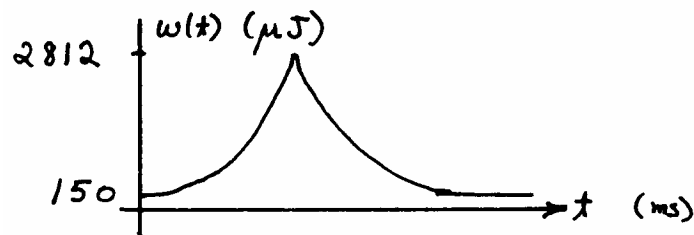

$$= 1.5 \times 10^{-6} \times v^2(t)$$

P3.21* (a) $C_{eq} = 1 + \frac{1}{1/2 + 1/2} = 2 \mu\text{F}$

(b) The two $4\text{-}\mu\text{F}$ capacitances are in series and have an equivalent capacitance of $\frac{1}{1/4 + 1/4} = 2 \mu\text{F}$. This combination is in parallel with the $2\text{-}\mu\text{F}$ capacitance, giving an equivalent of $4 \mu\text{F}$. Then the $6 \mu\text{F}$ is in series, giving a capacitance of $\frac{1}{1/6 + 1/4} = 2.4 \mu\text{F}$. Finally, the $3 \mu\text{F}$ is in parallel, giving an equivalent capacitance of $C_{eq} = 3 + 2.4 = 5.4 \mu\text{F}$.

P3.25 $C_{eq} = \frac{1}{1/C_1 + 1/C_2} = 2/3 \mu\text{F}$

The charges stored on each capacitor and on the equivalent capacitance are equal.

$$Q = C_{eq} \times 12 \text{ V} = 8 \mu\text{C}$$

$$v_1 = \frac{Q}{C_1} = 8 \text{ V}$$

$$v_2 = \frac{Q}{C_2} = 4 \text{ V}$$

As a check, we verify that $v_1 + v_2 = 12 \text{ V}$.

P3.30* The charge Q remains constant because the terminals of the capacitor are open-circuited.

$$Q = C_1 V_1 = 1000 \times 10^{-12} \times 1000 = 1 \mu\text{C}$$


$$W_1 = (1/2)C_1(V_1)^2 = 500 \mu\text{J}$$

After the distance between the plates is doubled, the capacitance becomes $C_2 = 500 \text{ pF}$.


The voltage increases to $V_2 = \frac{Q}{C_2} = \frac{10^{-6}}{500 \times 10^{-12}} = 2000 \text{ V}$ and the stored energy is $W_2 = (1/2)C_2(V_2)^2 = 1000 \mu\text{J}$. The additional energy is supplied by the force needed to pull the plates apart.

P3.40* $L = 2 \text{ H}$


$$v_L(t) = L \frac{di_L(t)}{dt}$$

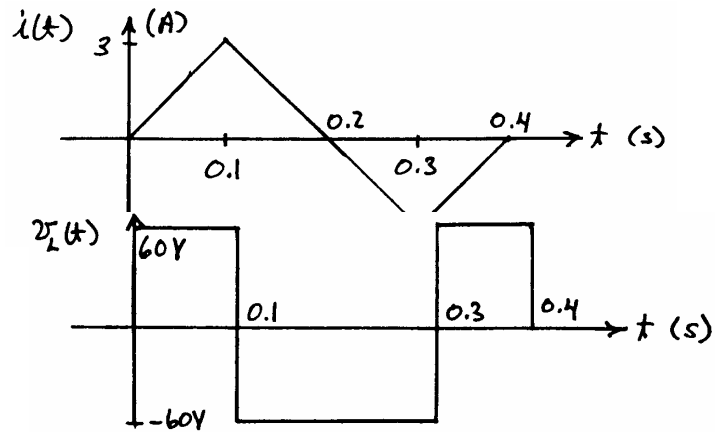

$$p(t) = v_L(t)i_L(t)$$

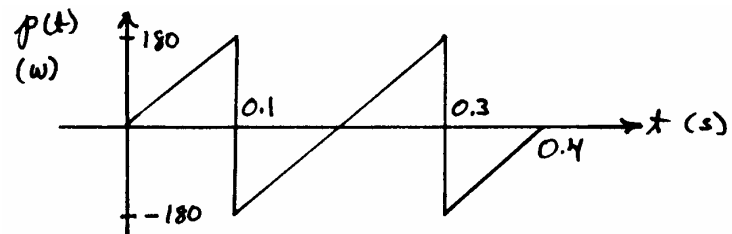

$$w(t) = \frac{1}{2} L [i_L(t)]^2$$

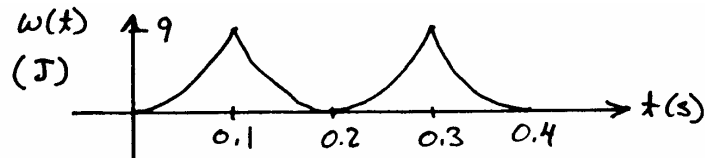

P3.48 $i_L(t_0) = \frac{1}{L} \int_0^{t_0} v_L(t) dt + i_L(0)$ $i_L(2) = \frac{1}{3} \int_0^2 5 dt + 0 = 3.333 \text{ A}$
 $p(2) = v_L(2)i_L(2) = 16.67 \text{ W}$ $w(2) = \frac{1}{2} L i_L^2(2) = 16.67 \text{ J}$

P3.54 (a) The 2 H inductors and 0.5 H inductor have no effect because they are in parallel with a short circuit. Thus, $L_{eq} = 1 \text{ H}$.

(b) The two 2-H inductances in parallel are equivalent to 1 H. Also, the 1 H in parallel with the 3 H inductance is equivalent to 0.75 H. Thus,

$$L_{eq} = 1 + \frac{1}{1/(1+1) + 1/(2+0.75)} = 2.158 \text{ H}.$$

P3.59 (a) $v_R(t) = Ri(t) = 0.1 \cos(10^5 t)$
 $v_L(t) = L \frac{di(t)}{dt} = -100 \sin(10^5 t)$
 $v(t) = v_R(t) + v_L(t)$
 $= 0.1 \cos(10^5 t) - 100 \sin(10^5 t)$

In this case to obtain 1% accuracy, the resistance can be neglected.

(b) For $i(t) = 0.1 \cos(10t)$, we have


$$v_R(t) = 0.1 \cos(10t)$$

$$v_L(t) = -0.01 \sin(10t)$$

$$v(t) = 0.1 \cos(10t) - 0.01 \sin(10t)$$

Thus in this case, the parasitic resistance cannot be neglected.

P3.64* (a)

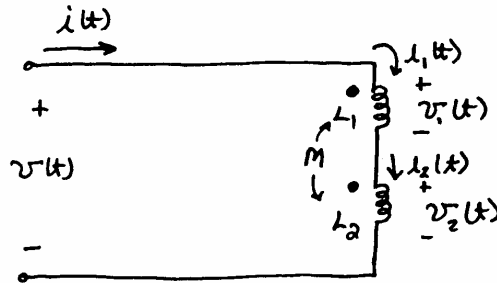

As in Figure 3.23a, we can write

$$v_1(t) = L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt}$$

$$v_2(t) = M \frac{di_1(t)}{dt} + L_2 \frac{di_2(t)}{dt}$$

However, for the circuit at hand, we have $i(t) = i_1(t) = i_2(t)$.

Thus,

$$v_1(t) = (L_1 + M) \frac{di(t)}{dt}$$

$$v_2(t) = (L_2 + M) \frac{di(t)}{dt}$$

Also, we have $v(t) = v_1(t) + v_2(t)$.

Substituting, we obtain $v(t) = (L_1 + 2M + L_2) \frac{di(t)}{dt}$.

Thus, we can write $v(t) = L_{eq} \frac{di(t)}{dt}$, in which

$$L_{eq} = L_1 + 2M + L_2.$$

(b) Similarly, for the dot at the bottom end of L_2 , we have

$$L_{eq} = L_1 - 2M + L_2$$