## **CHAPTER 4**



P4.7 Prior to t = 0, we have v(t) = 0 because the switch is closed. After t = 0, we can write the following KCL equation at the top node of the circuit:

$$\frac{v(t)}{R} + C \frac{dv(t)}{dt} = 1 \,\mathrm{mA}$$

Multiplying both sides by *R* and substituting values, we have

$$0.01 \frac{dv(t)}{dt} + v(t) = 10$$
 (1)

The solution is of the form

$$v(t) = K_1 + K_2 \exp(-t/RC) = K_1 + K_2 \exp(-100t)$$
(2)

Substituting Equation (2) into Equation (1), we eventually obtain  $K_1 = 10$ 

The voltage across the capacitance cannot change instantaneously, so we have

$$\nu(0 +) = \nu(0 -) = 0$$
  

$$\nu(0 +) = 0 = K_1 + K_2$$
  
Thus,  $K_2 = -K_1 = -10$ , and the solution is  

$$\nu(t) = 10 - 10 \exp(-100t) \text{ for } t > 0$$



P4.15\* In steady state, the equivalent circuit is:



Thus, we have

 $i_1 = 0$  $i_3 = i_2 = 2 A$  P4.21 With the switch closed and the circuit in steady state prior to t = 0, the capacitor behaves as an open circuit, and  $v_c(0-) = 25$  V. Because there cannot be infinite current in this circuit when the switch opens, we have  $v_{c}(0+) = 25 \text{ V}$ . After switching and the circuit reaches steady state, we have  $v_c(\infty) = 25 \frac{15 \text{ k}\Omega}{10 \text{ k}\Omega + 15 \Omega \text{ k}} = 15 \text{ V}$ . For  $t \ge 0$ , the Thévenin resistance seen by the capacitor is  $R_t = \frac{1}{1/10 + 1/15} = 6 \text{ k}\Omega$ , and the time constant is  $\tau = R_t C = 60$  ms. The general form of the solution for  $t \ge 0$  is  $v_{c}(t) = K_{1} + K_{2} \exp(-t/\tau)$ . However, we know that  $v_{c}(0+) = 25 = K_{1} + K_{2}$ and  $\nu_c(\infty) = 15 = K_1$ . Solving, we find that  $K_2 = 10$ . Thus, we have  $V_{c}(t) = 25 \quad t \leq 0$  $= 15 + 10 \exp(-t/\tau)$   $t \ge 0$ でけ 251 15V



P4.30\* In steady state with the switch closed, we have i(t) = 0 for t < 0because the closed switch shorts the source.

120

180

In steady state with the switch open, the inductance acts as a short circuit and the current becomes  $i(\infty) = 1A$ . The current is of the form

240

$$i(t) = K_1 + K_2 \exp(-Rt/L)$$
 for  $t \ge 0$ 

60

in which  $R = 20 \Omega$ , because that is the Thévenin resistance seen looking back from the terminals of the inductance with the switch open. Also, we have

$$i(0+) = i(0-) = 0 = K_1 + K_2$$
  
 $i(\infty) = 1 = K_1$ 

0

-60

Thus,  $K_2 = -1$  and the current (in amperes) is given by

$$\dot{t}(t) = 0$$
 for  $t < 0$   
= 1 - exp(-20t) for  $t \ge 0$ 

P4.35 Write a current equation at the top node:

$$5\cos(10t) = \frac{v(t)}{R} + \frac{1}{L} \int_0^t v(t) dt + i_L(0)$$

Differentiate each term with respect to time to obtain a differential equation:

$$-50\sin(10t) = \frac{1}{R}\frac{dv(t)}{dt} + \frac{v(t)}{L}$$

Substitute the particular solution suggested in the hint:

$$-50\sin(10t) = \frac{1}{R} [-10A\sin(10t) + 10B\cos(10t)] + \frac{1}{L} [A\cos(10t) + B\sin(10t)]$$

Equating coefficients of sine and cosine terms, we have

$$-50 = \frac{-10A}{R} + \frac{B}{L}$$
$$0 = \frac{10B}{R} + \frac{A}{L}$$

Solving for *A* and *B* and substituting values of the circuit parameters, we find A = 25 and B = -25. The time constant is  $\tau = L/R = 0.1$  s, and the general form of the solution is

 $v(t) = K_1 \exp(-t/\tau) + v_p(t) = K_1 \exp(-t/\tau) + 25\cos(10t) - 25\sin(10t)$ However, because the current in the inductor is zero at t = 0+, the 5 A supplied by the source must flow through the 10- $\Omega$  resistor and we have v(0+) = 50. Substituting this into the general solution we find  $K_1 = 25$ . Thus

 $\nu(t) = 25 \exp(-t / \tau) + 25 \cos(10t) - 25 \sin(10t) \quad t \ge 0$ 

P4.37\* Applying KVL, we obtain the differential equation:

$$L\frac{di(t)}{dt} + Ri(t) = 5\exp(-t) \text{ for } t > 0$$
(1)

We try a particular solution of the form:

$$i_{p}(t) = A \exp(-t) \tag{2}$$

in which A is a constant to be determined. Substituting Equation (2) into Equation (1), we have

 $-LA\exp(-t) + RA\exp(-t) = 5\exp(-t)$ 

which yields

$$A = \frac{5}{R-L} = -1$$

The complementary solution is of the form

 $i_c(t) = K_1 \exp(-Rt/L)$ 

The complete solution is

 $i(t) = i_{\rho}(t) + i_{c}(t) = -\exp(-t) + K_{1}\exp(-Rt/L)$ 

Before the switch closes, the current must be zero. Furthermore, the current cannot change instantaneously, so we have i(0+) = 0. Therefore, we have  $i(0+) = 0 = -1 + K_1$  which yields  $K_1 = 1$ . Finally, the current is given by  $i(t) = -\exp(-t) + \exp(-Rt/L)$  for  $t \ge 0$ .

P4.45\* Applying KVL to the circuit, we obtain

$$L\frac{di(t)}{dt} + Ri(t) + v_c(t) = v_s = 50$$
<sup>(1)</sup>

For the capacitance, we have

$$i(t) = C \frac{dv_c(t)}{dt}$$
<sup>(2)</sup>

Using Equation (2) to substitute into Equation (1) and rearranging, we have

$$\frac{d^2 v_c(t)}{dt^2} + (R/L) \frac{dv_c(t)}{dt} + (1/LC) v_c(t) = 50/LC$$

$$\frac{d^2 v_c(t)}{dt^2} + 4 \times 10^4 \frac{dv_c(t)}{dt} + 10^8 v_c(t) = 50 \times 10^8$$
(3)

We try a particular solution of the form  $v_{Cp}(t) = A$ , resulting in A = 50. Thus,  $v_{Cp}(t) = 50$ . (An alternative method to find the particular solution is to solve the circuit in dc steady state. Since the capacitance acts as an open circuit, the steady-state voltage across it is 50 V.) Comparing Equation (3) with Equation 4.67 in the text, we find

$$\alpha = \frac{R}{2L} = 2 \times 10^4$$
$$\omega_0 = \frac{1}{\sqrt{LC}} = 10^4$$

Since we have  $\alpha > \omega_0$ , this is the overdamped case. The roots of the characteristic equation are found from Equations 4.72 and 4.73 in the text.

$$S_{1} = -\alpha + \sqrt{\alpha^{2} - \omega_{0}^{2}} = -0.2679 \times 10^{4}$$
$$S_{2} = -\alpha - \sqrt{\alpha^{2} - \omega_{0}^{2}} = -3.732 \times 10^{4}$$

The complementary solution is

 $v_{cc}(t) = K_1 \exp(s_1 t) + K_2 \exp(s_2 t)$ 

and the complete solution is

 $v_{c}(t) = 50 + K_{1} \exp(s_{1}t) + K_{2} \exp(s_{2}t)$ 

The initial conditions are

$$v_{c}(0) = 0$$
 and  $i(0) = 0 = C \frac{dv_{c}(t)}{dt}|_{t=0}$ 

Thus, we have

$$\frac{v_{c}(0) = 0 = 50 + K_{1} + K_{2}}{\frac{dv_{c}(t)}{dt}}\Big|_{t=0} = 0 = s_{1}K_{1} + s_{2}K_{2}$$

Solving, we find  $K_1 = -53.87$  and  $K_2 = 3.867$ . Finally, the solution is  $v_c(t) = 50 - 53.87 \exp(s_1 t) + 3.867 \exp(s_2 t)$ 

P4.48 (a) Using Equation 4.103 from the text, the damping coefficient is  $\alpha = \frac{1}{2RC} = 20 \times 10^{6}$ 

Equation 4.104 gives the undamped resonant frequency

$$\omega_0 = \frac{1}{LC} = 10 \times 10^6$$

Equation 4.71 gives the damping ratio

$$\zeta = \alpha / \omega_0 = 2$$

Thus, we have an overdamped circuit.

(b) Writing a current equation at t = 0 +, we have  $\frac{\nu(0+)}{R} + i_{L}(0+) + C\nu'(0+) = 1$ Substituting  $\nu(0+) = 0$  and  $i_{L}(0+) = 0$ , yields  $\nu'(0+) = 1/C = 10^{9}$ 

(c) Under steady-state conditions, the inductance acts as a short circuit. Therefore, the particular solution for  $\nu(t)$  is:

$$V_p(t) = 0$$

(d) The roots of the characteristic equation are found from Equations 4.72 and 4.73 in the text.

$$S_{1} = -\alpha + \sqrt{\alpha^{2} - \omega_{0}^{2}} = -2.679 \times 10^{6}$$
$$S_{2} = -\alpha - \sqrt{\alpha^{2} - \omega_{0}^{2}} = -37.32 \times 10^{6}$$

The complementary solution is

 $\nu_c(t) = K_1 \exp(s_1 t) + K_2 \exp(s_2 t)$ 

and (since the particular solution is zero) the complete solution is  $v(t) = K_1 \exp(s_1 t) + K_2(s_2 t)$ 

The initial conditions are

 $\nu(0+) = 0$  and  $\nu'(0+) = 10^9$ 

Thus, we have

$$\nu(0+) = 0 = K_1 + K_2$$

 $v'(0+) = 10^9 = s_1K_1 + s_2K_2$ Solving, we find  $K_1 = 28.87$  and  $K_2 = -28.87$ . Finally, the solution is

 $v(t) = 28.87 \exp(s_1 t) - 28.87 \exp(s_2 t)$ 

$$i(t) = 0.025\cos(100t) + 0.00193\exp(s_1t) - 0.02693\exp(s_2t)$$