

電工學期中考參考解答

12/06/2006

1. (a)

We can write the following expression for the resistance seen by the 2-V source.

$$R_{eq} = 1 + \frac{1}{1/R_{eq} + 1/2}$$

The solutions to this equation are $R_{eq} = 2\Omega$ and $R_{eq} = -1\Omega$. However, we reason

that the resistance must be positive and discard the negative root. Then, we have


$$i_1 = \frac{2V}{R_{eq}} = 1A, \quad i_2 = i_1 \frac{R_{eq}}{2 + R_{eq}} = \frac{i_1}{2} = 0.5A, \quad i_3 = \frac{i_1}{2} = 0.5A, \quad \text{and} \quad i_6 = 0.125A.$$

(b)

$$P = IV = I^2 R, \quad P_3 = i_3^2 R_3 = 0.25W, \quad P_6 = i_6^2 R_6 = 1/32W = 0.03125W.$$

2. (a)

Node voltage analysis:

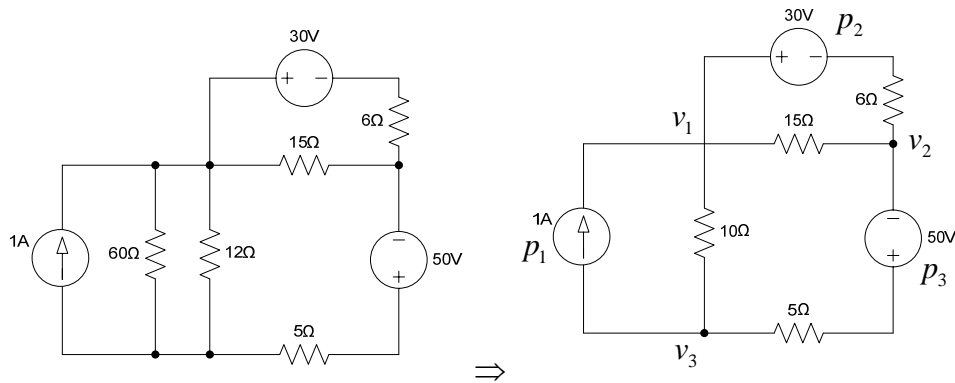

$$\begin{cases} -1 + \frac{v_1 - v_3}{10} + \frac{v_1 - 30 - v_2}{6} + \frac{v_1 - v_2}{15} = 0 \\ \frac{v_2 - v_1 + 30}{6} + \frac{v_2 - v_1}{15} + \frac{v_2 + 50 - v_3}{5} = 0 \end{cases}$$

Solving, we obtain $v_1 - v_2 = 30V$ and $v_2 - v_3 = -40V$


So the power supplied by each independent source is

$$p_1 = 1A \cdot (v_3 - v_1) = 10W, \quad p_2 = \left(\frac{v_2 - v_1 + 30}{6} \right) \cdot 30V = 0, \quad \text{and}$$

$$p_3 = \left(\frac{v_2 + 50 - v_3}{5} \right) \cdot 50V = 100W$$

(b)

Mesh current analysis:

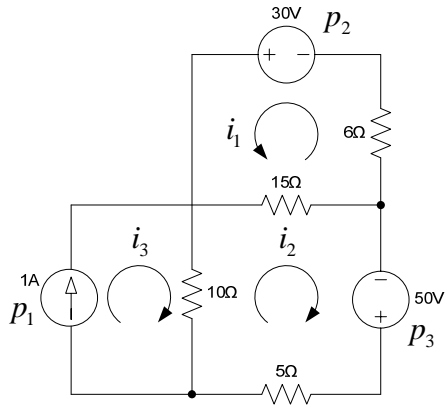

$$\begin{cases} i_3 = 1 \\ 15(i_1 + i_2) + 6i_1 = 30 \\ 5i_2 + 10(i_2 - i_3) + 15(i_2 + i_1) = 50 \end{cases}$$

Solving, we obtain $i_1 = 0$ and $i_2 = 2A$

So the power supplied by each independent source is

$$p_1 = 1A \cdot (10i_3) = 10W, \quad p_2 = i_1 \cdot 30V = 0, \quad \text{and} \quad p_3 = i_2 \cdot 50V = 100W$$

3. Applying KVL to the circuit, we obtain $L \frac{di(t)}{dt} + Ri(t) + v_c(t) = v_s = 50$.

For the capacitance, we have $i(t) = C \frac{dv_c(t)}{dt}$.

$$\text{So } \frac{d^2 v_c(t)}{dt^2} + \frac{R}{L} \frac{dv_c(t)}{dt} + \frac{1}{LC} v_c(t) = \frac{50}{LC}. \quad (1)$$

In dc steady state, since the capacitance acts as an open circuit, the steady-state voltage across it is 50 V. That is, $v_{cp}(t) = 50$.

Comparing Equation (1) with Equation 4.67 in the text, we find

$$\alpha = \frac{R}{2L} = 10^4, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 10^4, \quad \zeta = \frac{\alpha}{\omega_0} = 1.$$

Since we have $\zeta = 1$, this is the critically damped case. The roots are real and equal, and the complementary solution is

$$v_{cc}(t) = K_1 \exp(s_1 t) + K_2 t \exp(s_1 t), \quad \text{where } s_1 = -\alpha.$$

The complete solution is

$$v_c(t) = 50 + K_1 \exp(s_1 t) + K_2 t \exp(s_1 t).$$

The initial conditions are

$$v_c(0+) = 0 \quad \text{and} \quad i(0+) = 0 = C \left. \frac{dv_c(t)}{dt} \right|_{t=0}.$$

Thus, we have

$$v_c(0+) = 50 + K_1 = 0 \quad \text{and} \quad \left. \frac{dv_c(t)}{dt} \right|_{t=0} = 0 = s_1 K_1 + K_2.$$

Solving them, we find $K_1 = -50$ and $K_2 = -s_1 K_1 = \alpha K_1 = -5 \times 10^5$.

Finally, the solution is

$$v_c(t) = 50 - 50 \exp(s_1 t) - 5 \times 10^5 t \exp(s_1 t).$$

4. Writing KVL equations around the meshes, we obtain

$$\begin{cases} 5I_1 + j15(I_1 - I_2) = 20 \\ -j10I_2 + j15(I_2 - I_1) = 10 \end{cases}$$

Solving, we obtain

$$I_1 = 1.644 \angle 80.54^\circ, \quad I_2 = 2.977 \angle 74.20^\circ.$$

$$V_1 = 20 - 5I_1 = 20.335 \angle -23.50^\circ$$

$$v(t) = 20.335 \cos(\omega t - 23.50^\circ) V$$

$$v_{rms} = \frac{20.335}{\sqrt{2}} = 14.379 V$$

5. Using the voltage-division principle, we find $\frac{v_{out}}{v_{in}} = \frac{R}{\frac{1}{j\omega C} + R}$.

The input is $v_{in}(t) = 5 \cos(200\pi t) + 5 \cos(2000\pi t)$,

$$\text{for } \omega = 200\pi, \quad \frac{v_{out}}{v_{in}} = \frac{\sqrt{101}}{101} \angle 84.29^\circ, \quad \text{and for } \omega = 2000\pi, \quad \frac{v_{out}}{v_{in}} = \frac{\sqrt{2}}{2} \angle 45^\circ.$$

So the output in steady state conditions will be

$$v_{out}(t) = 0.4975 \cos(200\pi t + 84.29^\circ) + 3.5355 \cos(2000\pi t + 45^\circ).$$

6. (a)

The all-pass network has the unique characteristic of unity gain at all frequencies and a frequency-dependent phase relationship between output and input.

(b)

$$v_{in}(t) = \cos(\omega_1 t) + 2 \cos(2\omega_1 t)$$

$$v_{out}(t) = v_{in}(t - \tau_0) = \cos(\omega_1 t - \omega_1 \tau_0) + 2 \cos(2\omega_1 t - 2\omega_1 \tau_0)$$

For the transfer function $H(f) = \frac{V_{out}}{V_{in}}$,

$$\left| H\left(\frac{\omega_1}{2\pi}\right) \right| = \left| H\left(\frac{2\omega_1}{2\pi}\right) \right| = 1, \text{ that means } |H(f)| = 1 \text{ for any given frequency.}$$

$$\angle H\left(\frac{\omega_1}{2\pi}\right) = -\omega_1 \tau_0, \quad \angle H\left(\frac{2\omega_1}{2\pi}\right) = -2\omega_1 \tau_0, \text{ that means } \angle H(f) = -2\pi f \tau_0.$$

That is, the transfer function of the all-pass network must have a unity gain for all frequencies and a linear frequency-dependent phase. By that way, we can thus have a relationship as $v_{out}(t) = v_{in}(t - \tau_0)$ between output and input.